

# CARLETON UNIVERSITY

FINAL  
EXAMINATION  
April 1999

**DURATION 3 HOURS**

No. Of Students 39

Department Name & Course Number: Electronics 97.477

Course Instructor(s): Prof. Calvin Plett

AUTHORIZED MEMORANDA


Official Course Summary and Calculators Allowed

**Students MUST count the number of pages in this examination question paper before beginning to write, and report any discrepancy immediately to a proctor. This question paper has 3 pages.**

**This examination question paper MAY be taken from the examination room.**


## Question 1 (Total 30 Marks)


For the CMOS Opamp shown:

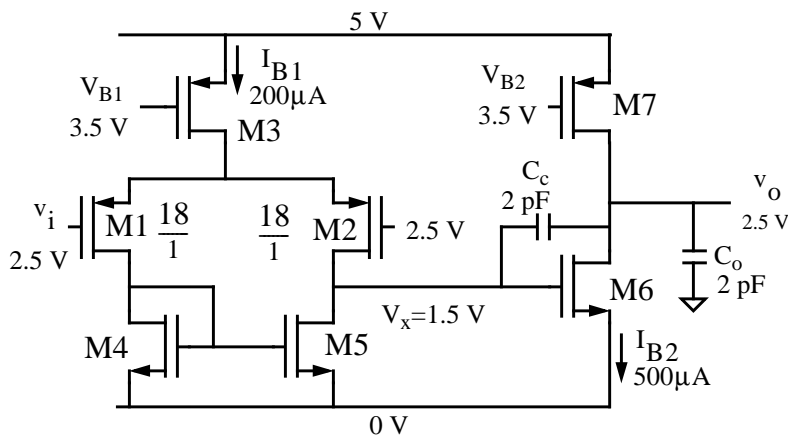

- With an opamp having a circuit as shown, and bias currents and other parameters as specified, pick and specify any necessary transistor sizes to establish an internal bias voltage level  $V_x$  of 1.5V as shown, and an output bias of 2.5 V.
- Determine the DC magnitude gain of the two stages ( $v_x/v_i$ ,  $v_o/v_x$ ) and the overall DC gain in dB.
- Calculate the pole and zero frequencies and the UGBW of the opamp in Hertz. Determine if the opamp is stable. Explain your reasoning.
- Find the positive and negative common-mode input range. Identify which transistors will leave the saturation region.

**Question 2 (Total 10 marks)**

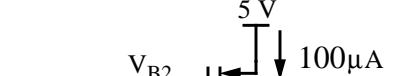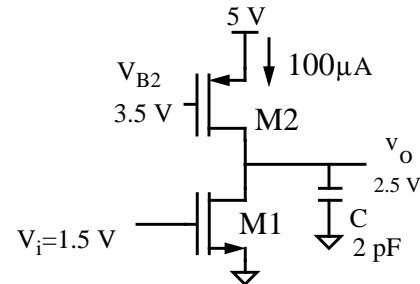- a) A first-order filter has a passband from DC to 20 kHz, with a passband voltage gain of 5. An opamp used to realize this filter has a unity-gain frequency of 1 MHz and a DC gain of 80 dB. Calculate the maximum gain error for this filter and the frequency for which this maximum gain error occurs.
- b) For the following circuit with  $v_{tn} = 0.5\text{ V}$ , the nominal input voltage is 1.5 V at which time the nominal current is 100  $\mu\text{ A}$  and the output voltage is 2.5 V. Calculate the positive and negative slew rate for the input at  $1.5 \pm 0.5\text{ V}$ , that is, it is switching between 2 V and 1V.
- 



**Question 3 (Total 15 Marks)**


A circuit has the transfer function

$$\frac{v_o}{v_i} = -\frac{z^{-1}}{1 - 2z^{-1} + 2z^{-2}}$$

- Determine the magnitude of the frequency response in the ideal sampled-data domain at DC,  $f_{clock}/4$ ,  $f_{clock}/2$ , and  $f_{clock}$ .
- Suppose the input frequency is fixed at  $5/4$  of the clock frequency and the frequency range from DC to twice the clock is looked at. Sketch the frequency spectrum seen by a spectrum analyzer, with approximate relative amplitudes. Explain your reasoning.
- Determine the first four points ( $n = 0, 1, 2, 3$ ) of the response in the time domain for a 1 V step input at  $t = 0$ .

### **Question 4 (Total 15 Marks)**


For the circuit shown below:

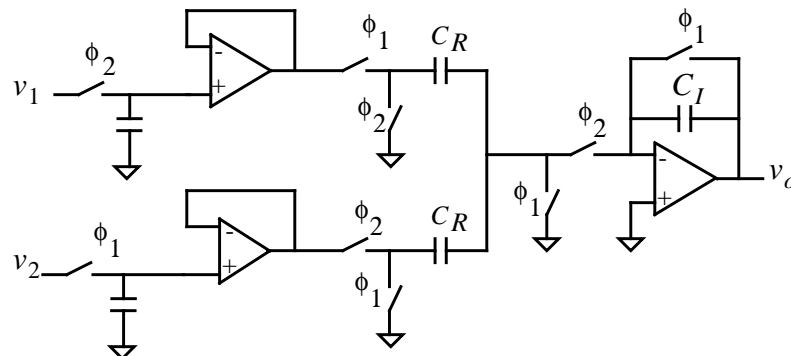

- Do a charge balance analysis for the above circuit.
- Determine the Z transform in the form  $v_o = H_1(z)v_1 + H_2(z)v_2$ .

**Question 5 (Total 15 marks)**

For the circuit shown below:

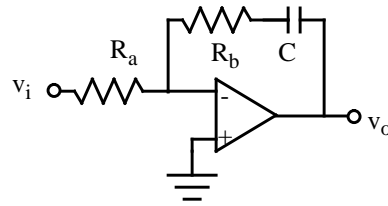

$$R_a = 1 \text{ M}\Omega \quad R_b = 2 \text{ M}\Omega \quad C = 5 \text{ pF}$$

- Find the transfer functions relating the noise due to  $R_a$  and  $R_b$  to the output.
- Calculate the power spectral density at the output due to  $R_a$  and  $R_b$  at 100 kHz.
- Find the integrated output noise due to  $R_b$  up to a bandwidth of 1 MHz.
- The opamp has input referred thermal noise voltage  $v_n$  of  $20 \text{ nV}/\sqrt{\text{Hz}}$ . Sketch the output noise density due to  $v_n$  from 1 kHz to 1 MHz (for the same circuit as above).

**Question 6 (Total 15 marks) (Full Marks will not be given if answer is not grammatical).**

- Define and discuss in no more than 3 pages, replication, aliasing, and  $\sin(x)/x$  in sampled data systems. Describe how these effects would be seen in both the frequency domain and in the time domain.