

Your Name:

Student Number:

1


Only official course summary allowed. Do all questions directly on this paper. For extra space or for rough work, use back if necessary. Time 1 hour. - Total Marks 20%.

**Question 1. (6 Marks)** For the circuit shown, assume  $\lambda_n = 0$ ,  $\lambda_p = 0.1$ , CMRR =  $\infty$ . The following two measurements were done

- i)  $v_i = 0 \text{ V}$ ,  $v_o = -0.1 \text{ V}$ .
- ii)  $v_i = 0.02 \text{ V}$ ,  $v_o = 0.4 \text{ V}$ .

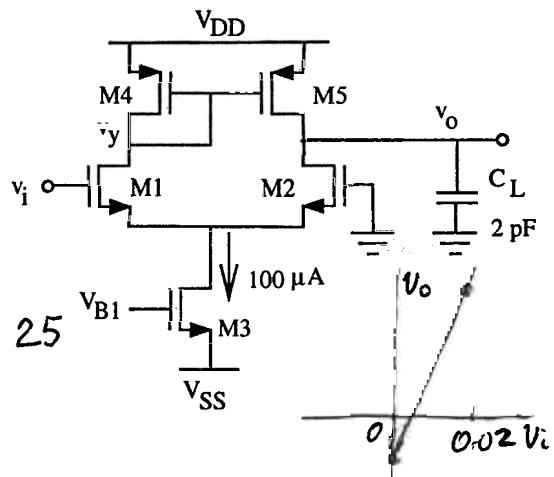a) Find the difference-mode gain.

$$A_d = \frac{\Delta v_o}{\Delta v_i} = \frac{0.4 - (-0.1)}{0.02 - 0} = \frac{0.5}{0.02} = 25$$



b) What is the offset referred to the input?

$$v_{o,\text{in}} = \frac{v_{o,\text{out}}}{A_d} = \frac{-0.1}{25} = -0.004 = -4 \text{ mV}$$

c) What is the common-mode component of the input voltage for the case ii) above?

$$v_c = \frac{v_1 + v_2}{2} = \frac{0.02 + 0}{2} = 0.01 \text{ V}$$

d) Find the output resistance  $r_o$  of the amplifier.

$$A_d = r_o = \frac{1}{I(\lambda_n + \lambda_p)} = \frac{1}{50 \mu \text{A}(0. + 0.1)} = \frac{1}{5 \mu} = 200 \text{ k}\Omega$$

e) Find the transconductance of  $M_2$ .

$$A_d = g_m r_o, \quad g_m = \frac{A_d}{r_o} = \frac{25}{200 \text{ k}\Omega} = 125 \mu \text{A/V}$$

f) Find the UGBW in MHz.

$$\omega_u = \frac{g_m}{C} = \frac{125 \mu}{2 \text{ p}} = 62.5 \text{ Mrad/sec}, \quad f_{u\text{GBW}} = \frac{62.5 \text{ M}}{2\pi} = 9.95 \text{ MHz}$$