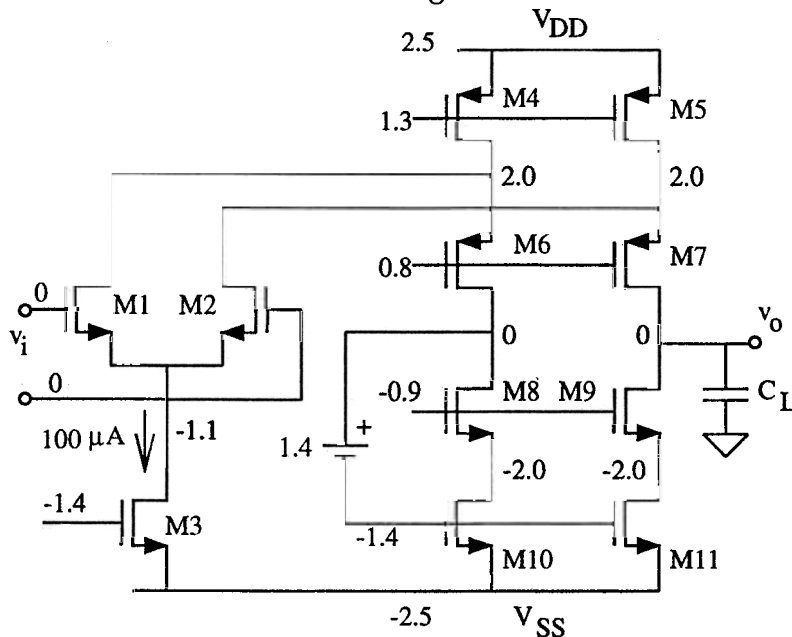


Question 2. (5 Marks) A folded cascode amplifier, similar to the one designed in the lab is shown. All the bias voltages are shown as well. Assume $V_{TP} = -0.9V$, $V_{TN} = 0.8V$.



a) Estimate the input common-mode range, both directions

- negative: nmos $V_{on} = V_{gs} - V_T = 0.3V$, min $V_{D3} = -2.5 + 0.3 = -2.2V$
 $V_{G1} = 1.1V$, min $V_{in} = -2.2 + 1.1 = -1.1V$
- 2 positive: V_{D1}, V_{D2} fixed at $2.0V$ (by sources of M_6, M_7)
 increase V_i to $2.0V + V_T = 2.8V$

b) Estimate the output voltage range both directions.

- negative: $-2V$ fixed by sources of M_{10}, M_9
 $V_{D9, min} = V_{on} = 0.3V \therefore V_{O, min} = -1.7V$
- 2 positive: $+2V$ at V_{S7} fixed by source of M_7
 $|V_{D7, min}| = 0.3V$, $\therefore V_{O, max} = +1.7V$

c) For $C_L = 2 pF$, what is the slew rate?

1 Slew Rate = $\frac{I_3}{C_L} = \frac{100\mu A}{2pF} = 50V/\mu sec$