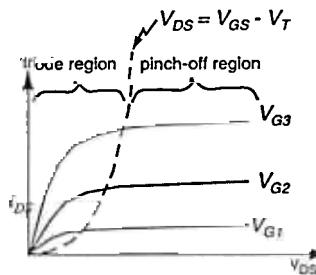


97.477 Analog Integrated Electronics, Summary

Transistor Characteristics (N Channel)



Simple Square Law Equations

$$\text{Triode: } I_{DS} = k_p \frac{W}{L} \left(V_{GS} - V_T - \frac{V_{DS}}{2} \right) V_{DS} \quad V_{DS} < V_{GS} - V_T$$

$$\text{Pinch Off: } n: I_{DS} = \frac{k_p W}{2 L} (V_{GS} - V_T)^2 \quad V_{DS} > V_{GS} - V_T$$

$$(\text{use } |V| \text{ for pmos}) \quad |I_{DS}|_p = \frac{k_p W}{2} \left(\frac{W}{L} \right)_p (|V_{GS}| - |V_T|)^2$$

$$K_{pn} = \frac{\mu_n \epsilon_{ox}}{t_{ox}} = \mu_n C_{ox} \quad K_{pp} = \frac{\mu_p \epsilon_{ox}}{t_{ox}} = \mu_p C_{ox}$$

Channel Length Modulation slope factor $\lambda: \frac{\Delta I_d}{I_d} = \lambda \Delta v_d, \quad \lambda \propto 1/L$.


Transistor equations including channel length modulation:

$$\text{Triode: } I_{DS} = K_p \frac{W}{L} \left(V_{GS} - V_T - \frac{V_{DS}}{2} \right) V_{DS} (1 + \lambda v_{DS}) \quad \text{Pinch Off: } I_{DS} = \frac{K_p W}{2 L} (V_{GS} - V_T)^2 (1 + \lambda v_{DS})$$

Body Effect γ - nonzero V_{SB} changes the threshold voltage as:



$$V_T = V_{TO} + \gamma [\sqrt{2|\phi_F|} + V_{SB} - \sqrt{2|\phi_F|}] \quad \text{typically } 2|\phi_F| = 0.7 \text{ V} \quad \text{Result: threshold is increased}$$

Small Signal Parameters in Pinch-Off

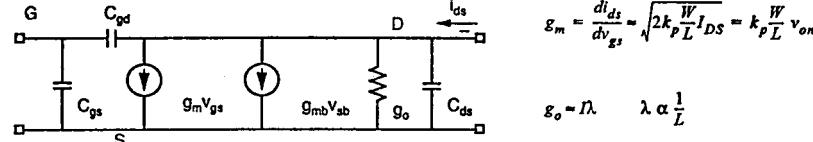

Diode Connection and Current Mirrors: Diode Connection: as M_1 below, connect drain and gate, hence

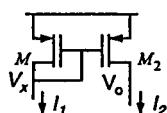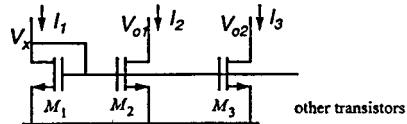$V_{DS} = V_{GS}$, if $V_{DS} > V_T$, then always in pinch off. Small signal model with $g = g_m + g_o$.




Current Mirror: $I_2 = I_1$ if $V_{o1} = V_x$. Otherwise currents will not match exactly because of output impedance e.g., at V_{o1} it is given by r_o of M_2 . Can increase by using cascode or other types of mirrors.

Winter 2000


97.477 Analog Integrated Electronics, Summary

Gain Stages (Shown with NMOS Drivers)

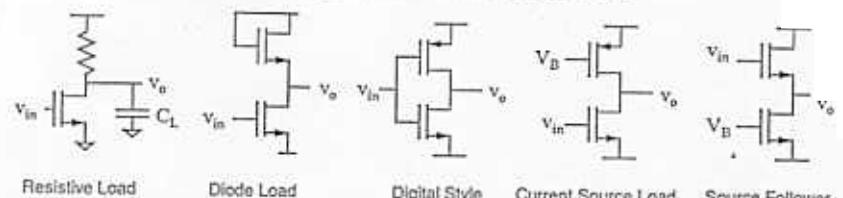

$$\frac{V_o}{V_{in}} = \frac{g_m}{g_{d1} + g_{d2}} \quad \frac{V_o}{V_{in}} = \frac{g_{m1}}{g_{m2} + g_{d11} + g_{d12}} \quad \frac{V_o}{V_{in}} = \frac{g_{m1} + g_{m2}}{g_{d11} + g_{d12}} \quad \frac{V_o}{V_{in}} = \frac{g_{m1}}{g_{d11} + g_{d12}} \quad \frac{V_o}{V_{in}} = \frac{g_{m1}}{g_{m1} + g_{d11}}$$


Gain Stages (Shown with PMOS Drivers)

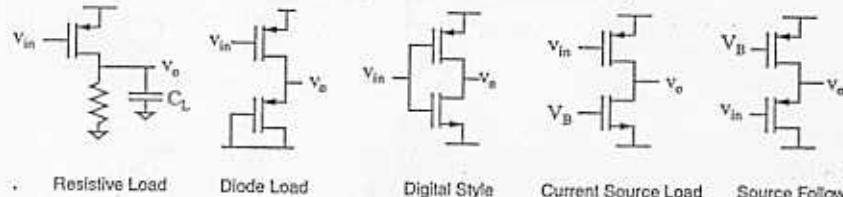


$$\frac{V_o}{V_{in}} = \frac{g_m}{g_{d1} + g_{d2}} \quad \frac{V_o}{V_{in}} = \frac{g_{m1}}{g_{m2} + g_{d11} + g_{d12}} \quad \frac{V_o}{V_{in}} = \frac{g_{m1} + g_{m2}}{g_{d11} + g_{d12}} \quad \frac{V_o}{V_{in}} = \frac{g_{m1}}{g_{d11} + g_{d12}} \quad \frac{V_o}{V_{in}} = \frac{g_{m1}}{g_{m1} + g_{d11}}$$

Small Signal Model

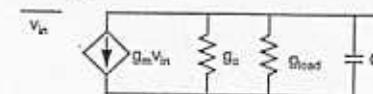
The gain of each, except for the last two is $\frac{g_m}{g_{eq}}$ where $g_{eq} = g_m + g_{load}$, and model is as below



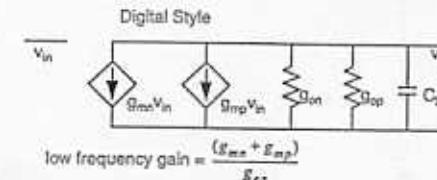where g_{load} and C_L are determined by the load


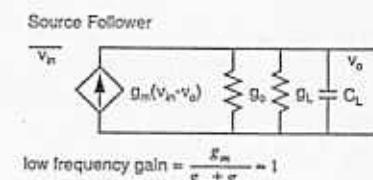
$$\text{low frequency gain} = \frac{(g_{m1} + g_{m2})}{g_{eq}}$$



$$\text{low frequency gain} = \frac{g_m}{g_m + g_{eq}} \approx 1$$

Slew Rate: Use current into capacitor, calculate $i = C \frac{\Delta v}{\Delta t}$ where $\frac{\Delta v}{\Delta t}$ is the slew rate.

Pole Frequency: $\omega_p = \frac{1}{r_{eq} C}$

$$\text{where } r_{eq} = \frac{1}{g_{eq}}$$

$$\text{Unity Gain Bandwidth: } UGBW = \frac{g_m}{C_L}$$