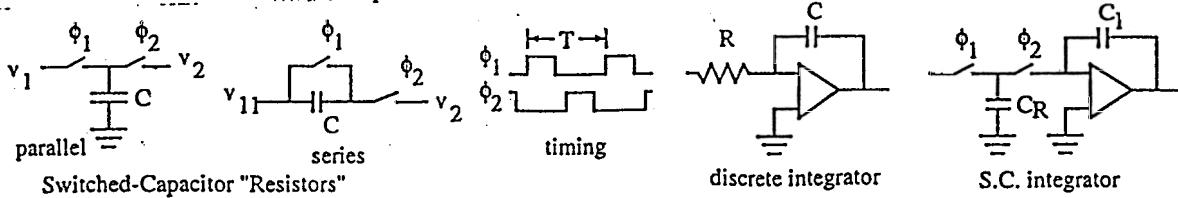



D Switched-Capacitor Filter Summary

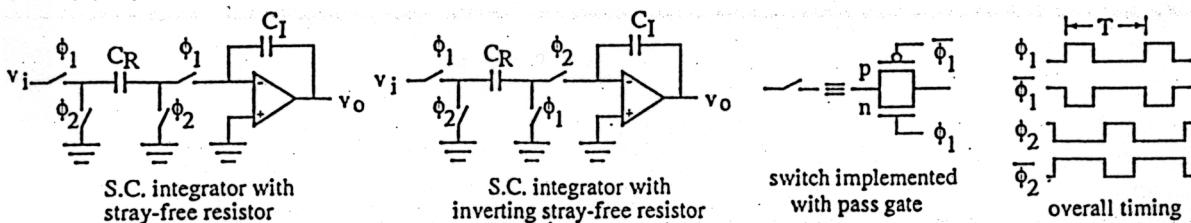97.477 Official Course Summary
Winter 2000, Page 3



$$R_{equiv} = \frac{T}{C_R} \quad \text{thus: } \frac{v_o}{v_i} = \frac{1}{sC_I R_{equiv}} = \frac{1}{sT C_I} = \frac{\alpha}{sT} \quad \text{where } \alpha = \frac{C_R}{C_I}$$

For a general filter, the pole frequency is given by $1/(2\pi RC_I) = f_{pole} = \alpha/(2\pi T) = \alpha f_{clock}/(2\pi)$. To avoid problems with stray capacitances, stray free resistors are used:



$$\sum i = \sum \frac{\Delta Q}{T} = \sum \frac{C \Delta V}{T} = 0$$

Where ΔV represents the difference in the voltage across a capacitor before and after the transition, expressed as $v_n, v_{n-\frac{1}{2}}, \dots$ etc. Result: difference equation. For integrators shown above:

- 1) $v_{o,n} = v_{o,n-1} - \alpha v_{in}$ for regular integrator with t_n at the end of ϕ_1
- 2) $v_{o,n} = v_{o,n-1} + \alpha v_{i,n-\frac{1}{2}}$ for negative resistor with t_n at the end of ϕ_2
- 3) $v_{o,n} = v_{o,n-1} + \alpha v_{i,n-1}$ for negative resistor with t_n at the end of ϕ_1

Z transform - replace the subscripts $n-1, n-\frac{1}{2}$ and n with $z^{-1}, z^{-\frac{1}{2}}, z^0$ multiplier. For example, the integrators from last section become:

$$1) \frac{v_o}{v_i} = -\frac{\alpha}{1-z^{-1}} \quad 2) \frac{v_o}{v_i} = \frac{\alpha z^{-\frac{1}{2}}}{1-z^{-1}} \quad 3) \frac{v_o}{v_i} = \frac{\alpha z^{-1}}{1-z^{-1}}$$

Here, z^{-1} represents a delay of 1 clock period T , where $z = e^{sT}$

- 2) The z transform is just a substitution for the Laplace transform for a delay. Here, the delay $T = 1/f_s$ is one period of the sampling clock.

$$z = e^{sT} = e^{j2\pi f T} = e^{j2\pi \frac{f}{f_s}} = 1/2\pi \frac{f}{f_s} = \cos\left(2\pi \frac{f}{f_s}\right) + j \sin\left(2\pi \frac{f}{f_s}\right)$$

This is a vector of magnitude 1 and angle is $\frac{f}{f_s}$ as a fraction of 360° . This results in the following table for frequency and values of z^{-1} .

$$\frac{f}{f_s} \quad 0 \rightarrow \quad 1/8 \searrow \quad 1/4 \downarrow \quad 1/2 \leftarrow \quad 1 \rightarrow$$

$$z^{-1} \quad 1 = 1/0 \quad \frac{1}{\sqrt{2}} - j \frac{1}{\sqrt{2}} = 1/ - 45^\circ \quad -j1 = 1/ - 90^\circ \quad -1 = 1/ - 180^\circ \quad 1 = 1/ - 360^\circ = 1/0$$

