

Sample Final Exam

FinalDay, FinalMonth, FinalYear

ELEC4708: Advanced Digital Electronics

Department of Electronics, Carleton University

Instructor: Maitham Shams

Exam Duration: 3 hour

Booklets: None

Number of Pages: 10 with this

Aids Allowed: Calculator

Number of Students: FinalNumber

Last Name: _____

First Name: _____

ID: _____

CANNOT BE TAKEN OUTSIDE EXAM AREA

Q1	Q2	Q3	Q4	Q5	Q6	Total
/30	/15	/15	/15	/10	/15	/100

-
- Write your name and ID number clearly on all pages. No questions answered.
 - Attempt all questions. Marking scheme for all questions are given.
 - If in a question you are asked to make an assumption, then you must use it.
 - Formula

$$\hat{D} = NF^{\frac{1}{N}} + P, \quad F = GBH, \quad \hat{f} = F^{\frac{1}{N}}, \quad H = \frac{C_{out}}{C_{in}}$$

$$f = gh, \quad b = \frac{C_{onpath} + C_{offpath}}{C_{onpath}}, \quad G = \Pi g_i, \quad P = \Sigma p_i$$

- Data

$$V_{DD} = 1.8 \text{ v}, \quad V_{tn} = 0.5 \text{ v}, \quad V_{tp} = 0.5 \text{ v}$$


[1] (30 marks, 1 marks each) Mark True or False.

1. Carry-Select Adder uses double the hardware for calculating all SUM bits. True False
2. Carry Signal C_i is the group generate signal up to bit i (i.e. $G_{i:0}$). True False
3. Body (substrate) of NMOS transistors are usually grounded. True False
4. NMOS transistors are best in passing 1s. True False
5. Symmetric functions have similar pull-up and pull-down networks. True False
6. Purely combinational logic is impossible to be described inside an always block in Verilog. True False
7. Clock gating may produce false clock edges. True False
8. in modern CMOS IC technologies diffusion capacitances are much smaller than gate-oxide capacitances. True False
9. Last-arriving inputs should be connected to the transistors attached to the power rails (i.e. GND and V_{DD}). True False
10. In modern CMOS digital circuits electron velocity doesn't saturate. True False
11. MOS threshold voltage is independent of source-body potential. True False
12. A positive-edge-triggered flip-flop is transparent when clock is 1. True False
13. Ignoring the diffusion capacitances, the stage effort for minimum delay is e . True False
14. In modern CMOS digital circuits junction leakage current is less than subthreshold leakage current. True False
15. Dynamic power dissipation increases linearly with frequency of operation. True False

 16. A junction capacitance gets larger as the magnitude of the reverse-biased potential across the junction increases. True False
17. Fast multi-input adders are simply produced by cascading 2-input adders. True False
18. Delay of N serially connected MOSFETs increases quadratically with N . True False
19. CMOS circuits have higher static power dissipation at lower temperatures. True False
20. Leakage current through the gates of MOSFETS increases as the gate-oxide thickness reduces. True False
21. CVSL is a ratioless CMOS logic style. True False
22. The sharper the input signal, the higher the short-circuit current through a CMOS inverter. True False
23. A problem with Domino logic gates is that they are inherently non-inverting. True False
24. The major block in a subtractor circuit, is an adder. True False
25. CPL logic gates need a couple of PMOS transistors to produce full-swing outputs. True False
26. Static sequencing elements do not use clock signals, but dynamic sequencing elements do. True False
27. When comparing two signed numbers A and B , we know that A is larger than B , if $A - B$ produces a carry-out. True False
28. Regular latches should not be driven by brief pulses for sequencing. True False
29. Semidynamic flip-flops have static inputs and dynamic outputs. True False
30. The output of a symmetric function is inverted when all its inputs are inverted. True False

[2] (15 marks) Show the transistor-level implementations of 3-input XOR gate in Pseudo NMOS, conventional CMOS, CPL, and DCVSL (your book calls it CVSL), and single-rail (regular) Domino logic. Assume that inputs A, B, C and their complements are all available. Use minimum number of transistors in each case.

[3] (15 marks) Consider the following circuit. The inverter has an input capacitance of 6 units (i.e. twice as large as the unit inverter). The output capacitance is 900 units.



- What is the optimum number of stages for lowest delay? Modify (sketch) the circuit for minimum delay by adding inverters if necessary. Hint: Assume optimum stage effort is 4.
- Calculate the minimum possible delay for the original and modified circuit, if the delay of a unit inverter is 15 ps in the technology.
- Find the sizes of all unknown PMOS and NMOS transistors in the modified circuit.
- How does the delay of the modified circuit change if the power-supply voltage is reduced to 1.2 v from 1.8 v?

[4] (15 marks) Sketch the block diagram and logic-gate level diagram of an 8-bit Carry-Lookahead Adder using valency-4 PG logic (two 4-bit adder blocks). Only use Inverters, two-input AND, OR, and XOR gates. Do not use any multi-input logic gates. Calculate the delay through the critical path, if the gate delays are: $t_i = 15$ ps (for INV), $t_a = 25$ ps (for AND), $t_o = 30$ ps (for OR), and $t_x = 40$ ps (for XOR), respectively.

[5] (10 marks) Draw the transistor-level circuit diagram of a positive-edge-triggered D-flipflop with synchronous set and reset control signals. Also draw the circuit diagram of one with asynchronous set and reset control signals. The inputs are D , ϕ , $\bar{\phi}$, $\overline{\text{set}}$, and $\overline{\text{reset}}$. The outputs are Q and \bar{Q} . The circuit diagram **MUST** show all transistors. You may start with logic-gate diagrams, then convert to transistor-level circuits.

[6] (15 marks) The Sum and Carry-Out of a full-adder cell are given by

$$S = A \oplus B \oplus C$$

$$C_o = AB + AC + BC$$

The inputs A, B and C have 0.5, 0.5 and 0.25 probabilities of being 1, respectively. Find the power consumption for the Sum and Carry-Out output nodes. Assume that each of these outputs have a load capacitance of 100 fF and the circuit operates at 1 GHz. Ignore the internal node capacitances.