

**Final Exam**  
**Sample Final Exam**  
**ELEC-5801: High-Speed and Low-Power VLSI**  
Department of Electronics, Carleton University

<b>Instructor:</b> Maitham Shams	<b>Exam Duration:</b> 3 hours
<b>Booklets:</b> None	<b>Number of Pages:</b> 9 with this
<b>Aids Allowed:</b> Scientific Calculator	<b>Number of Students:</b> 7

**Last Name:** \_\_\_\_\_  
**First Name:** \_\_\_\_\_  
**ID:** \_\_\_\_\_

Q1	Q2	Q3	Q4	Q5	Total
/30	/20	/15	/15	/20	/100

---

**Formula and Data**

$$I_n(\text{sat}) = 400 \frac{W}{L} (V_{GS} - V_{TN})^{1.30} \mu\text{A}$$

$$I_p(\text{sat}) = 150 \frac{W}{L} (V_{GS} - V_{TP})^{1.50} \mu\text{A}$$

$$V_{DD} = 1 \text{ V}$$

$$V_{TN} = 0.40 \text{ V}$$

$$V_{TP} = 0.35 \text{ V}$$

$$L_{\min} = 90 \text{ nm}$$

$$t_{ox} = 25 \text{ nm}$$

$$\epsilon_{ox} = 3.9 \times 8.854 \times 10^{-14} \text{ F/cm}$$

**[1] True or False****(30 marks, 0.5 each)**

1. At 100 MHz, the power dissipation of a modern MCML circuit is lower than its conventional CMOS version.  True  False
2. In  $\alpha$ -power law,  $\alpha = 2$  for long channel devices.  True  False
3. Dynamic CMOS circuits usually don't have short-circuit energy dissipation.  True  False
4. Abstraction is a powerful technique commonly applied in analog circuit design.  True  False
5. Dynamic circuits have to maintain a minimum clock frequency to avoid losing data.  True  False
6. Small voltage swing is a major factor for the superiority of MCML gates in speed compared to conventional CMOS gates.  True  False
7. An asynchronous circuit always consumes less energy than its synchronous counterpart.  True  False
8. In a multi- $V_T$  digital circuit, the critical path uses low- $V_T$  transistors.  True  False
9. When a static logic gate is not switching, there is always a path connecting the output to the power supply or ground.  True  False
10. Progressive transistor sizing improves speed of a fabricated IC by 10% or more.  True  False
11. Speed-independent circuits function correctly regardless of wire delays.  True  False
12. A disadvantage of dynamic CMOS circuits is that they produce glitches.  True  False
13. In a pseudo-NMOS logic gate, the lower the load resistance, the higher the nominal output low,  $V_{OL}$ .  True  False
14. Higher speed is always associated with higher power consumption.  True  False
15. A PTL circuit usually has a higher device count compared to its conventional CMOS counterpart.  True  False
16. Tree-like structures are generally less prone to glitches than chain-like structures.  True  False
17. The input resistance of an ideal logic gate is zero.  True  False
18. EMI is higher in an asynchronous circuit compared to its synchronous version.  True  False
19. Pre-computation is a proven power-reduction technique for comparators.  True  False
20. A limitation of the basic domino CMOS circuits is that they can only implement non-inverting cascaded functions.  True  False
21. pipelining a circuit reduces its latency.  True  False

22. In conventional CMOS circuits all of the energy eventually goes to ground.  True  False
23. The smaller the gate-oxide thickness, the lower the delay.  True  False
24. Electron mobility is a constant factor in modern CMOS IC circuits.  True  False
25. DCVSL is a ratio-less CMOS logic style.  True  False
26. Clock skew is becoming less of a problem by increasing integration density.  True  False
27. The overlap gate-source and gate-drain capacitances experience Miller Effect during switching.  True  False
28. The goal of parallelism is to sacrifice area for reducing power consumption or increasing speed.  True  False
29. The lower the slope of the input to a CMOS inverter, the higher the short-circuit energy dissipation.  True  False
30. In deep saturation, the effective channel length is shorter than the physical distance between the source and drain of a MOSFET.  True  False
31. The diffusion capacitances in a CMOS circuit may be ignored in calculating the delay, because the gate-oxide capacitances are much larger.  True  False
32. Leakage current through the gates of MOSFETS increases as the gate-oxide thickness reduces.  True  False
33. Any MOSFET with a feature length below a micron is considered a short-channel device.  True  False
34. Driving a large load in one stage is faster than driving it through two stages.  True  False
35. An XOR gate is considered delay insensitive the way it is normally operated in synchronous circuits.  True  False
36. In an 8-input conventional CMOS NAND gate, the NMOS transistor closest to the output usually has the highest  $V_T$ .  True  False
37. In using multiple or dual supplies the designers attempt to equalize the delays through the different paths.  True  False
38. The maximum value of a reversed-biased diffusion capacitance is when the applied potential across it is closer to zero.  True  False
39. An  $n$ -input NAND gate has a lower logical effort than an  $n$ -input NOR gate.  True  False
40. In an ideal logic gate the low and high noise margins are both zero.  True  False

41. In DCVSL circuits, the rising delay is always larger than falling delay.  True  False
42. Last-arriving inputs should be connected to the transistors attached to the power rails (i.e. GND and  $V_{DD}$ ).  True  False
43. A multiplier is usually more power consuming than several adders with the same input sizes.  True  False
44. The static operation of a conventional CMOS logic gate depends on its fan-out.  True  False
45. Delay of N serially connected MOSFETs increases quadratically with N.  True  False
46. CPL logic gates need a couple of PMOS transistors to produce full-swing outputs.  True  False
47. A level-restorer is needed when a circuit using a higher  $V_{DD}$  connects to a circuit with a lower  $V_{DD}$ .  True  False
48. When driving a very large capacitance it is better to use a tri-state buffer with a single stack of transistors at the output rather than a double stacked one.  True  False
49. Since MOSFET is a symmetric device, its source and drain terminals are identified by their relative voltage potentials.  True  False
50. Power dissipation remains almost constant in fixed-voltage technology scaling.  True  False
51. In saturation mode, MOS current is totally independent of source-to-drain potential.  True  False
52. Dynamic power dissipation of MCML gates increases linearly with frequency.  True  False
53. Scaling both  $V_{DD}$  and  $V_T$  doesn't affect static power dissipation.  True  False
54. Short-channel devices have wider saturation region (in I-V curve) compared to long-channel devices operating within the same permissible voltage range.  True  False
55. Charge-sharing is more of a problem in a dynamic CMOS gate with a large output capacitance compared to its internal node capacitances.  True  False
56. Lower power dissipation is a definitive advantage of asynchronous circuits.  True  False
57. If used for short-channel devices, Shockley's square law over-estimates the current.  True  False
58. By enlarging the sizes of the logic gates along a path, the overall delay decreases.  True  False
59. It is impossible to implement a non-inverting function of the the primary inputs in one stage using conventional CMOS style.  True  False
60. Reducing the threshold voltage in digital CMOS circuits improves speed and reduces static power dissipation.  True  False

**[2] General Delay and Power Calculations****(20 marks)**

1. A two-input NAND gate in 90 nm technology that drives a 100 fF load in 50 ps, with equal rising and falling delays.

(a) Design this logic gate, i.e. find transistor sizes.

(b) What is the maximum frequency of operation while maintaining a full-swing output?

(c) What is the capacitive load at each input of this logic gate?

2. A CMOS chip fabricated in 90 nm technology operates at a maximum frequency of 3 GHz and dissipates 5 w with  $V_{DD} = 1$  V. The very same chip is then scaled-down and fabricated in 65 nm technology with  $V_{DD} = 0.9$  V.

(a) What is the maximum frequency of operation, approximately?

(b) What is the power dissipation, approximately?

**[3] CMOS Logic Styles****(15 marks)**

Consider the following Boolean function  $Z = \overline{AB + DE + C(AE + DB)}$ .

1. Implement in Conventional CMOS logic style with minimum number of transistors.

2. Implement in PTL with full-swing output.

**[4] Delay Optimization (Logical Effort)****(15 marks)**

A 6-input OR gate receives its input from an inverter and drives a capacitive load. The ratio of the output load to the input capacitance of the inverter is  $H$ . Which of the following two configurations for implementing this logic gate is better in terms of delay.

1. Input Inverter + (6-input NOR + Inverter) + Load

2. Input Inverter + (3-input NOR + 2-input NAND) + Load



**[5] Power Optimization (Switching Activity)****(20 marks)**

John wants to implement the function in the next pages with the given input probabilities. Mike sees the circuit and tells Mike that you have wired the gates such that it consumes the highest possible energy. Then Mike shows John how to do the wiring to minimize the energy consumption. On the figures show how John connected the inputs and the gates, and how Mike fixed it. Next calculate the energy savings by using Mike's method compared to John's by filling the table and the corresponding box. Finally write what general rule or rules Mike used to achieve the energy savings. Note that all internal nodes and the output have the same load capacitance and all other factors are ignorable. Use this page for your rough work.



$$Z=(A+B+C)(DEF)$$

Input	A	B	C	D	E	F
$P_1$	0.3	0.5	0.8	0.7	0.4	0.2

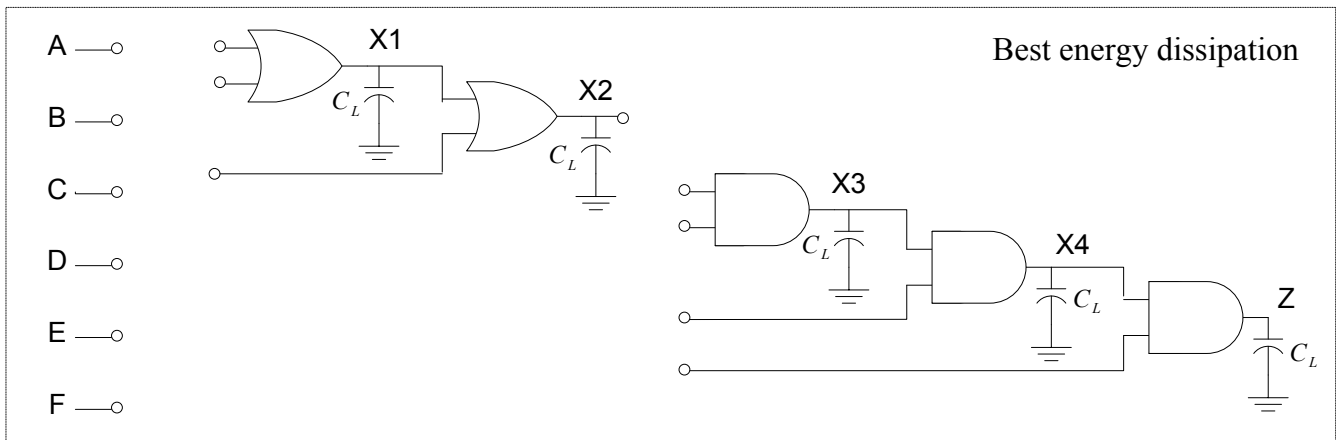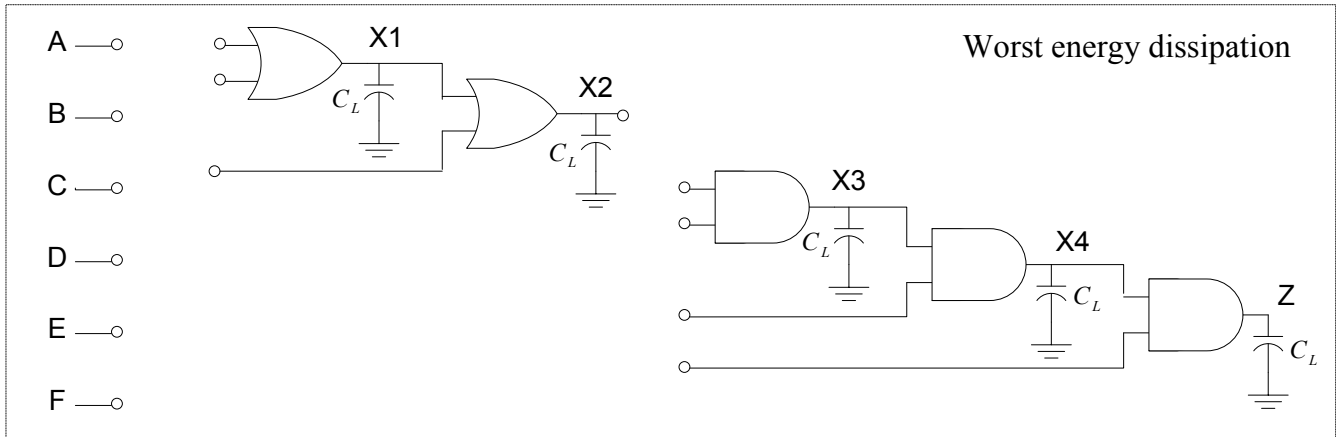

Node	Worst Case			Best Case		
	$P_0$	$P_1$	$\alpha$	$P_0$	$P_1$	$\alpha$
X1						
X2						
X3						
X4						
Z						

$$E_{Saved} = \frac{E_{Best} - E_{Worst}}{E_{Worst}} =$$

What is(are) the rule(s) to be used for lowest energy dissipation?

.....

.....

.....

.....