 


Bit Serial Adder



Is very suitable when the data is coming in/going out serially.
 - very small and can deal with data streams at ~ 1Ghz (0.18um)

Carry-Save Adder (CSA) and Carry Save Trees

Regular Way

- add each column and bring carries over to the next column
- the $C_n + A_n + B_n = \{C_{n+1}, SUM_n\}$

			carry-bits
	000110		
A	10011	19	
+ B	+ 00110	6	
	011001	25	



This calculation can also be done if we separately produce the sum and carry bits and add them at the end!

			19
	10011		
	+ 00110		6
(A xor B) IntSum	10101		21
Carry	00010		2*2
	011001		25

So far this isn't particularly useful, but if we look at a 3 input adder:

A	01100	12	INDEPENDENTLY, for each column produce a sum and carry bit with a normal full-adder
+ B	10011	19	
+ C	00110	6	
Sum bits	11001	25	
Carry bits	00110	6*2	
Final Result	100101	37	Eventually add them up for the final result.

A CSA adder representation

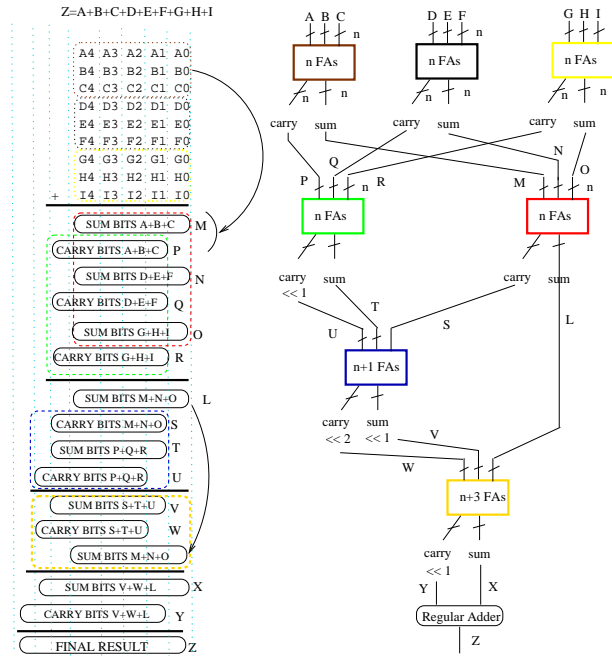 

Multipliers Intro

A	1 0 1 1 0	22
* B	0 1 1 0 1	13
	1 0 1 1 0	
	0 0 0 0 0	
	1 0 1 1 0	
	1 0 1 1 0	
	0 0 0 0 0	
	1 0 0 0 1 1 1 1 0	286

Output width is width of A + width of B

If the multiplier is implemented with CSA adders it is a 'Wallace Tree'

Delay = 4 Full Adders + regular cleanup adder

Signed Multipliers: Sign extend and remove extra logic

A	1 1 1 1 1 0 1 1 0	-10
* B	0 0 0 0 0 1 1 0 1	13
	1 1 1 1 1 1 1 0 1 0	
	0 0 0 0 0 0 0 0 0 0	
	1 1 1 1 1 1 1 0 1 0	
	1 1 1 1 1 1 1 0 1 0	
	0 0 0 0 0 0 0 0 0 0	
	0 0 0 0 0 0 0 0 0 0	
	0 0 0 0 0 0 0 0 0 0	
	0 0 0 0 0 0 0 0 0 0	
	0 0 0 0 0 0 0 0 0 0	
	1 1 0 1 1 1 1 1 1 0	-130

Output width is width of A + width of B