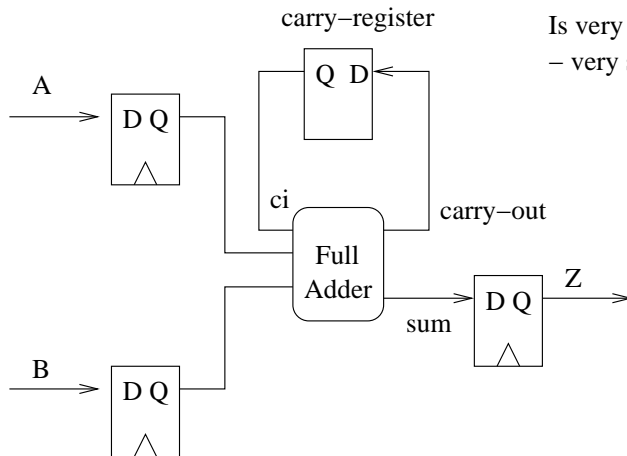


Bit Serial Adder



Is very suitable when the data is coming in/going out serially.
 - very small and can deal with data streams at ~ 1Ghz (0.18um)

Carry-Save Adder (CSA) and Carry Save Trees

Regular Way

- add each column and bring carries over to the next column
- the $C_n + A_n + B_n = \{C_{n+1}, SUM_n\}$

This calculation can also be done if we separately produce the sum and carry bits and add them at the end!


	00110	← carry-bits	
A	10011	19	
+ B	+ 00110	6	
	011001	25	

	10011	19
	+ 00110	6
(A xor B) IntSum	10101	21
Carry	00010	2*2
	011001	25

So far this isn't particularly usefull, but if we look at a 3 input adder:

A	01100	12)	INDEPENDENTLY, for each column produce a sum and carry bit with a normal full-adder
+ B	10011	19		
+ C	00110	6		
Sum bits	11001	25		
Carry bits	00110	6*2		
Final Result	100101	37		Eventually add them up for the final result.

A CSA adder representation

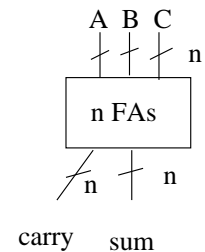

A 3 to 2 reduction of terms!

We can build a tree and get a logarithmic circuit!