

Open book.

In the spirit of the code of honor of Carleton University I solemnly declare this examination is completely my own work, and I did not aid my answer to any question by dishonorable means.


NAME _____ STUDENT No _____

Write answers on the question sheet. Use additional paper if necessary. Attempt all questions.

1 General

a) Find the Σ of Π for the following expression: $F = (A + B)(B + \bar{C})(\bar{A} + D)$. (10%)

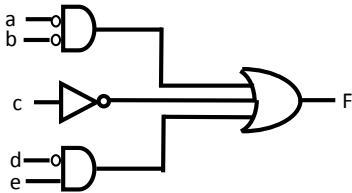
b) Redraw the following circuit using only NAND, and NOR gates and inverters. (10%)



c) Simplify the following expression: $G = \bar{E}A\bar{B}C\bar{D} + \bar{A}B\bar{D}C\bar{F} + \bar{A}B\bar{D}C\bar{F} + \bar{A}BCD + ABCD + ABC\bar{D} + A\bar{B}CD + \bar{A}B\bar{C}D\bar{E}$. Hint: There may be a couple of variables that are “easier” than the rest. (10%)



d) How many flip flops are required to make a finite state machine with 5 states? Is this the maximum number of states that can be made with this number of flip flops? Explain. (5%)

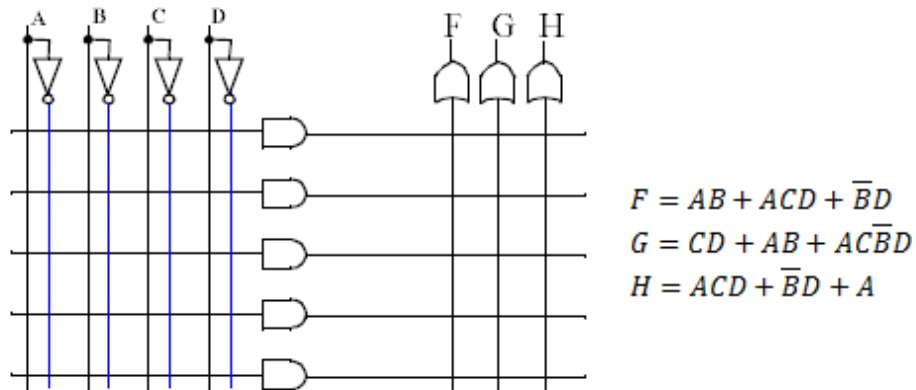e) Implement the following three functions on the PLA given below: (10%)





2 Draw the Waveforms (15%)

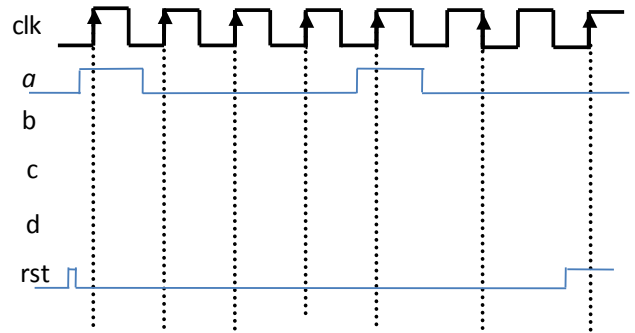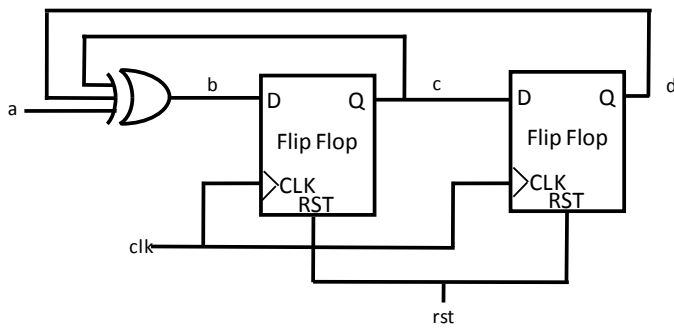Plot all of the waveforms for the circuit below. The input rst is an asynchronous reset signal.



3 Five Variable Maps (20%)

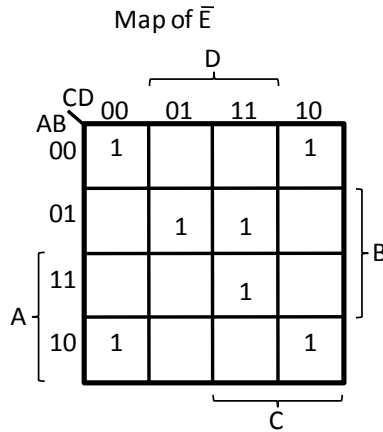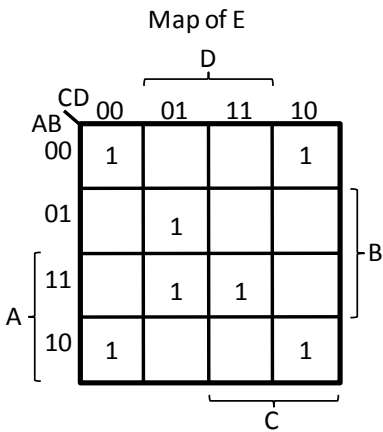Circle the maps below to determine an optimal expression for F.



4 Multi Variable Maps (20%)

Circle the following three maps to provide the lowest gate count possible.

