


# LCR Circuits with Phasors

①

Represent sinusoidal power supply voltage as phasor  $V(t) = V_0 e^{j\omega t}$

$\text{Re}\{V(t)\} = V_0 \cos \omega t$  has physical meaning

## 1. Capacitors

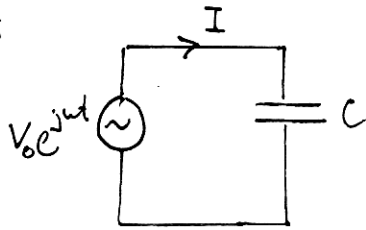


$$I = \frac{dQ}{dt} = C \frac{dV}{dt} = j\omega C V_0 e^{j\omega t}$$

$$\therefore \text{impedance } Z_{\text{cap}} = \frac{V}{I} = \frac{1}{j\omega C} \quad \text{admittance } Y_{\text{cap}} = \frac{1}{Z_{\text{cap}}} = j\omega C$$

NB current and voltage are  $90^\circ$  out of phase in capacitor; I leads V

## 2. Inductors

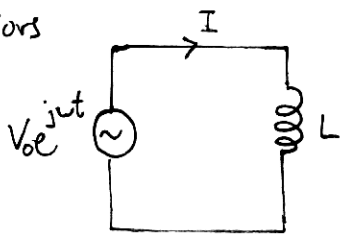


$$V = L \frac{dI}{dt} \rightarrow \text{integrate over } t \text{ to get } I = \frac{V_0}{j\omega L} e^{j\omega t}$$

$$\therefore \text{impedance } Z_{\text{ind}} = \frac{V}{I} = j\omega L \quad \text{admittance } Y_{\text{ind}} = \frac{1}{j\omega L}$$


I lags V by  $90^\circ$

## 3. Impedances add in series:

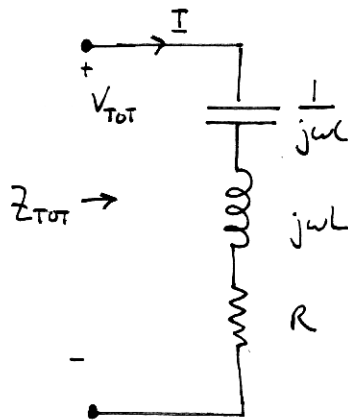

$$Z_{\text{TOT}} = \frac{V_{\text{TOT}}}{I} = \frac{1}{j\omega C} + R + j\omega L$$

4. Admittances add in parallel:

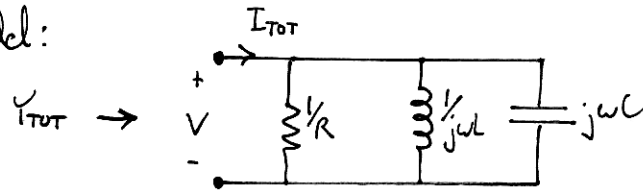

$$Y_{TOT} = \frac{I_{TOT}}{V} = \frac{1}{R} + \frac{1}{j\omega L} + j\omega C$$

5. Resonance: suppose  $\omega L = \frac{1}{\omega C}$  in either the series or par<sup>ll</sup> circuit above;

then the inductive and capacitive terms cancel out and we are left with only the resistance!

This is called a resonance condition

$$\text{NB } \omega L = \frac{1}{\omega C} \Rightarrow \omega = \frac{1}{\sqrt{LC}}$$