

Brief description for incorporating a circuit element into the admittance matrix (Y matrix) of the overall circuit, and related adjoint sensitivity.

Q.J. Zhang

Notations

Suppose the overall circuit has N nodes. Suppose \mathbf{V} is a vector of size N containing node voltages of the circuit. Suppose \mathbf{I} is a vector of size N containing independent current sources of the circuit. Let \mathbf{Y} be a N by N matrix representing the nodal admittance matrix of the entire circuit.

The elements of the \mathbf{V} vector are:

$$\mathbf{V} = [V_1 \ V_2 \ \dots \ V_N]^T$$

Where V_i , $i = 1, 2, \dots, N$, is the nodal voltage at node i .

Circuit Simulation:

Given \mathbf{Y} and \mathbf{I} , the \mathbf{V} vector can be solved by solving the linear equations:

$$\mathbf{Y} \mathbf{V} = \mathbf{I}$$

Adjoint Voltages

Let V_{out} be the output voltage of interests in the circuit. V_{out} can be expressed as

$$V_{\text{out}} = \mathbf{u}^T \mathbf{V}$$

where \mathbf{u} is a constant vector of size N . For example, if V_{out} is the nodal voltage at node 2 of the circuit, \mathbf{u} will be a vector with a value of 1 at the 2nd location and zero everywhere else.

Let $\hat{\mathbf{V}}$ be a vector of size N containing adjoint voltages

$$\hat{\mathbf{V}} = [\hat{V}_1 \ \hat{V}_2 \ \dots \ \hat{V}_N]^T$$

$\hat{\mathbf{V}}$ can be solved by the following linear equations:

$$\mathbf{Y}^T \hat{\mathbf{V}} = \mathbf{u}$$

Example 1: Resistor

Suppose that a resistor is connected between node i and node j .



The contribution of the resistor to the Y matrix of the overall circuit is zero everywhere except 4 locations in the Y matrix:

$$\begin{array}{l} \text{row } i \rightarrow \\ \text{row } j \rightarrow \end{array} \left[\begin{array}{cc} \frac{1}{R} & -\frac{1}{R} \\ -\frac{1}{R} & \frac{1}{R} \end{array} \right]_{N \times N}$$

\uparrow \uparrow
 column i column j

The sensitivity of the V_{out} with respect to parameter R is:

$$\begin{aligned} \frac{\partial V_{out}}{\partial R} &= -(\hat{V}_i - \hat{V}_j) \frac{\partial(\frac{1}{R})}{\partial R} (V_i - V_j) \\ &= -(\hat{V}_i - \hat{V}_j) \left(-\frac{1}{R^2}\right) (V_i - V_j) \end{aligned}$$

Example 2: Capacitor

Suppose that a capacitor is connected between node i and node j .



The contribution of the capacitor to the Y matrix of the overall circuit is zero everywhere except 4 locations in the Y matrix:

$$\begin{array}{l} \text{row } i \rightarrow \\ \text{row } j \rightarrow \end{array} \left[\begin{array}{cc} j\omega C & -j\omega C \\ -j\omega C & j\omega C \end{array} \right]_{N \times N}$$

\uparrow column i \uparrow column j

The sensitivity of the V_{out} with respect to parameter C is:

$$\begin{aligned} \frac{\partial V_{out}}{\partial C} &= -(\hat{V}_i - \hat{V}_j) \frac{\partial(j\omega C)}{\partial C} (V_i - V_j) \\ &= -(\hat{V}_i - \hat{V}_j)(j\omega)(V_i - V_j) \end{aligned}$$

Example 3: A 2-Port Blackbox Element


Suppose that a 2-port blackbox element is represented by its short-circuit admittance matrix representation. Let Y_{port} be such a matrix:

$$\underline{Y}_{port} = \begin{bmatrix} Y_{port 11} & Y_{port 12} \\ Y_{port 21} & Y_{port 22} \end{bmatrix}$$

Where

$$Y_{port 11} = \frac{I_{port 1}}{V_{port 1}} \Big|_{V_{port 2} = 0}$$


$$Y_{port 21} = \frac{I_{port 2}}{V_{port 1}} \Big|_{V_{port 2} = 0}$$

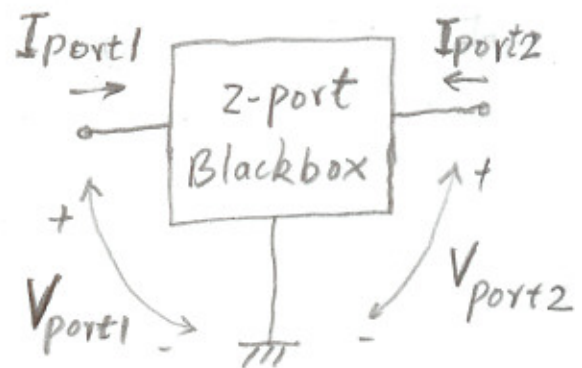

$$Y_{port12} = \frac{I_{port1}}{V_{port2}} \Big|_{V_{port1}=0}$$

$$Y_{port22} = \frac{I_{port2}}{V_{port2}} \Big|_{V_{port1}=0}$$

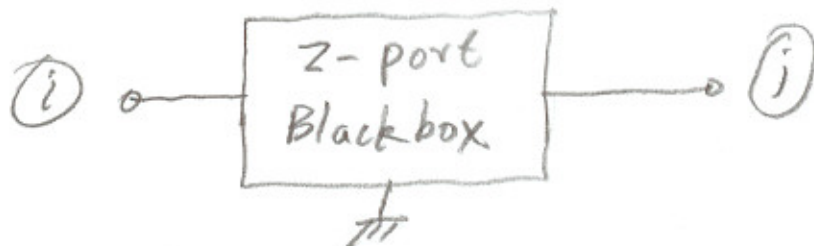Suppose this 2-port element is connected to the overall circuit this way: port 1 of the blackbox is connected to node i of the circuit, and port 2 of the blackbox is connected to node j of the circuit.



The contribution of the 2-port blackbox to the Y matrix of the overall circuit is zero everywhere except 4 locations in the Y matrix of the overall circuit:

$$\begin{array}{l} \text{row } i \rightarrow \\ \text{row } j \rightarrow \end{array} \left[\begin{array}{cc} Y_{port11} & Y_{port12} \\ Y_{port21} & Y_{port22} \end{array} \right]$$

\uparrow column i \uparrow column j

The sensitivity of the V_{out} with respect to any parameter inside the 2-port blackbox is:

$$\frac{\partial V_{out}}{\partial \phi} = - [\hat{V}_i \quad \hat{V}_j] \frac{\partial Y_{port}}{\partial \phi} \begin{bmatrix} V_i \\ V_j \end{bmatrix}$$

where ϕ is a generic variable inside the 2-port blackbox

Example 4: 2-Port Blackbox Originally represented by S-parameters

If the original representation of the 2-port is by other than the admittance (Y-parameter) parameters, we can first convert them into admittance parameter and then follow Example 3 to incorporate the admittance parameters into the overall circuit matrix.

Examples of 2-port parameters: S-parameters, Z-parameters, ABCD matrix. They can all be converted into Y-parameters using standard formulas in textbooks. Attached is a table of such formulas from the book by D.M. Pozar, Microwave Engineering, Addison-Wesley, Reading, MA, 1990, pp 235.

TABLE 5.2 Conversions Between Two-Port Network Parameters

	S	Z	Y	ABCD
S_{11}	S_{11}	$\frac{(Z_{11} - Z_0)(Z_{22} + Z_0) - Z_{12}Z_{21}}{\Delta Z}$	$\frac{(Y_0 - Y_{11})(Y_0 + Y_{22}) + Y_{12}Y_{21}}{\Delta Y}$	$\frac{A + B/Z_0 - CZ_0 - D}{A + B/Z_0 + CZ_0 + D}$
S_{12}	S_{12}	$\frac{2Z_{12}Z_0}{\Delta Z}$	$\frac{-2Y_{12}Y_0}{\Delta Y}$	$\frac{2(AD - BC)}{A + B/Z_0 + CZ_0 + D}$
S_{21}	S_{21}	$\frac{2Z_{21}Z_0}{\Delta Z}$	$\frac{-2Y_{21}Y_0}{\Delta Y}$	$\frac{2}{A + B/Z_0 + CZ_0 + D}$
S_{22}	S_{22}	$\frac{(Z_{11} + Z_0)(Z_{22} - Z_0) - Z_{12}Z_{21}}{\Delta Z}$	$\frac{(Y_0 + Y_{11})(Y_0 - Y_{22}) + Y_{12}Y_{21}}{\Delta Y}$	$\frac{-A + B/Z_0 - CZ_0 + D}{A + B/Z_0 + CZ_0 + D}$
Z_{11}	$Z_0 \frac{(1 + S_{11})(1 - S_{22}) + S_{12}S_{21}}{(1 - S_{11})(1 - S_{22}) - S_{12}S_{21}}$	Z_{11}	$\frac{Y_{22}}{ Y }$	$\frac{A}{C}$
Z_{12}	$Z_0 \frac{2S_{12}}{(1 - S_{11})(1 - S_{22}) - S_{12}S_{21}}$	Z_{12}	$\frac{-Y_{12}}{ Y }$	$\frac{AD - BC}{C}$
Z_{21}	$Z_0 \frac{2S_{21}}{(1 - S_{11})(1 - S_{22}) - S_{12}S_{21}}$	Z_{21}	$\frac{-Y_{21}}{ Y }$	$\frac{1}{C}$
Z_{22}	$Z_0 \frac{(1 - S_{11})(1 + S_{22}) + S_{12}S_{21}}{(1 - S_{11})(1 - S_{22}) - S_{12}S_{21}}$	Z_{22}	$\frac{Y_{11}}{ Y }$	$\frac{D}{C}$
Y_{11}	$Y_0 \frac{(1 - S_{11})(1 + S_{22}) + S_{12}S_{21}}{(1 + S_{11})(1 + S_{22}) - S_{12}S_{21}}$	$\frac{Z_{22}}{ Z }$	Y_{11}	$\frac{D}{B}$
Y_{12}	$Y_0 \frac{-2S_{12}}{(1 + S_{11})(1 + S_{22}) - S_{12}S_{21}}$	$\frac{-Z_{12}}{ Z }$	Y_{12}	$\frac{BC - AD}{B}$
Y_{21}	$Y_0 \frac{-2S_{21}}{(1 + S_{11})(1 + S_{22}) - S_{12}S_{21}}$	$\frac{-Z_{21}}{ Z }$	Y_{21}	$\frac{-1}{B}$
Y_{22}	$Y_0 \frac{(1 + S_{11})(1 - S_{22}) + S_{12}S_{21}}{(1 + S_{11})(1 + S_{22}) - S_{12}S_{21}}$	$\frac{Z_{11}}{ Z }$	Y_{22}	$\frac{A}{B}$
A	$\frac{(1 + S_{11})(1 - S_{22}) + S_{12}S_{21}}{2S_{21}}$	$\frac{Z_{11}}{Z_{21}}$	$\frac{-Y_{22}}{Y_{21}}$	A
B	$Z_0 \frac{(1 + S_{11})(1 + S_{22}) - S_{12}S_{21}}{2S_{21}}$	$\frac{ Z }{Z_{21}}$	$\frac{-1}{Y_{21}}$	B
C	$\frac{1}{Z_0} \frac{(1 - S_{11})(1 - S_{22}) - S_{12}S_{21}}{2S_{21}}$	$\frac{1}{Z_{21}}$	$\frac{- Y }{Y_{21}}$	C
D	$\frac{(1 - S_{11})(1 + S_{22}) - S_{12}S_{21}}{2S_{21}}$	$\frac{Z_{22}}{Z_{21}}$	$\frac{-Y_{11}}{Y_{21}}$	D

$|Z| = Z_{11}Z_{22} - Z_{12}Z_{21}; \quad |Y| = Y_{11}Y_{22} - Y_{12}Y_{21}; \quad \Delta Y = (Y_{11} + Y_0)(Y_{22} + Y_0) - Y_{12}Y_{21}; \quad \Delta Z = (Z_{11} + Z_0)(Z_{22} + Z_0) - Z_{12}Z_{21}; \quad Y_0 = 1/Z_0$

Exercise 1: Implementation

Attached file “UserCKTComponent_1.cpp” is a c++ program implementation of Example 1 (the resistor example). As an exercise, you can use this file as a template to do an implementation of Example 2 (the capacitor example).

The symbols used in the c++ program correspond to our notations according to following table.

Symbols in C++ program	Notation used in Theory	Explanation
MNA_Matrix[][]	\mathbf{Y} matrix	nodal admittance matrix of the overall circuit
MNA_V[]	\mathbf{V} vector	vector of nodal voltages
MNA_VHat[]	$\hat{\mathbf{V}}$ vector	vector of adjoint nodal voltages
omega	ω	angular frequency

Note: the word “MNA” precisely mean “Modified Nodal Admittance”. In all our examples (Examples 1 to 4), there is no “modification” necessary therefore MNA matrix is the nodal admittance matrix.