

Solutions

Chapter 5

5.1 $I_o = 2\text{mA}$

5.3 $I_o = 1.14\text{mA}$

5.7 $I_o = -3.2\text{mA}$

5.9 $V_o = 8\text{V}$

5.11 $V_o = 4.125\text{V}$

5.13 $I_o = 0.4\text{mA}$

5.15 $I_a = -9.75\text{mA}$

5.17 $V_o = 6\text{V}$

5.19 $I_o = 0.909\text{mA}$

5.21 $I_o = 0.27\text{mA}$

5.23 $V_o = 6\text{V}$

5.25 $V_o = 8\text{V}$

5.27 $V_o = 0.21\text{V}$

5.29 $I_o = 2\text{mA}$

5.31 $I_o = 3.5\text{mA}$

5.33 $I_o = 5.2\text{mA}$

5.35 $V_o = 1.375\text{V}$

5.37 $V_o = -8\text{V}$

5.39 $I_o = 1.56\text{mA}$

5.41 $V_{ab} = 20\text{V}$

5.43 $I_o = 1\text{mA}$

5.45 $I_o = 2.57\text{mA}$

5.47 $V_o = 8\text{V}$

- 5.49 $I_o = 0.908 \text{ mA}$
- 5.51 $I_o = 1.55 \text{ mA}$
- 5.77 $V_o = 2 \text{ V}$
- 5.79 $V_o = -3 \text{ V}$
- 5.81 $V_o = -1.05 \text{ V}$
- 5.83 $I_o = 1.5 \text{ mA}$
- 5.85 $I_o = -0.375 \text{ mA}$
- 5.87 $I_o = -1.4 \text{ mA}$
- 5.89 $V_o = 2 \text{ V}$
- 5.91 $I_o = 0.267 \text{ mA}$
- 5.93 $I_o = 1 \text{ mA}$
- 5.95 $I_o = 1.6 \text{ mA}$
- 5.97 $R_l = 2.22 \text{ k}\Omega, P_l = 3.2 \text{ mW}$
- 5.99 $R_l = 1.5 \text{ k}\Omega, P_l = 5.04 \text{ mW}$
- 5.101 $R_l = 2.33 \text{ k}\Omega, P_l = 0.429 \text{ mW}$

Chapter 6

- 6.1 $V = 40 \text{ V}$
- 6.5 $i(t) = \pm 9.23 \cos(377t) \text{ A}$
- 6.7 $v(t) = 0 \text{ V}, t < 0$
 $100t \text{ V}, 0 \leq t \leq t_1$
 $0.2 \text{ V}, t \geq t_1$
- 6.9 $i(t) = 24 \text{ A}, 0 \leq t \leq 6 \mu\text{s}$
 $-60 \text{ A}, 6 \mu\text{s} \leq t \leq 10 \mu\text{s}$
 $16 \text{ A}, 10 \mu\text{s} \leq t \leq 16 \mu\text{s}$
 $0 \text{ A}, t \geq 16 \mu\text{s}$

- 6.11 $i(t) = 0 \text{ A}, \quad t \leq 0$
 $1.2 \text{ A}, \quad 0 \leq t \leq 20 \text{ s}$
 $4.8 \text{ A}, \quad 20 \text{ s} \leq t \leq 30 \text{ s}$
 $1.2 \text{ A}, \quad 30 \text{ s} \leq t \leq 50 \text{ s}$
 $0 \text{ A}, \quad t \geq 50 \text{ s}$
- 6.17 $V_c(0) = 1 \text{ V}, V_c(1 \text{ ms}) = 2.5 \text{ V}, V_c(3 \text{ ms}) = 5.5 \text{ V}, V_c(4 \text{ ms}) = 4.5 \text{ V}, V_c(5 \text{ ms}) = 3.5 \text{ V}$
- 6.19 $W_c(6) = 169 \text{ J}, P_s(6) = 60 \text{ W}$
- 6.21 $V(t) = 75.4 \cos(377t) \text{ V}, W(t) = 0.2 \sin^2(377t) \text{ J}$
- 6.25 $V_l(t) = 0 \text{ V}, \quad t < 0$
 $V_l(t) = 0.1e^{-4t}(1-4t) \text{ V}, \quad t > 0$
- 6.35 (a) 0.9 mJ , (b) $56.25 \mu\text{J}$, (c) 0 V , (d) 17.5 V , (e) -40 V
- 6.37 (a) $9 \text{ mH} \leq L \leq 11 \text{ mH}$, (b) $1.9 \text{ nH} \leq L \leq 2.1 \text{ nH}$, (c) $61.2 \mu\text{H} \leq L \leq 74.8 \mu\text{H}$
- 6.41 $L = 50 \text{ mH}$
- 6.43 $P_r = 21.33 \text{ W}, W_c = 144 \text{ J}$
- 6.45 $C_{\min} = 0.5 \mu\text{F}, C_{\max} = 8 \mu\text{F}$
- 6.49 yes
- 6.51 $C_t = 6 \mu\text{F}$
- 6.53 $C_{\text{eq}} = 10.67 \mu\text{F}$
- 6.55 (a) $10 \mu\text{F}$, (b) $10 \mu\text{F}$
- 6.57 $C = 468 \text{ nF}$
- 6.59 $V_o = 5.33 \text{ V}$
- 6.61 $L_{\text{ab}} = 5 \text{ mH}$
- 6.63 $L_t = 2.4 \text{ mH}$
- 6.67 $L = 3 \text{ mH}$
- 6.69 $L_{\text{eq}} = 32 \text{ mH}, W_{\text{tot}} = 16 \text{ mJ}$

Chapter 8

- 8.7 (a) $i(t)=3.77\cos(377t+60^\circ)$ mA, $I = 3.77\angle 60^\circ$ mA
(b) $i(t)=1.89\cos(377t+60^\circ)$ mA, $I = 1.89\angle 60^\circ$ mA
- 8.9 $Z=2.24\angle 63.43^\circ$ ohms
- 8.11 $Z=1.414\angle 45^\circ$ ohms
- 8.13 $Y=0.5\angle 0^\circ$ S
- 8.15 $Z=6.69 + j5.28$ ohms
- 8.17 $Z=7.11\angle 44.22^\circ$ ohms
- 8.19 $C=1.4$ mF
- 8.21 $L=703.6$ uH
- 8.23 $C=15$ uF
- 8.25 $f=71.2$ Hz
- 8.27 $Z=4.1-j4.92$ ohms
- 8.29 $i(t)=0.6\cos(1000t-53.26^\circ)$ A
- 8.32 $V_o=7.3\cos(10^5t-2.14^\circ)$ V, $V_c=12.16\cos(10^5t-126.87^\circ)$ V
- 8.33 $V_o=12.9\cos(5t+1.85^\circ)$ V
- 8.35 $V(t)=23.49\cos(20t-104.97^\circ)$ V
- 8.43 $V=70.71\angle -45^\circ$ V
- 8.45 $I=6\angle -53.13^\circ$ A
- 8.47 $V=0.894\angle 56.57^\circ$ V
- 8.49 $I=2\angle 125^\circ$ A
- 8.55 $I_1=3\angle -45^\circ$ A
- 8.61 $Z=1.99\angle 83.1^\circ$ ohms
- 8.65 $I_o=2\angle -36.87^\circ$ A
- 8.69 $I_o=1.65\angle -56.5^\circ$ A

8.77 $V_o=6.5\angle 157.5^\circ \text{ V}$

8.85 $V_o=3.58\angle 153.4^\circ \text{ V}$

8.91 $V_o=2.82\angle 8.2^\circ \text{ V}$

8.95 $I_o=3.24\angle -177.31^\circ \text{ A}$

8.101 $V_o=3.6\angle 153.4^\circ \text{ V}$

8.105 $V_o=17.9\angle -26.57^\circ \text{ V}$

8.111 $I_o=3.38\angle 150.8^\circ \text{ V}$