

VARIABLE-FREQUENCY NETWORK PERFORMANCE

Variable-Frequency Response Analysis

Network performance as function of frequency.
Transfer function

Sinusoidal Frequency Analysis

Bode plots to display frequency response data

VARIABLE FREQUENCY-RESPONSE ANALYSIS

In AC steady state analysis the frequency is assumed constant (e.g., 60Hz). Here we consider the frequency as a variable and examine how the performance varies with the frequency.

Variation in impedance of basic components

Resistor

$$Z_R \longrightarrow$$

$$R$$

$$Z_R = R = R\angle 0^\circ$$




(b)




(c)


Inductor

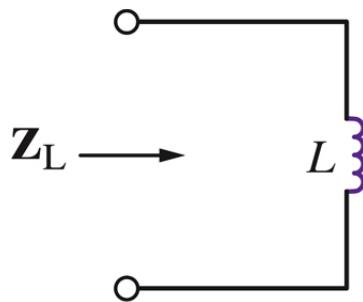
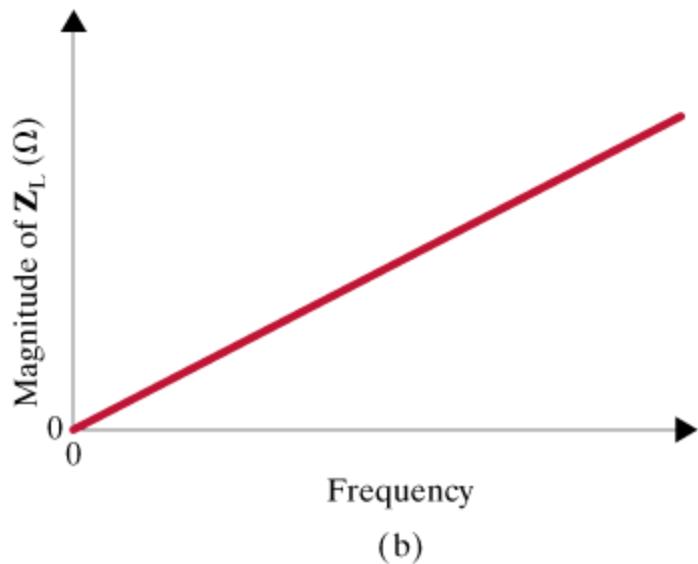
$$\mathbf{Z}_L = j\omega L = \omega L \angle 90^\circ$$




(b)

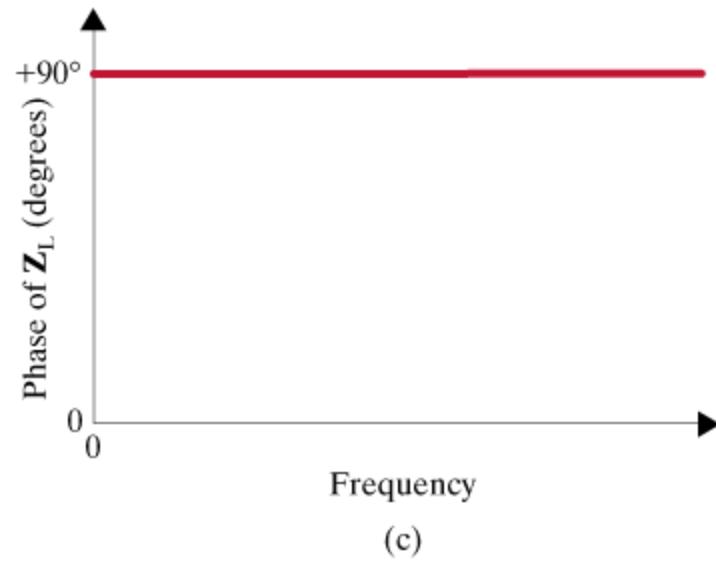


(c)


Capacitor

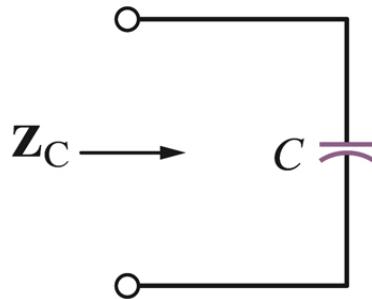
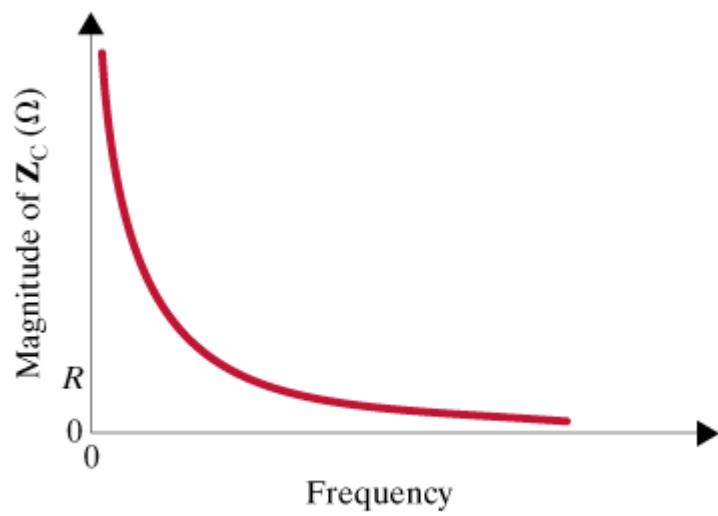
$$Z_c = \frac{1}{j\omega C} = \frac{1}{\omega C} \angle -90^\circ$$




(b)

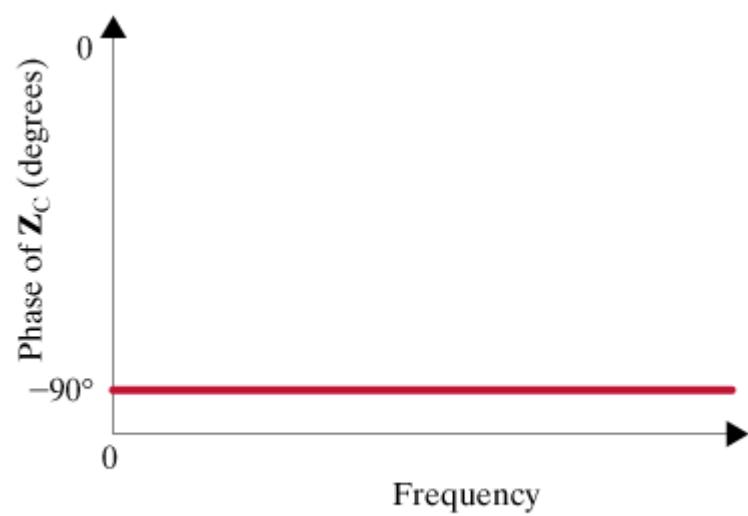

(c)

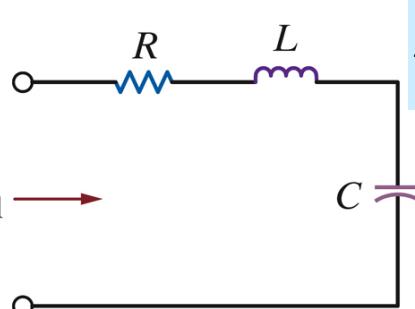Frequency dependent behavior of series RLC network




$$Z_{eq} = R + j\omega L + \frac{1}{j\omega C} = \frac{(j\omega)^2 LC + j\omega RC + 1}{j\omega C} \times \frac{-j}{-j} = \frac{\omega RC + j(\omega^2 LC - 1)}{\omega C}$$

"Simplification in notation" $j\omega \approx s$


$$Z_{eq}(s) = \frac{s^2 LC + sRC + 1}{sC}$$

$$|Z_{eq}| = \frac{\sqrt{(\omega RC)^2 + (\omega^2 LC - 1)^2}}{\omega C}$$
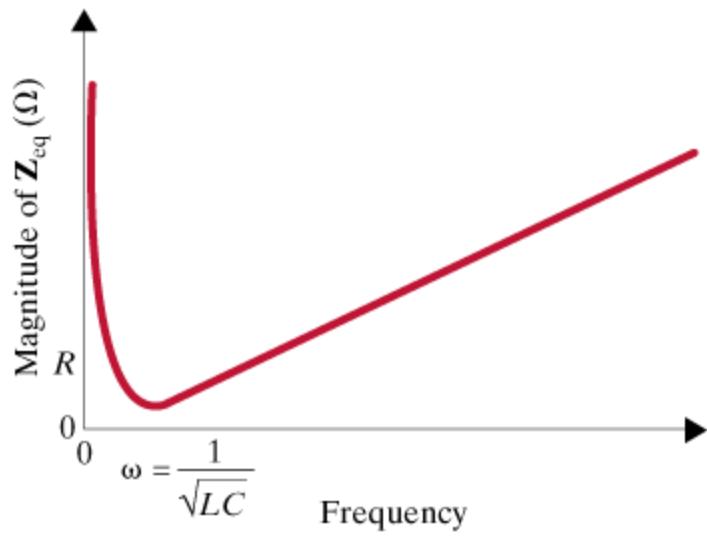
$$\angle Z_{eq} = \tan^{-1} \left(\frac{\omega^2 LC - 1}{\omega RC} \right)$$



(b)

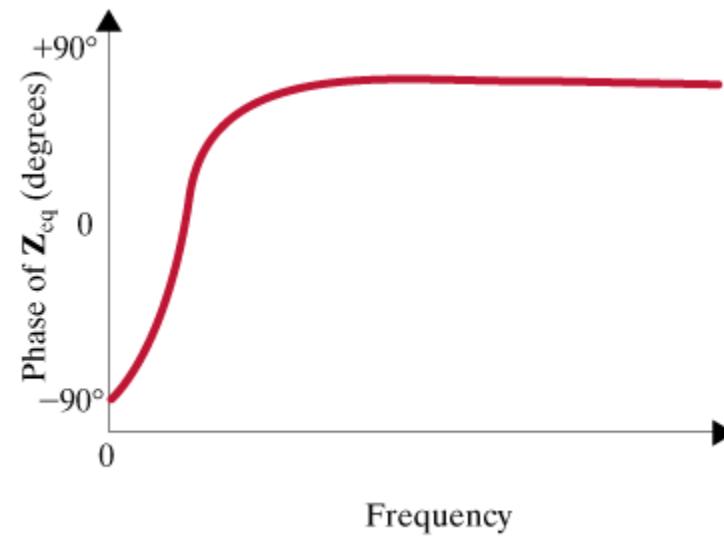

(c)


Simplified notation for basic components

$$Z_R(s) = R, \quad Z_L(s) = sL, \quad Z_C = \frac{1}{sC}$$

For all cases seen, and all cases to be studied, the impedance is of the form

$$Z(s) = \frac{a_m s^m + a_{m-1} s^{m-1} + \dots + a_1 s + a_0}{b_n s^n + b_{n-1} s^{n-1} + \dots + b_1 s + b_0}$$

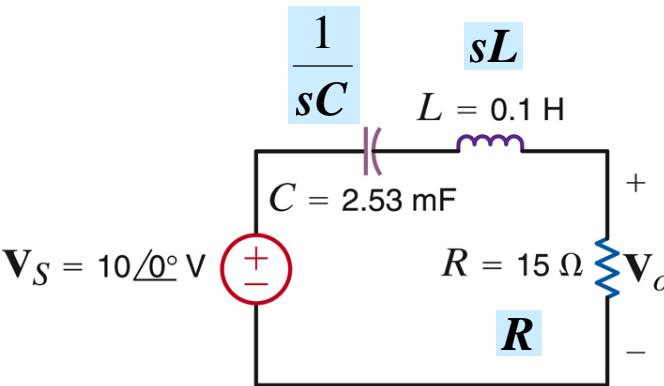Moreover, if the circuit elements (L,R,C, dependent sources) are real then the expression for any voltage or current will also be a rational function in s



$$V_o(s) = \frac{R}{R + sL + 1/sC} V_s = \frac{sRC}{s^2LC + sRC + 1} V_s$$

$$s \approx j\omega$$

$$V_o = \frac{j\omega RC}{(j\omega)^2 LC + j\omega RC + 1} V_s$$


$$V_o = \frac{j\omega(15 \times 2.53 \times 10^{-3})}{(j\omega)^2(0.1 \times 2.53 \times 10^{-3}) + j\omega(15 \times 2.53 \times 10^{-3}) + 1} 10\angle 0^\circ$$

When voltages and currents are defined at different terminal pairs we define the ratios as **Transfer Functions**

| INPUT | OUTPUT | TRANSFER FUNCTION | SYMBOL |
|---------|---------|-------------------|----------|
| Voltage | Voltage | Voltage Gain | $G_v(s)$ |
| Current | Voltage | Transimpedance | $Z(s)$ |
| Current | Current | Current Gain | $G_i(s)$ |
| Voltage | Current | Transadmittance | $Y(s)$ |

If voltage and current are defined at the same terminals we define **Driving Point Impedance/Admittance**

EXAMPLE

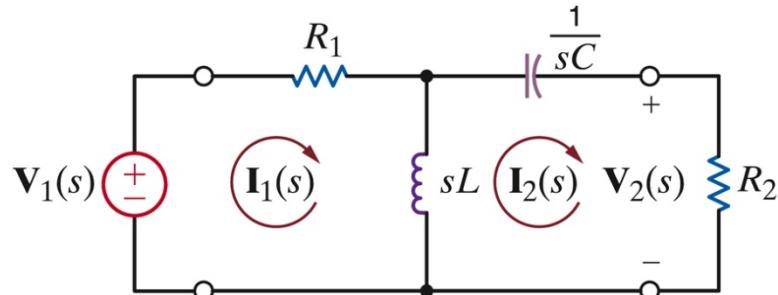


To compute the transfer functions one must solve the circuit. Any valid technique is acceptable

$$Y_T(s) = \frac{I_2(s)}{V_1(s)} \left\{ \begin{array}{l} \text{Transadmittance} \\ \text{Transfer admittance} \end{array} \right.$$

$$G_v(s) = \frac{V_2(s)}{V_1(s)} \quad \text{Voltage gain}$$

EXAMPLE

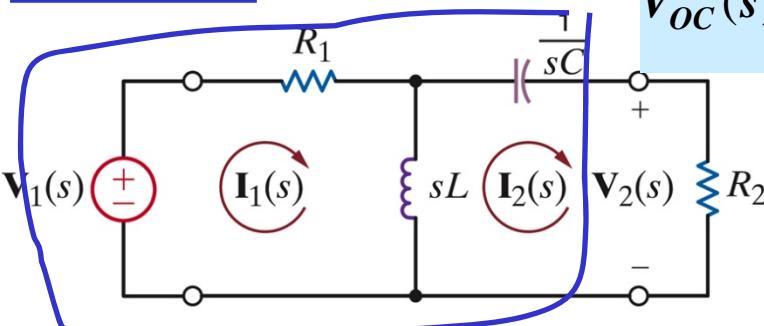

$$V_{OC}(s) = \frac{sL}{sL + R_1} V_1(s)$$


$$Y_T(s) = \frac{I_2(s)}{V_1(s)} \begin{cases} \text{Transadmittance} \\ \text{Transfer admittance} \end{cases}$$

$$G_v(s) = \frac{V_2(s)}{V_1(s)} \quad \text{Voltage gain}$$

We will use Thevenin's theorem

$$Z_{TH}(s) = \frac{1}{sC} + R_1 \parallel sL = \frac{1}{sC} + \frac{sLR_1}{sL + R_1}$$
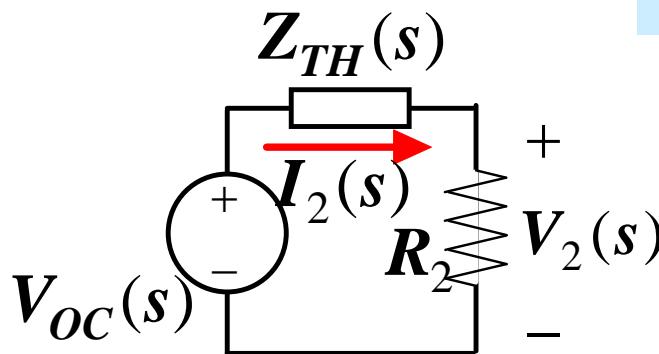
$$Z_{TH}(s) = \frac{s^2 LCR_1 + sL + R_1}{sC(sL + R_1)}$$



$$I_2(s) = \frac{V_{OC}(s)}{R_2 + Z_{TH}(s)} = \frac{\frac{sL}{sL + R_1} V_1(s)}{R_2 + \frac{s^2 LCR_1 + sL + R_1}{sC(sL + R_1)}} \times \frac{sC(sL + R_1)}{sC(sL + R_1)}$$

$$Y_T(s) = \frac{s^2 LC}{s^2(R_1 + R_2)LC + s(L + R_1R_2C) + R_1}$$

$$G_v(s) = \frac{V_2(s)}{V_1(s)} = \frac{R_2 I_2(s)}{V_1(s)} = R_2 Y_T(s)$$

$$H(s) = \frac{a_m s^m + a_{m-1} s^{m-1} + \dots + a_1 s + a_0}{b_n s^n + b_{n-1} s^{n-1} + \dots + b_1 s + b_0}$$

Arbitrary network function

Using the roots, every (monic) polynomial can be expressed as a product of first order terms

$$H(s) = K_0 \frac{(s - z_1)(s - z_2)\dots(s - z_m)}{(s - p_1)(s - p_2)\dots(s - p_n)}$$

z_1, z_2, \dots, z_m = zeros of the network function

p_1, p_2, \dots, p_n = poles of the network function

The network function is uniquely determined by its poles and zeros and its value at some other value of s (to compute the gain)

EXAMPLE

zeros : $z_1 = -1$,


poles : $p_1 = -2 + j2, p_2 = -2 - j2$

$H(0) = 1$

$$H(s) = K_0 \frac{(s + 1)}{(s + 2 - j2)(s + 2 + j2)} = K_0 \frac{s + 1}{s^2 + 4s + 8}$$

$$H(0) = K_0 \frac{1}{8} = 1 \Rightarrow H(s) = 8 \frac{s + 1}{s^2 + 4s + 8}$$

SINUSOIDAL FREQUENCY ANALYSIS

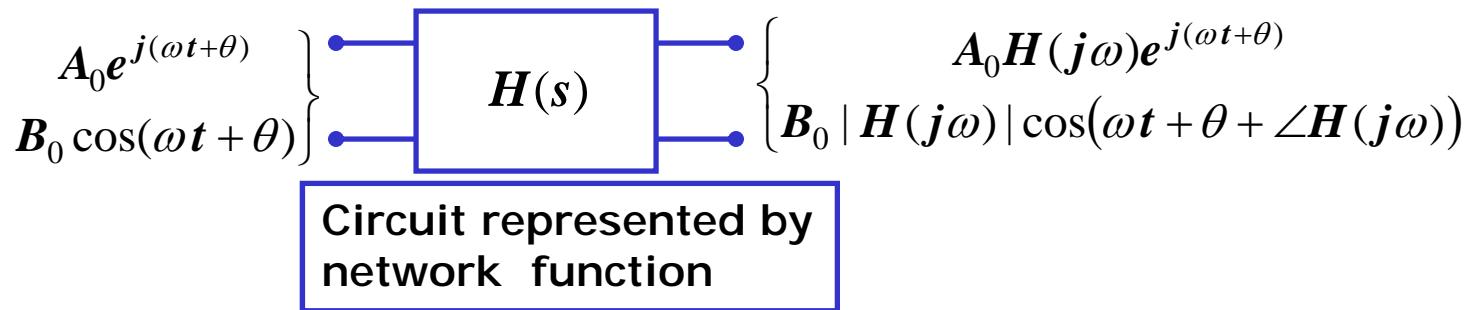

To study the behavior of a network as a function of the frequency we analyze the network function $H(j\omega)$ as a function of ω .

Notation

$$M(\omega) = |H(j\omega)|$$

$$\phi(\omega) = \angle H(j\omega)$$

$$H(j\omega) = M(\omega) e^{j\phi(\omega)}$$

Plots of $M(\omega), \phi(\omega)$, as function of ω are generally called magnitude and phase characteristics.

BODE PLOTS $\begin{cases} 20 \log_{10}(M(\omega)) \\ \phi(\omega) \end{cases}$ vs $\log_{10}(\omega)$

HISTORY OF THE DECIBEL

Originated as a measure of relative (radio) power

$$P_2 |_{dB} \text{ (over } P_1) = 10 \log \frac{P_2}{P_1}$$

$$P = I^2 R = \frac{V^2}{R} \Rightarrow P_2 |_{dB} \text{ (over } P_1) = 10 \log \frac{V_2^2}{V_1^2} = 10 \log \frac{I_2^2}{I_1^2}$$

$$V |_{dB} = 20 \log_{10} |V|$$

$$I |_{dB} = 20 \log_{10} |I|$$

$$G |_{dB} = 20 \log_{10} |G|$$

By extension

Using log scales the frequency characteristics of network functions have simple asymptotic behavior.

The asymptotes can be used as reasonable and efficient approximations

General form of a network function showing basic terms

Frequency independent

$$H(j\omega) = \frac{K_0(j\omega)^{\pm N}}{(1+j\omega\tau_a)[1+2\zeta_b(j\omega\tau_b)+(j\omega\tau_b)^2]\dots} [1+2\zeta_3(j\omega\tau_3)+(j\omega\tau_3)^2]\dots$$

Poles/zeros at the origin

$$\log(AB) = \log A + \log B$$

First order terms

$$\log\left(\frac{N}{D}\right) = \log N - \log D$$

Quadratic terms for complex conjugate poles/zeros

$$|\mathbf{H}(j\omega)|_{dB} = 20\log_{10} |\mathbf{H}(j\omega)| = 20\log_{10} K_0 \pm N 20\log_{10} |j\omega|$$

$$+ 20\log_{10} |1+j\omega\tau_1| + 20\log_{10} |1+2\zeta_3(j\omega\tau_3)+(j\omega\tau_3)^2| + \dots$$

$$- 20\log_{10} |1+j\omega\tau_a| - 20\log_{10} |1+2\zeta_b(j\omega\tau_b)+(j\omega\tau_b)^2| - \dots$$

$$\angle z_1 z_2 = \angle z_1 + \angle z_2$$

$$\angle \frac{z_1}{z_2} = \angle z_1 - \angle z_2$$

$$\angle \mathbf{H}(j\omega) = 0 \pm N 90^\circ$$


$$+ \tan^{-1} \omega\tau_1 + \tan^{-1} \frac{2\zeta_3\omega\tau_3}{1-(\omega\tau_3)^2} + \dots$$

$$- \tan^{-1} \omega\tau_a - \tan^{-1} \frac{2\zeta_b\omega\tau_b}{1-(\omega\tau_b)^2} - \dots$$

Display each basic term separately and add the results to obtain final answer

Let's examine each basic term



Constant Term

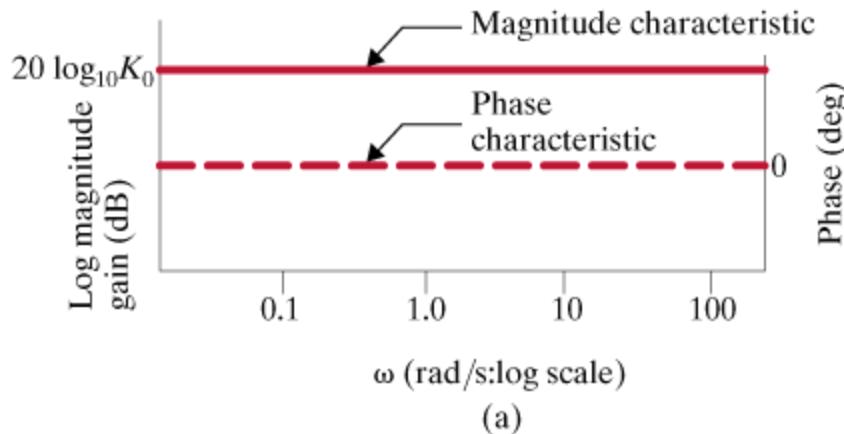

the x - axis is $\log_{10}\omega$
this is a straight line

Poles/Zeros at the origin

$$(j\omega)^{\pm N} \rightarrow \begin{cases} |(j\omega)^{\pm N}|_{dB} = \pm N \times 20 \log_{10}(\omega) \\ \angle(j\omega)^{\pm N} = \pm N 90^\circ \end{cases}$$

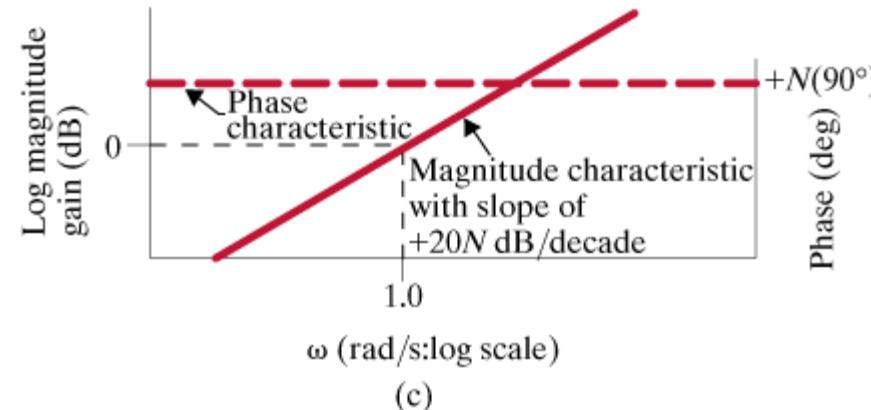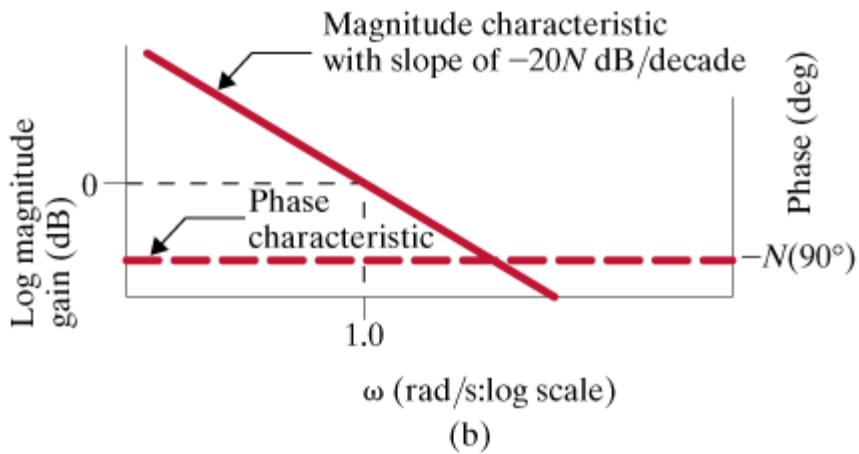

Simple pole or zero $1 + j\omega\tau$

$$\begin{cases} |1 + j\omega\tau|_{dB} = 20 \log_{10} \sqrt{1 + (\omega\tau)^2} \\ \angle(1 + j\omega\tau) = \tan^{-1} \omega\tau \end{cases}$$

$\omega\tau \ll 1 \Rightarrow |1 + j\omega\tau|_{dB} \approx 0$ low frequency asymptote

$$\angle(1 + j\omega\tau) \approx 0^\circ$$


$\omega\tau \gg 1 \Rightarrow |1 + j\omega\tau|_{dB} \approx 20 \log_{10} \omega\tau$ high frequency asymptote (20dB/dec)



$$\angle(1 + j\omega\tau) \approx 90^\circ$$

The two asymptotes meet when $\omega\tau = 1$ (corner/break frequency)

Behavior in the neighborhood of the corner

| | Frequency Asymptote | Curve asymptote | distance to asymptote | Argument |
|--------------|---------------------|-----------------|-----------------------|----------|
| corner | $\omega\tau = 1$ | 0dB | 3dB | 3 |
| octave above | $\omega\tau = 2$ | 6dB | 7dB | 1 |
| octave below | $\omega\tau = 0.5$ | 0dB | 1dB | 1 |

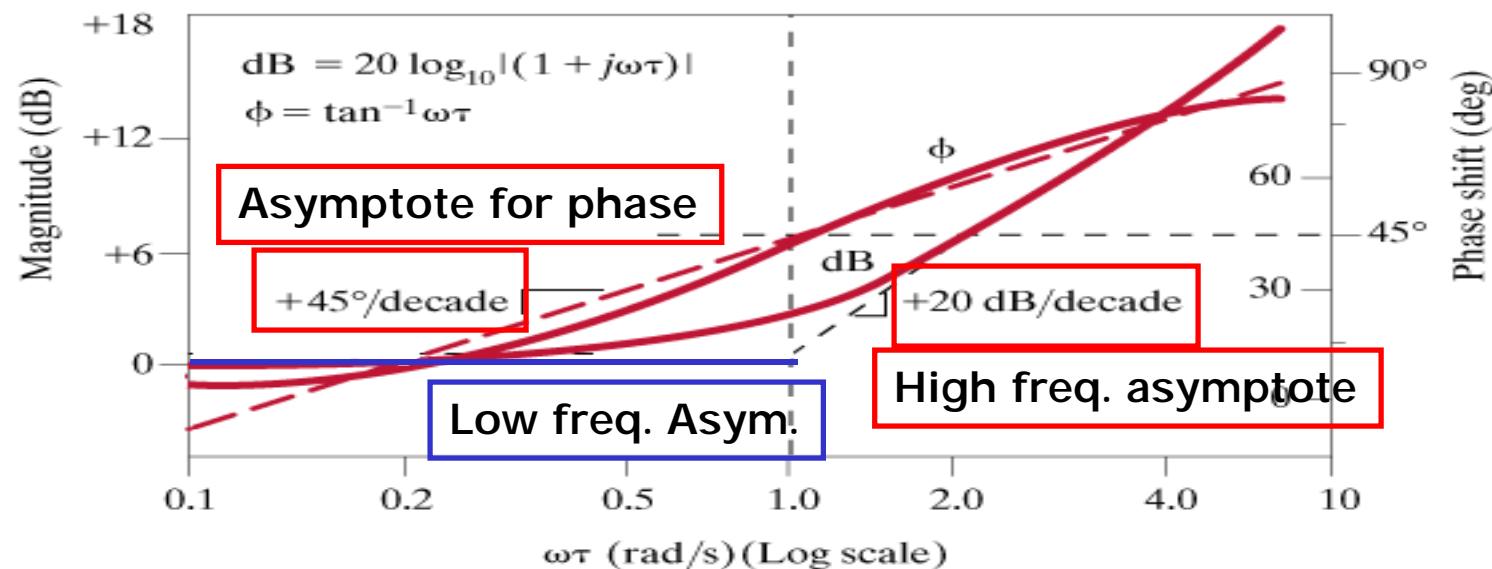

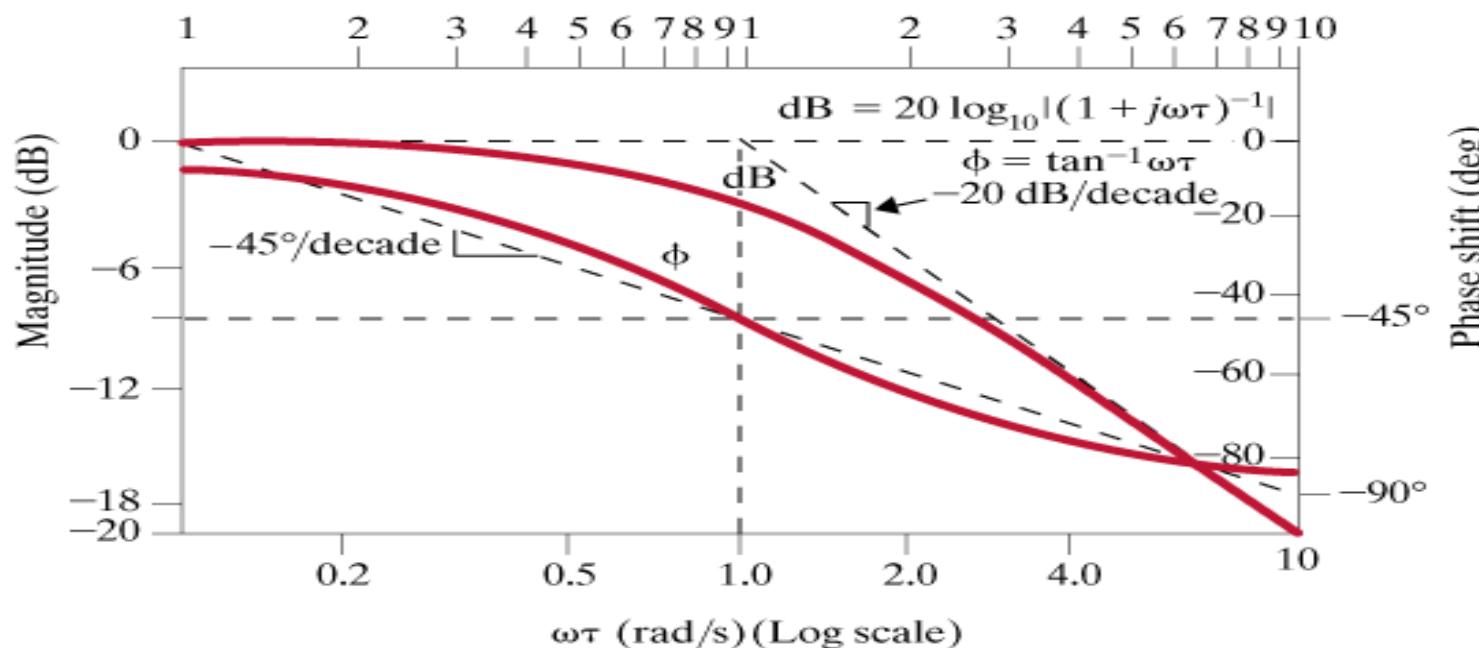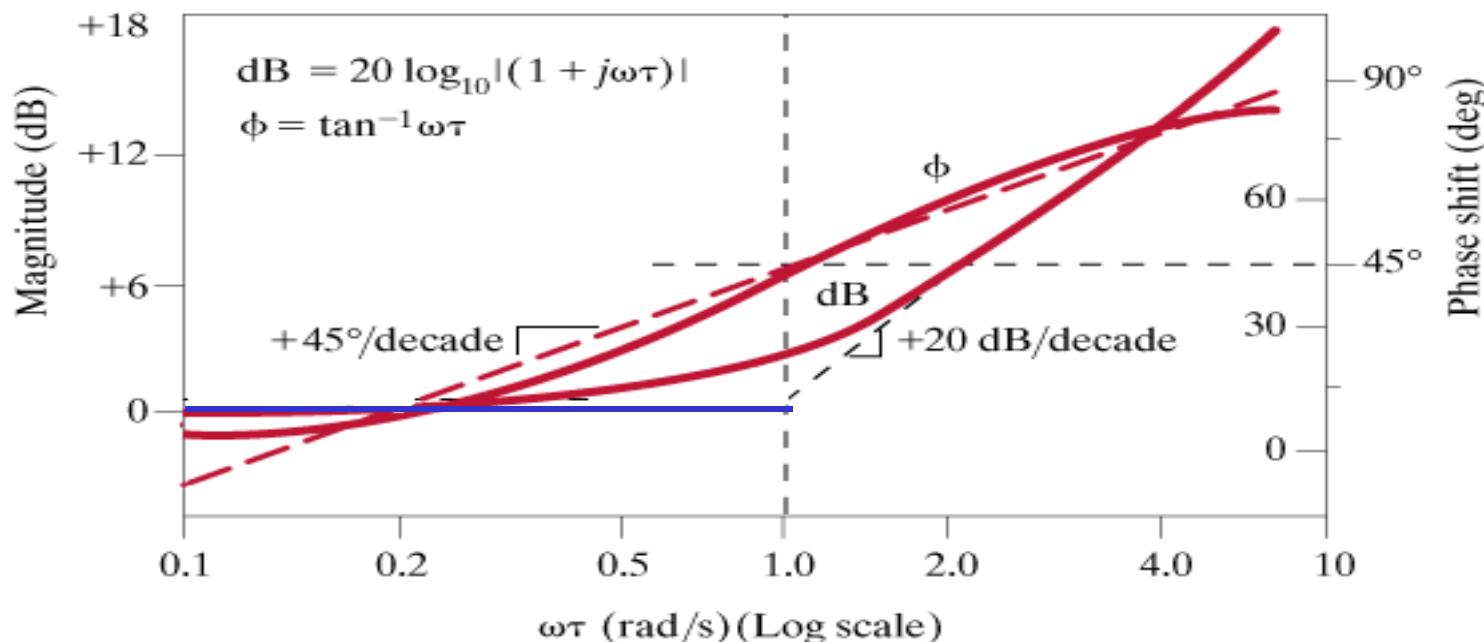

(a)

LEARNING EXAMPLE


Draw asymptotes
for each term


Draw composites

Generate magnitude and phase plots

$$G_v(j\omega) = \frac{10|0.1j\omega+1|}{(j\omega+1)(0.02j\omega+1)}$$

Breaks/corners : 1,10,50

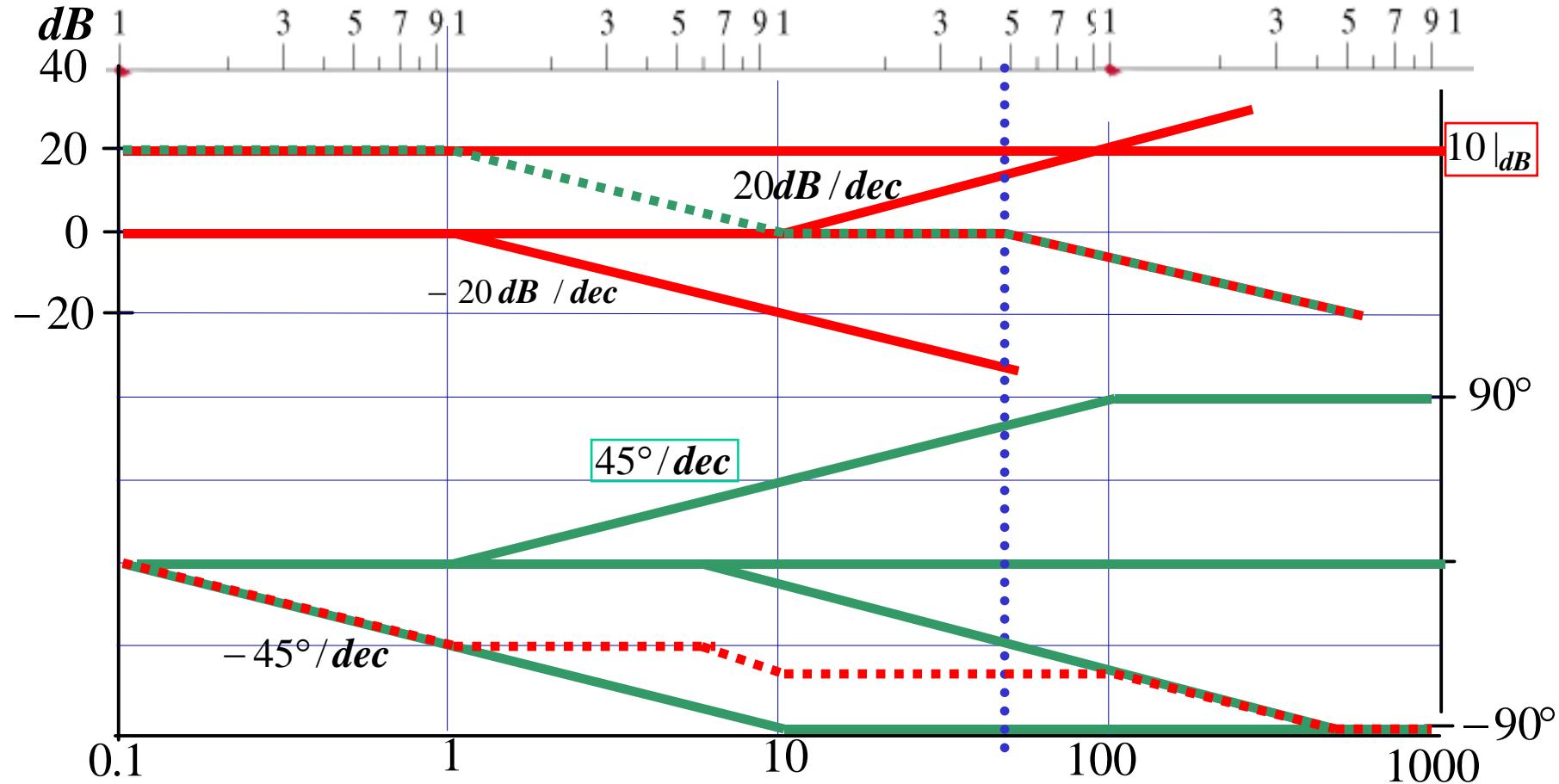


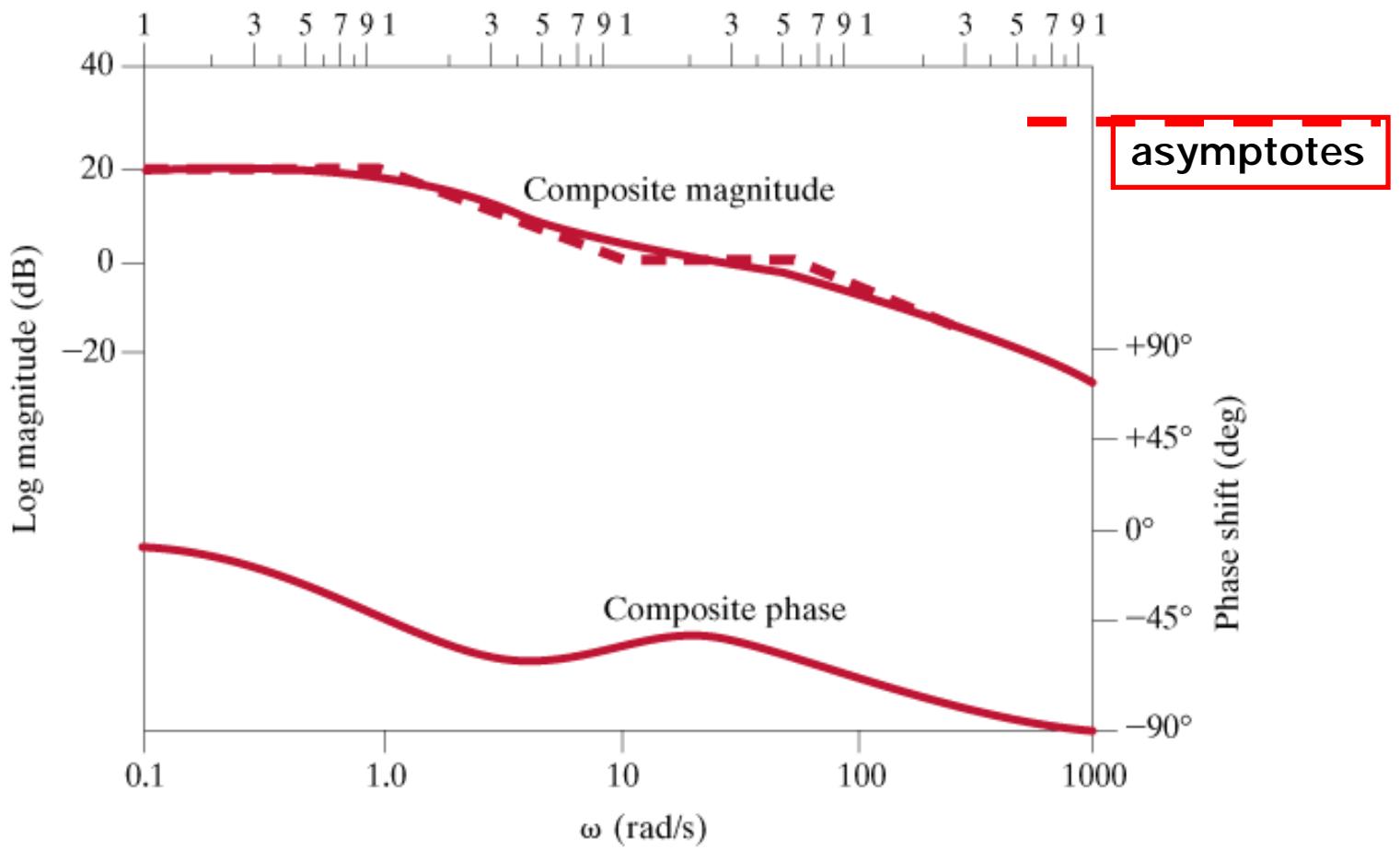

(b)

DETERMINING THE TRANSFER FUNCTION FROM THE BODE PLOT

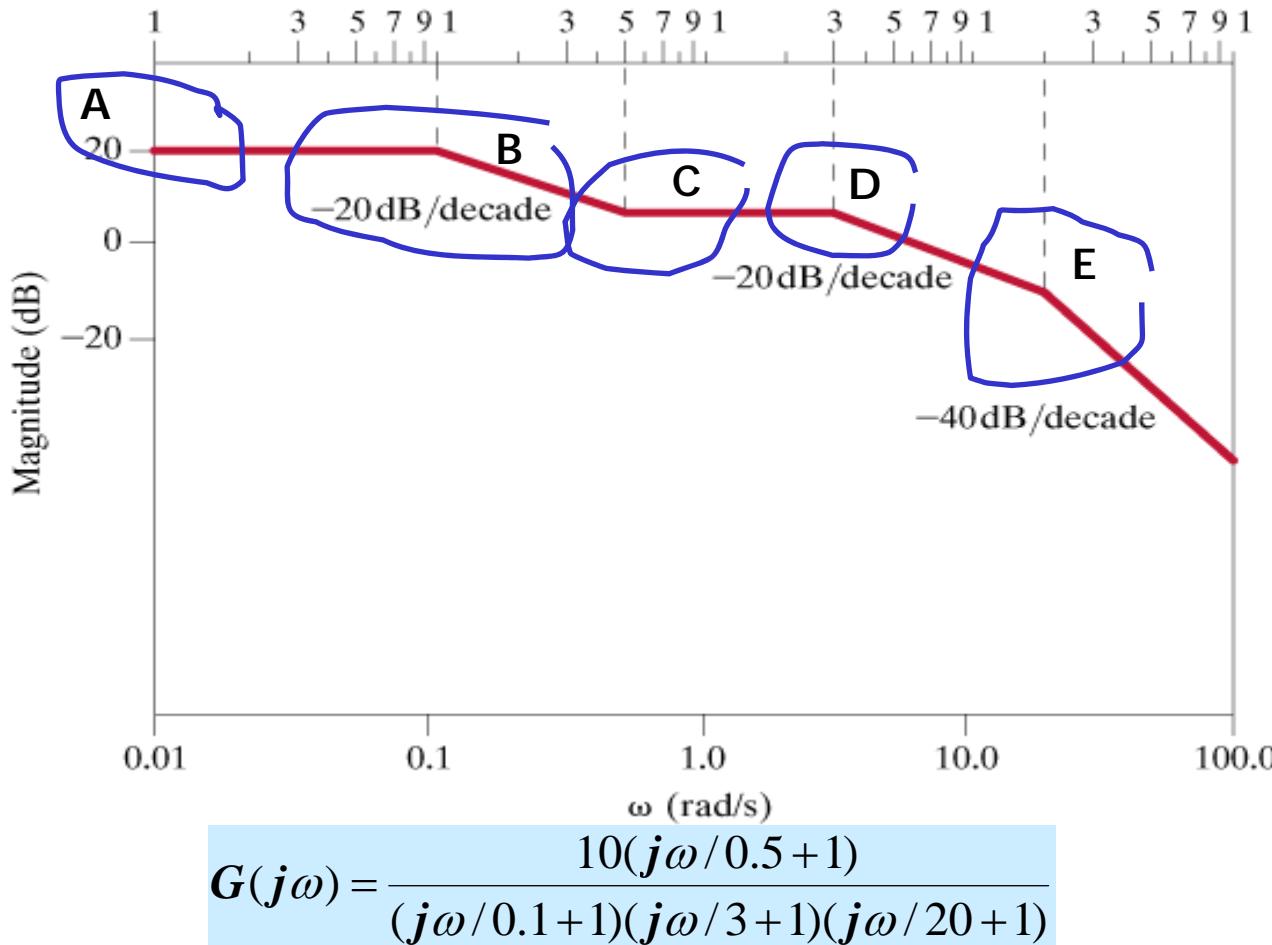This is the inverse problem of determining frequency characteristics. We will use only the composite asymptotes plot of the magnitude to postulate a transfer function. The slopes will provide information on the order



A. different from 0dB.
There is a constant K_0

$$K_0|_{dB} = 20 \Rightarrow K_0 = 10^{\frac{|K_0|_{dB}}{20}}$$

B. Simple pole at 0.1

$$(j\omega/0.1+1)^{-1}$$

C. Simple zero at 0.5

$$(j\omega/0.5+1)$$

D. Simple pole at 3

$$(j\omega/3+1)^{-1}$$

E. Simple pole at 20

$$(j\omega/20+1)^{-1}$$

If the slope is -40dB we assume double real pole. Unless we are given more data