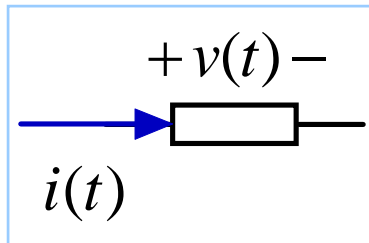


RESISTIVE CIRCUITS

- OHM'S LAW - DEFINES THE SIMPLEST PASSIVE ELEMENT: THE RESISTOR

RESISTORS



A resistor is a passive element characterized by an algebraic relation between the voltage across its terminals and the current through it

$v(t) = F(i(t))$ General Model for a Resistor

A linear resistor obeys OHM's Law

$$v(t) = Ri(t)$$

The constant, R , is called the resistance of the component and is measured in units of Ohm (Ω)

From a dimensional point of view Ohms is a derived unit of Volt/Amp

Since the equation is algebraic the time dependence can be omitted

Standard Multiples of Ohm

$M\Omega$ Mega Ohm ($10^6 \Omega$)

$k\Omega$ Kilo Ohm ($10^3 \Omega$)

A common occurrence is $\frac{\text{Volt}}{\text{mA}}$ resulting in resistance in $k\Omega$

Conductance

If instead of expressing voltage as a function of current one expresses current in terms of voltage, OHM's Law can be written


$$i = \frac{1}{R}v$$

We define $G = \frac{1}{R}$ as Conductance of the component and write


$$i = Gv$$

The unit of conductance is Siemens

Some practical resistors

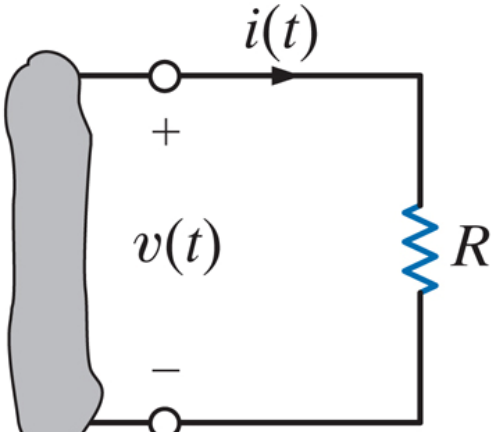


Symbol

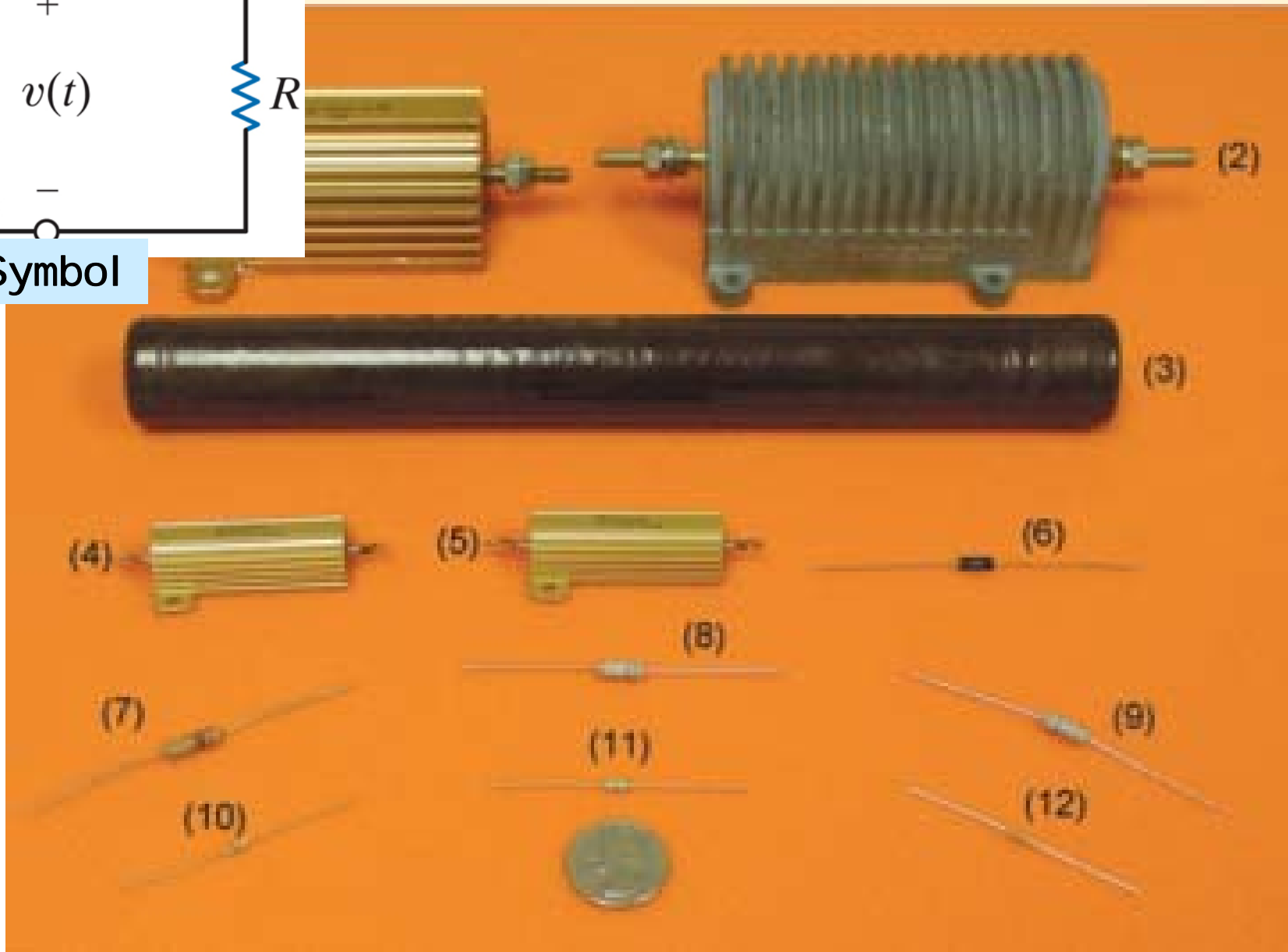


Two special resistor values


Notice passive sign convention

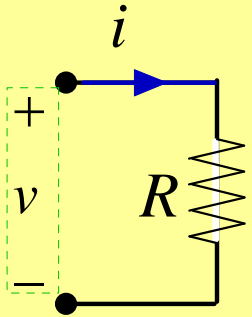


Circuit Representation

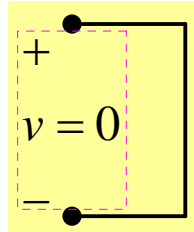

Short Circuit
 $R = 0$
 $G = \infty$

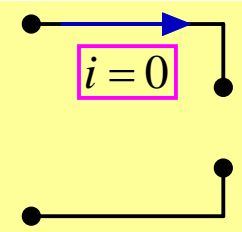

Open Circuit
 $R = \infty$
 $G = 0$

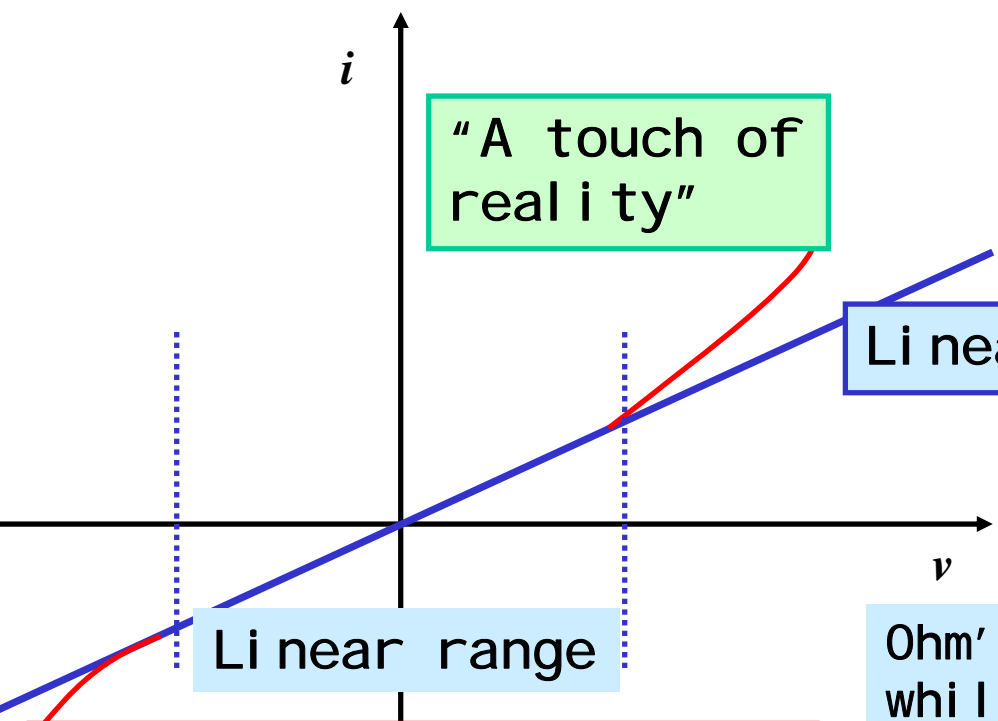

Linear approximation

Linear range

Actual v-I relationship


Ohm's Law is an approximation valid while voltages and currents remain in the Linear Range

OHM'S LAW PROBLEM SOLVING TIP

$v = Ri$ $i = Gv$ OHM's Law


One equation and three variables.
Given ANY two the third can be found

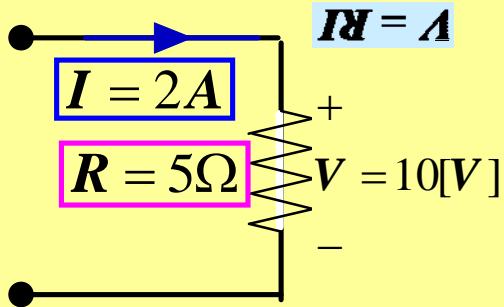Given current and resistance
Find the voltage




Notice use of passive sign convention

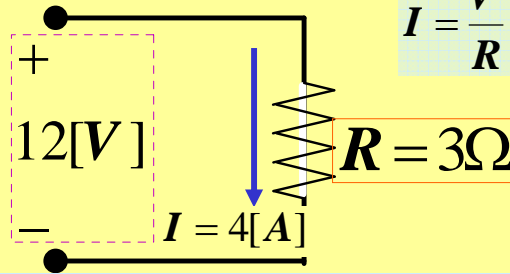Given Voltage and Resistance
Compute Current



Determine direction of the current using passive sign convention

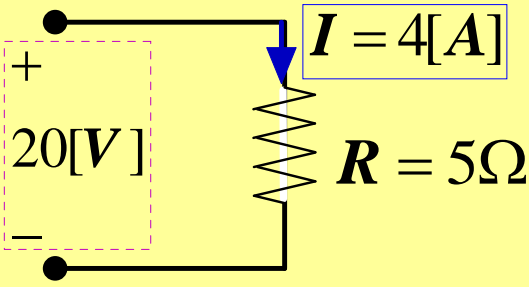Given Current and Voltage
Find Resistance




$$R = \frac{V}{I}$$

Table 1 Keeping Units Straight

Voltage	Current	Resistance
Volts	Amps	Ohms
Volts	mA	kΩ
mV	A	mΩ
mV	mA	Ω

Determine $i(t)$

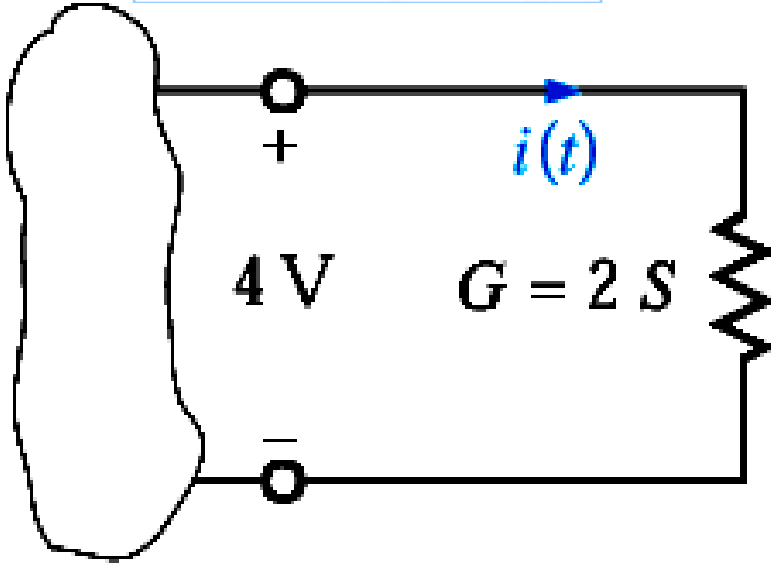

GIVEN VOLTAGE AND CONDUCTANCE
 REFERENCE DIRECTIONS SATISFY
 PASSIVE SIGN CONVENTION


$$i(t) = Gv(t) \quad \text{OHM'S LAW}$$

UNITS?

CONDUCTANCE IN SIEMENS, VOLTAGE
 IN VOLTS. HENCE CURRENT IN AMPERES


$$i(t) = 8[A]$$

Determine $i(t)$

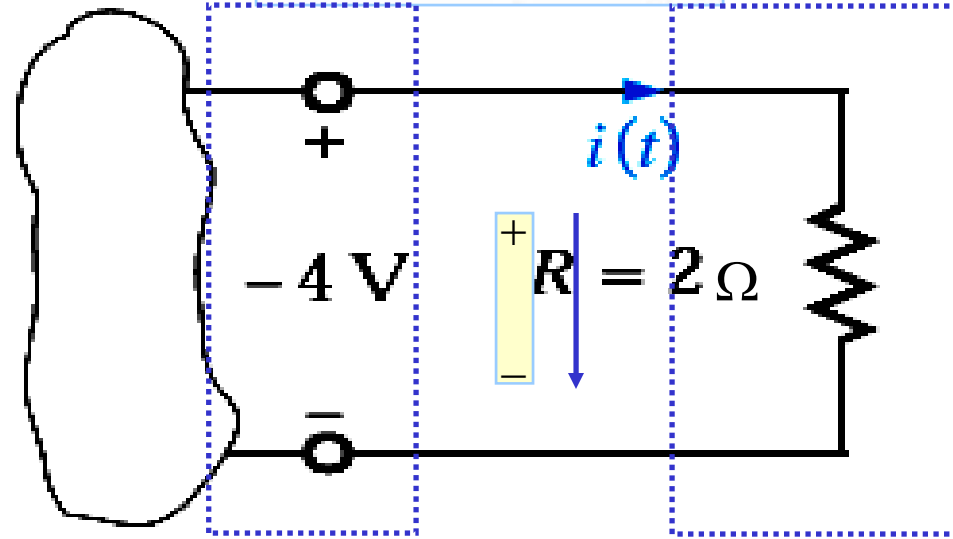

OHM'S LAW $v(t) = Ri(t)$ UNITS?
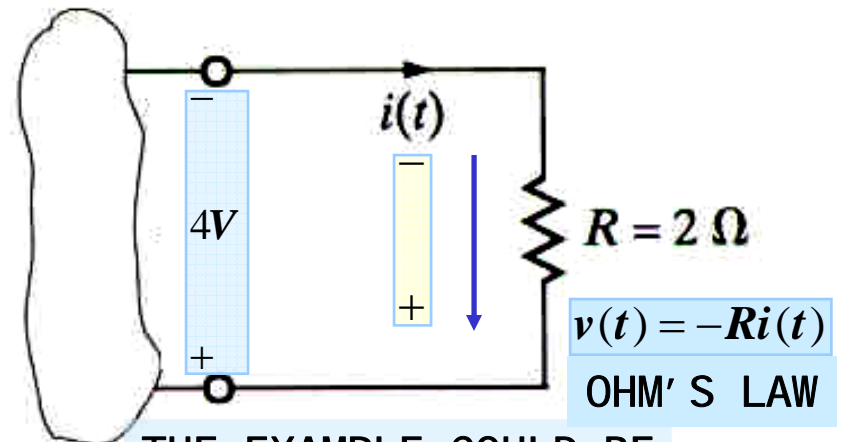
$$-4[V] = (2\Omega)i(t) \Rightarrow i(t) = -2[A]$$



$$v(t) = -Ri(t)$$

OHM'S LAW

THE EXAMPLE COULD BE
 GIVEN LIKE THIS

RESISTORS AND ELECTRIC POWER

Resistors are passive components that can only absorb energy. Combining Ohm's Law and the expressions for power we can derive several useful expressions

$$P = vi \quad (\text{Power})$$

$$v = Ri, \text{ or } i = Gv \quad (\text{Ohm's Law})$$

Problem solving tip: There are four variables (P, v, i, R) and two equations. Given any two variables one can find the other two.

Given P, i

$$v = \frac{P}{i}, R = \frac{v}{i}$$

Given v, R

$$i = \frac{v}{R}, P = vi = \frac{v^2}{R}$$

Given i, R

$$v = Ri, P = vi = Ri^2$$

Given P, R

$$i = \sqrt{\frac{P}{R}}, v = Ri = \sqrt{PR}$$

If not given, the reference direction for voltage or current can be chosen and the other is given by the passive sign convention

A MATTER OF UNITS

Working with SI units Volt, Ampere, Watt, Ohm, there is never a problem. One must be careful when using multiples or sub multiples.


EXAMPLE: $R = 40 \text{ k}\Omega, i = 2 \text{ mA}$

The basic strategy is to express all given variables in SI units

$$v = (40 * 10^3 \Omega) * (2 * 10^{-3} \text{ A}) = 80 [\text{V}]$$

$$P = Ri^2 = (40 * 10^3 \Omega) * (2 * 10^{-3} \text{ A})^2 = 160 * 10^{-3} [\text{W}]$$

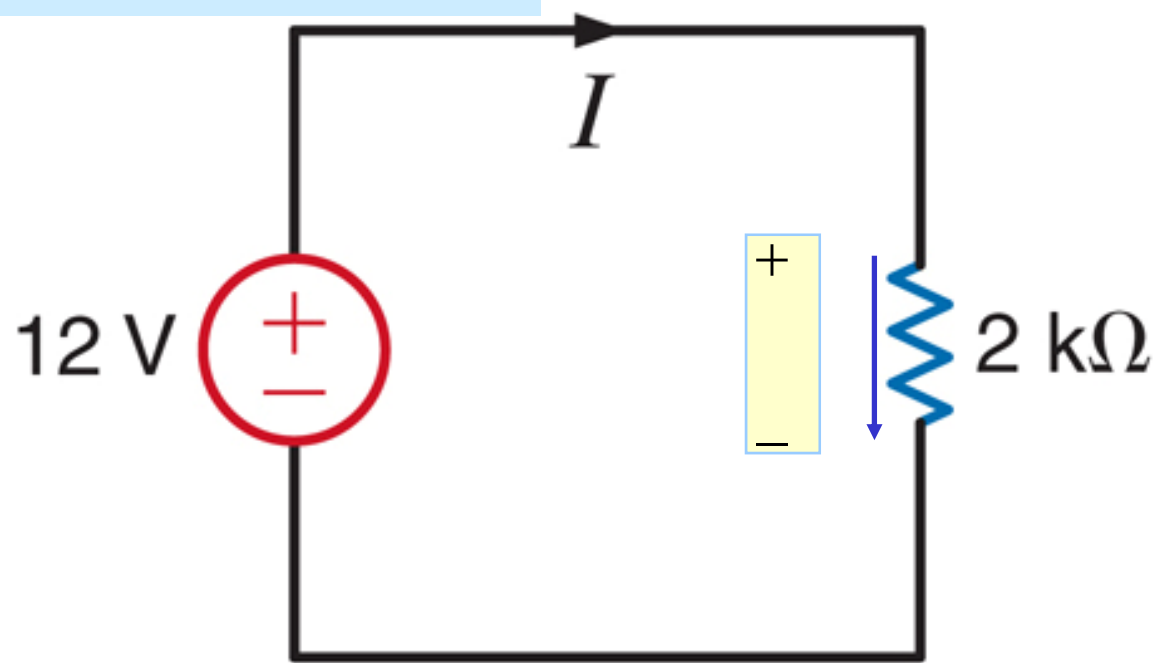
DETERMINE CURRENT AND POWER ABSORBED BY RESISTOR



$$I = V/R = 12/2k = 6mA$$

$$P = VI = I^2R = \frac{V^2}{R}$$


$$P = (12[V])(6[mA]) = 72[mW]$$

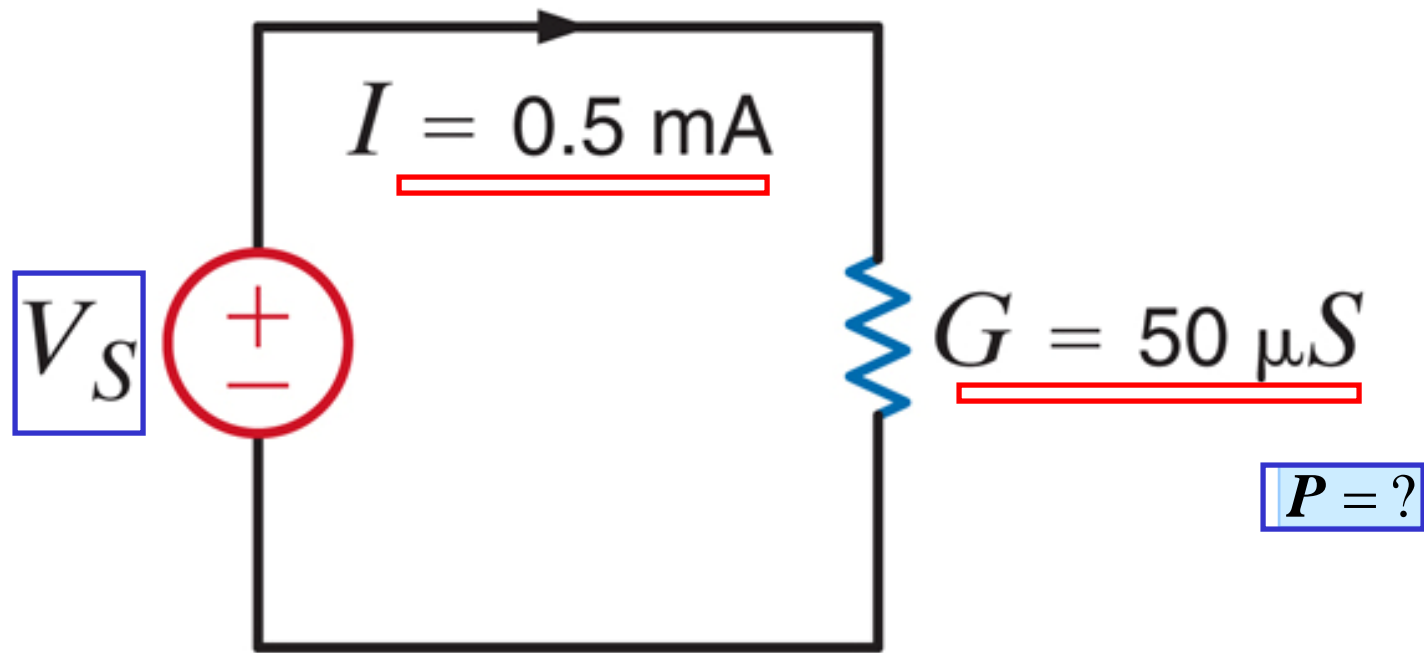

$$V_S = IR \Rightarrow V_S = \frac{I}{G} \quad V_S = \frac{0.5 \times 10^{-3} [\text{A}]}{50 \times 10^{-6} [\text{S}]} = 10 [\text{V}]$$

$$P = I^2 R = \frac{I^2}{G} \quad P = \frac{(0.5 \times 10^{-3} [\text{A}])^2}{50 \times 10^{-6} [\text{S}]} = 0.5 \times 10^{-2} [\text{W}]$$

$5 [\text{mW}]$

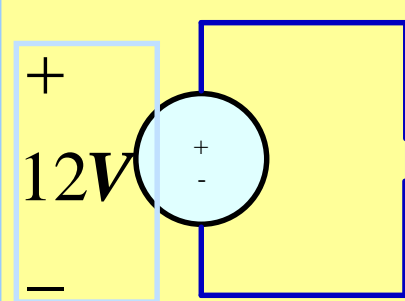

$$P = 60W$$

HALOGEN
LAMP

Resistance of Lamp $R = V/I = 2.4 \text{ Ohms}$

Current through Lamp $I = P/V = 5A$

$$q = \int \text{current}$$

Charge supplied by
battery in 1min

$$Q = 5 * 60 [C]$$

SAMPLE PROBLEM

Recognizing the type of problem:

This is an application of Ohm's Law

We are given Power and Voltage.

We are asked for Resistance, Current
and Charge

Possibly useful relationships

$$P = VI = \frac{V^2}{R} = I^2R$$

$$V = IR$$