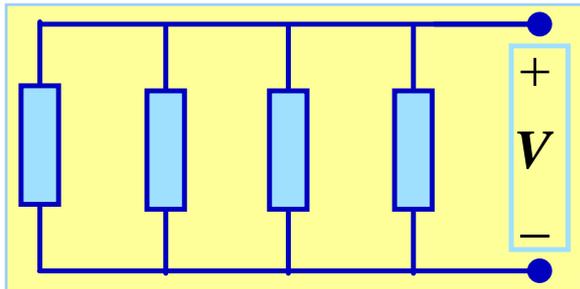


RESISTIVE CIRCUITS


- SINGLE NODE-PAIR CIRCUIT ANALYSIS

SINGLE NODE-PAIR CIRCUITS

THESE CIRCUITS ARE CHARACTERIZED BY ALL THE ELEMENTS HAVING THE SAME VOLTAGE ACROSS THEM - THEY ARE IN PARALLEL




EXAMPLE OF SINGLE NODE-PAIR

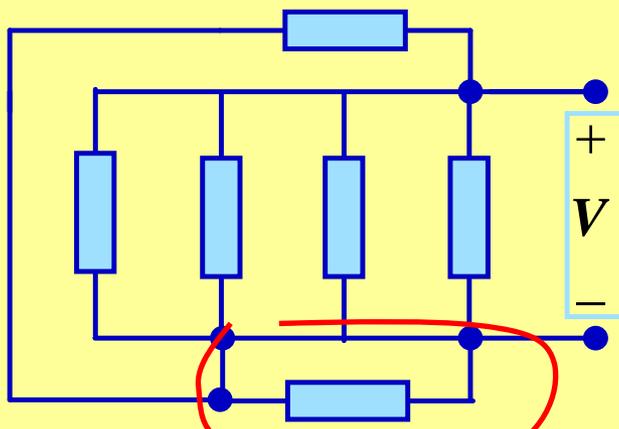

THIS ELEMENT IS INACTIVE (SHORT-CIRCUITED)

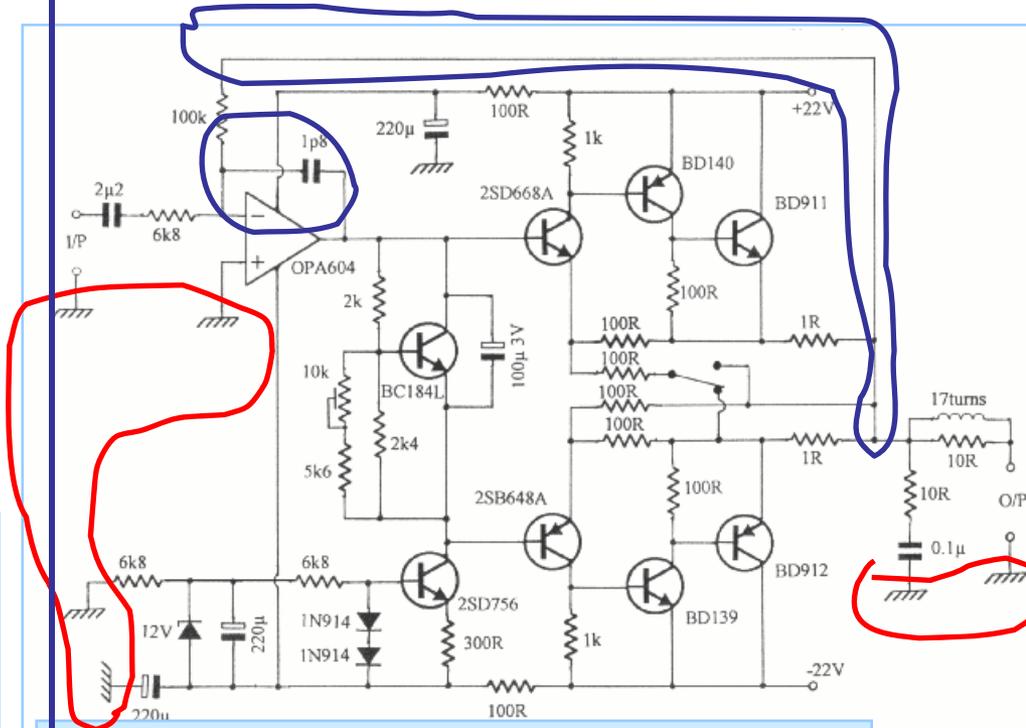IN PRACTICE NODES MAY ASSUME STRANGE FORMS




LOW DISTORTION POWER AMPLIFIER

LOW VOLTAGE POWER SUPPLY FOR CRT - PARTIAL VIEW




COMPONENT SIDE

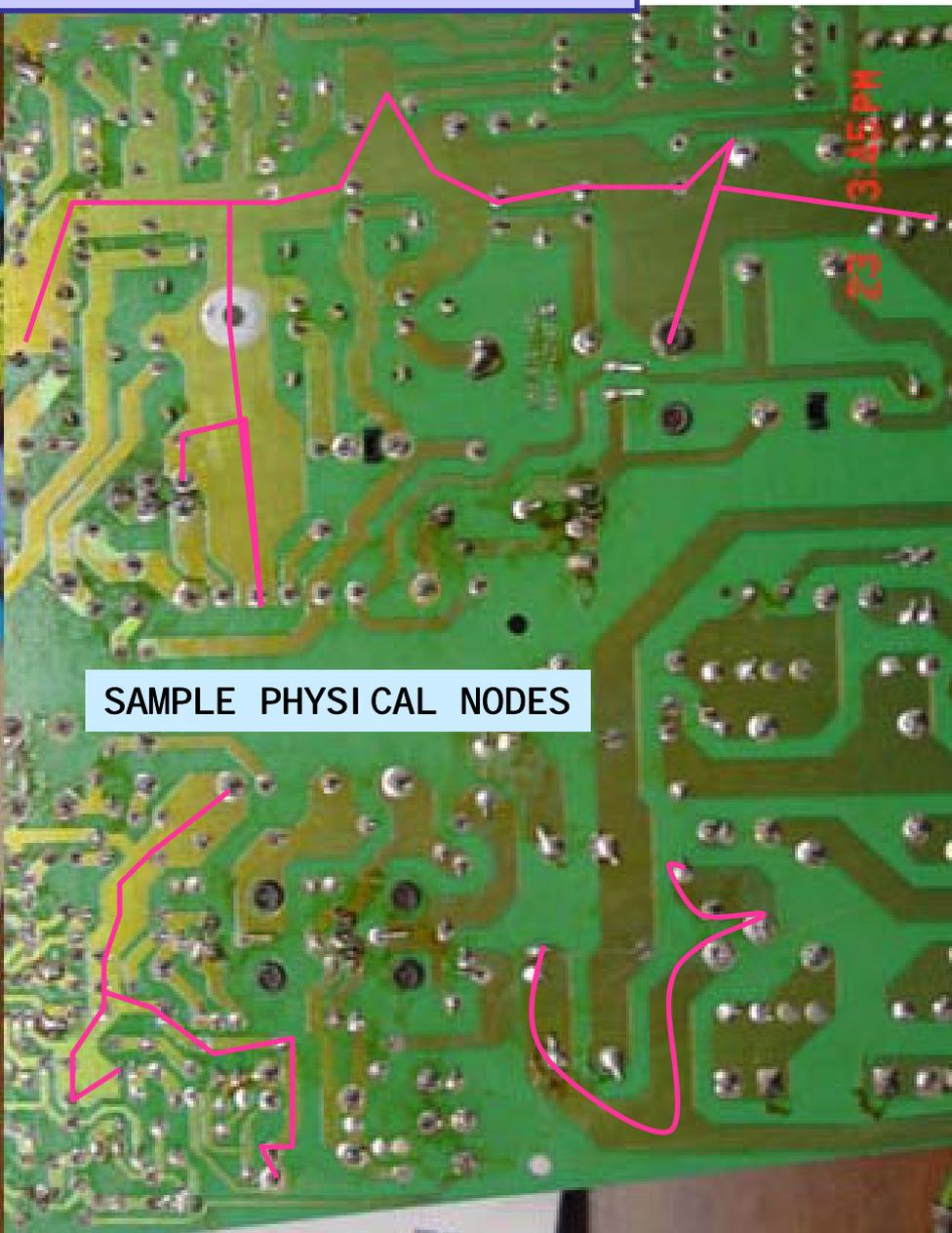

SAMPLE PHYSICAL NODES

CONNECTION SIDE

BASIC CURRENT DIVIDER

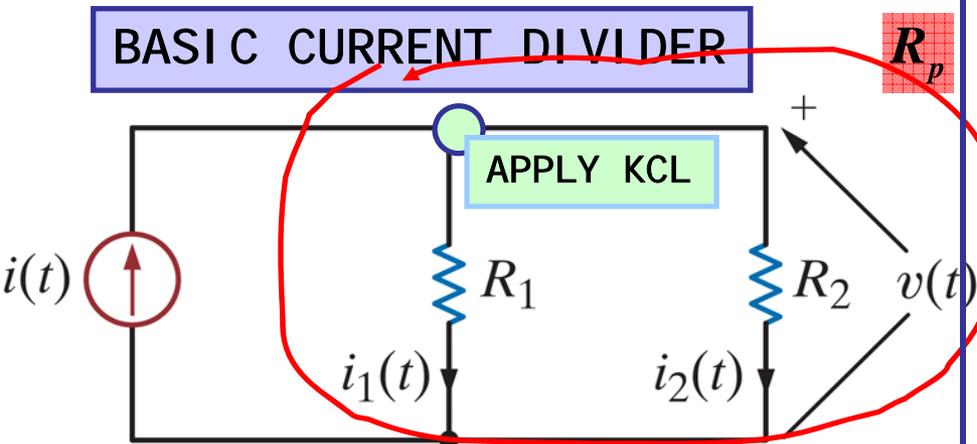

THE CURRENT $i(t)$ ENTERS THE NODE AND SPLITS - IT IS DIVIDED BETWEEN THE CURRENTS $i_1(t)$ AND $i_2(t)$

$$i(t) = i_1(t) + i_2(t)$$

USE OHM'S LAW TO REPLACE CURRENTS

$$\begin{aligned} i(t) &= \frac{v(t)}{R_1} + \frac{v(t)}{R_2} \\ &= \left(\frac{1}{R_1} + \frac{1}{R_2} \right) v(t) \end{aligned}$$

DEFINE "PARALLEL RESISTANCE COMBINATION"

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} \quad i(t) = \frac{1}{R_p} v(t)$$


$$R_p = \frac{R_1 R_2}{R_1 + R_2} \quad v(t) = \frac{R_1 R_2}{R_1 + R_2} i(t)$$

THE CURRENT DIVISION

$$i_1(t) = \frac{v(t)}{R_1} \quad i_2(t) = \frac{v(t)}{R_2}$$


$$i_1(t) = \frac{R_2}{R_1 + R_2} i(t) = \frac{R_1}{R_1 + R_2} i(t)$$

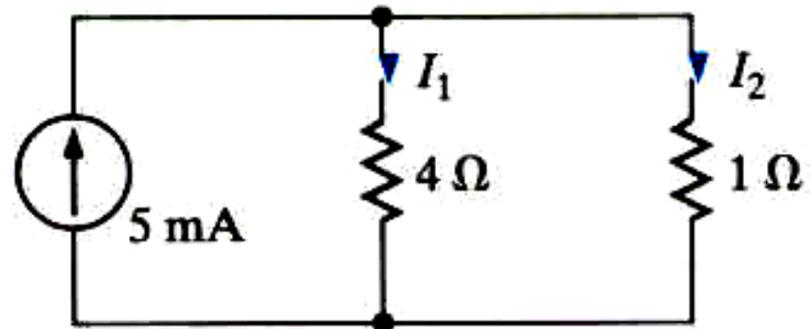Find I_1 and I_2 in the following circuit:




$$I_1 = \frac{1}{1+4} (5) = 1 \text{ mA} \quad I_2 = I - I_1 = \frac{4}{1+4} (5)$$

FIND I_1, I_2, V_o

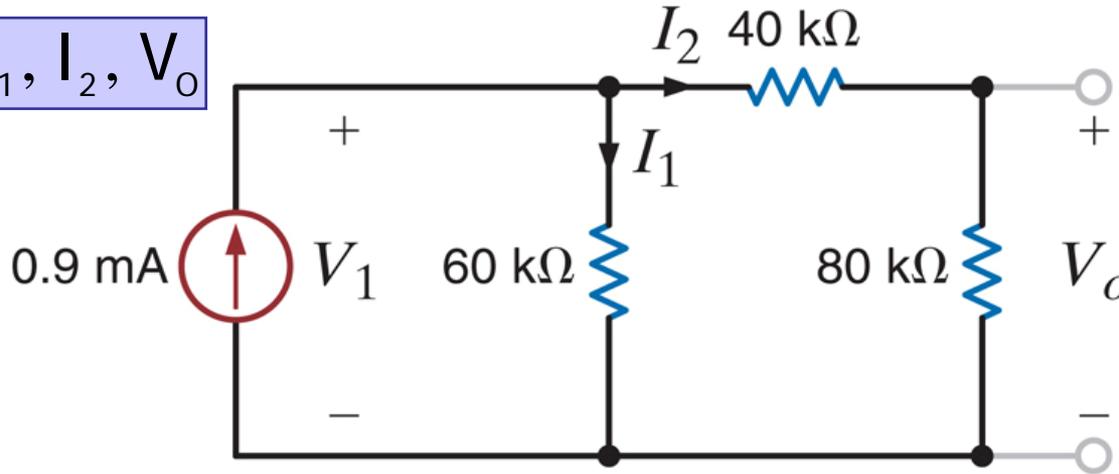

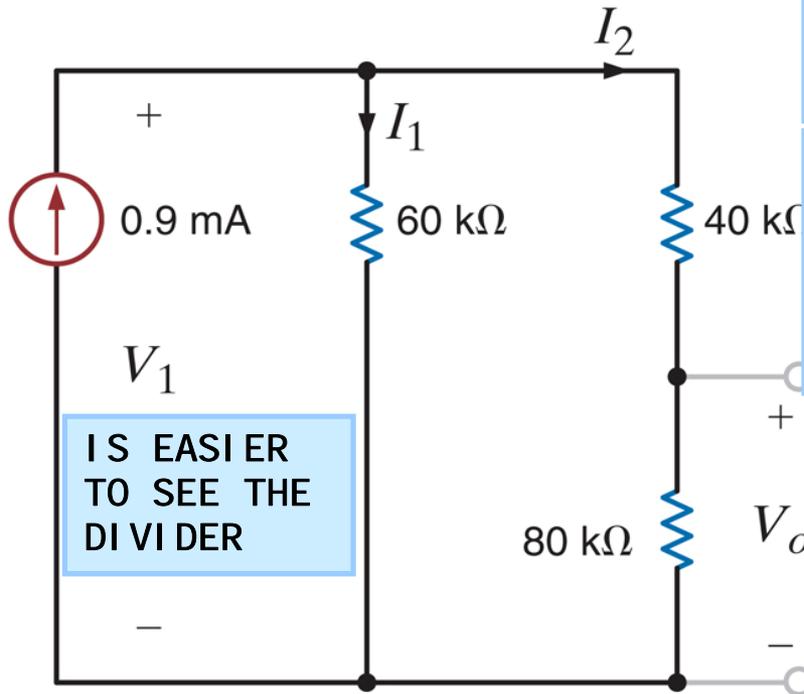WHEN I'N DOUBT... REDRAW THE CIRCUIT TO HIGHLIGHT ELECTRICAL CONNECTIONS!!



IS EASIER TO SEE THE DIVIDER

$$I_1 = \left[\frac{40k + 80k}{60k + (40k + 80k)} \right] (0.9 \times 10^{-3})$$

$$= 0.6 \text{ mA}$$



$$I_2 = \left[\frac{60k}{60k + (40k + 80k)} \right] (0.9 \times 10^{-3})$$

$$= 0.3 \text{ mA}$$

$$V_o = 80k * I_2$$

$$= 24V$$

CAR STEREO AND CIRCUIT MODEL

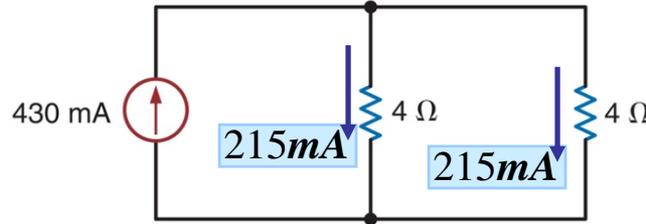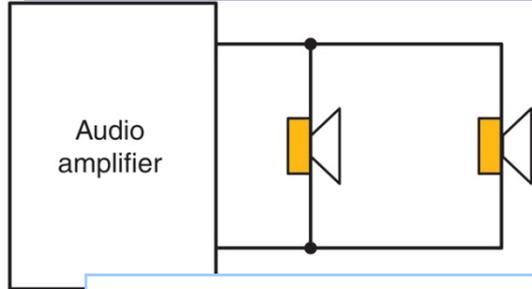

$$P = I^2 R$$

$$= (215 \times 10^{-3})^2 (4)$$


$$= 184.9 \text{ mW}$$

POWER PER SPEAKER $P = I^2 R$

LEARNING EXTENSION - CURRENT DIVIDER

THERE IS MORE THAN ONE OPTION TO COMPUTE I2

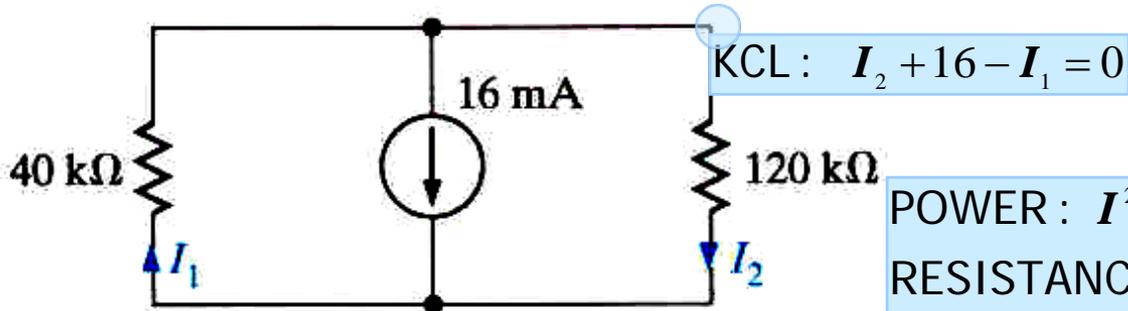I_1 and I_2 and the power absorbed by the 40-kΩ



USING CURRENT DIVIDER

$$I_2 = -\frac{40}{120 + 40}(16) = -4 \text{ mA}$$

POWER: $I^2 R$

RESISTANCE IN kΩ,


$$P = 144 * 40 \text{ mW} = 5.76 \text{ W}$$

CURRENT IN mA YIELD POWER IN mW

$$I_1 = \frac{120}{120 + 40}(16) \quad I_1 = 12 \text{ mA}$$


FIRST GENERALIZATION: MULTIPLE SOURCES

APPLY KCL TO THIS NODE

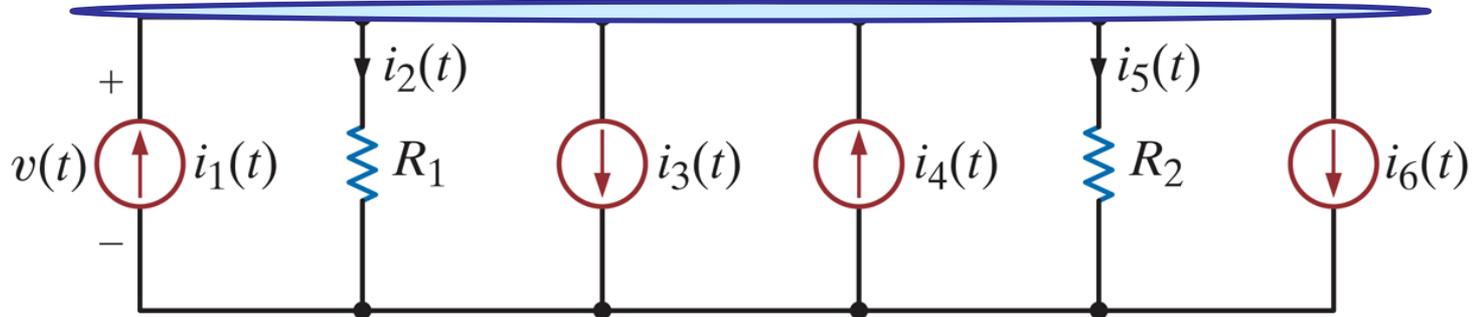

$$\underline{i_1(t)} - i_2(t) - \underline{i_3(t)} + \underline{i_4(t)} - i_5(t) - \underline{i_6(t)} = 0$$

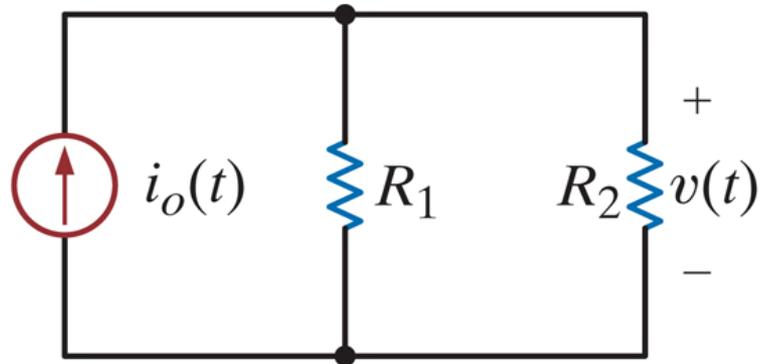EQUIVALENT SOURCE $i_o(t) = i_1(t) - i_3(t) + i_4(t) - i_6(t)$



DEFINE "PARALLEL RESISTANCE COMBINATION"



$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$R_p = \frac{R_1 R_2}{R_1 + R_2}$$

$$i_o(t) = \frac{1}{R_p} v(t)$$

$$v(t) = \frac{R_1 R_2}{R_1 + R_2} i_o(t)$$

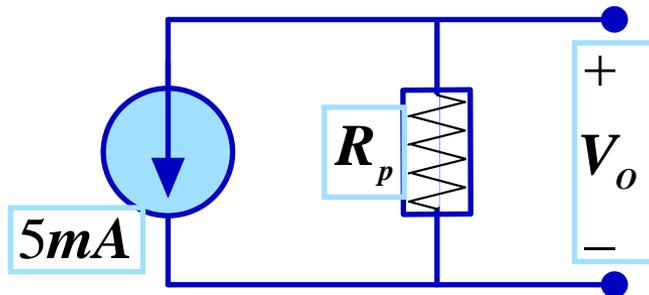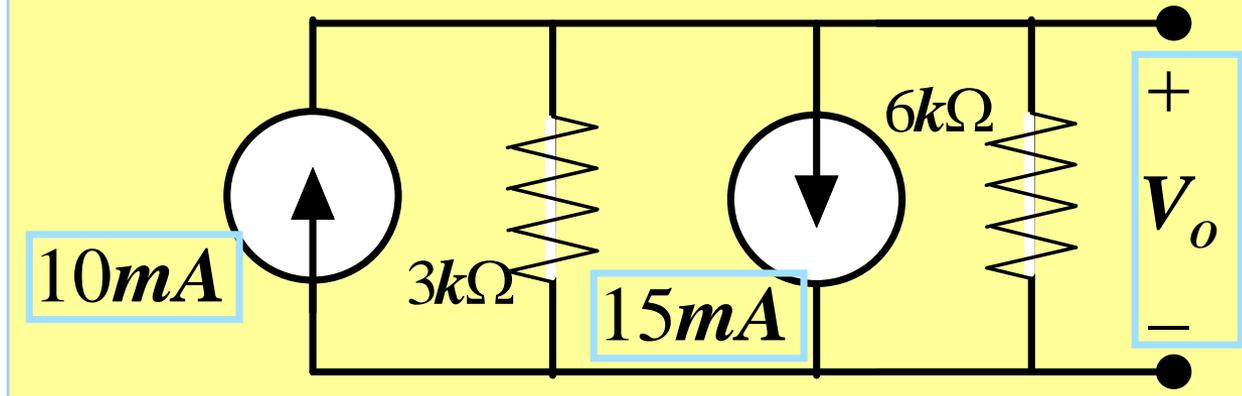FIND V_o AND THE POWER SUPPLIED BY THE SOURCES



$$R_p = \frac{6k * 3k}{6k + 3k} = 2k\Omega$$


$$V_o = -10V$$

$$P_{15mA} = V_o (15mA) = -150mW$$

$$P_{10mA} = V_o (-10mA) = 100mW$$

SECOND GENERALIZATION: MULTIPLE RESISTORS

APPLY KCL TO THIS NODE

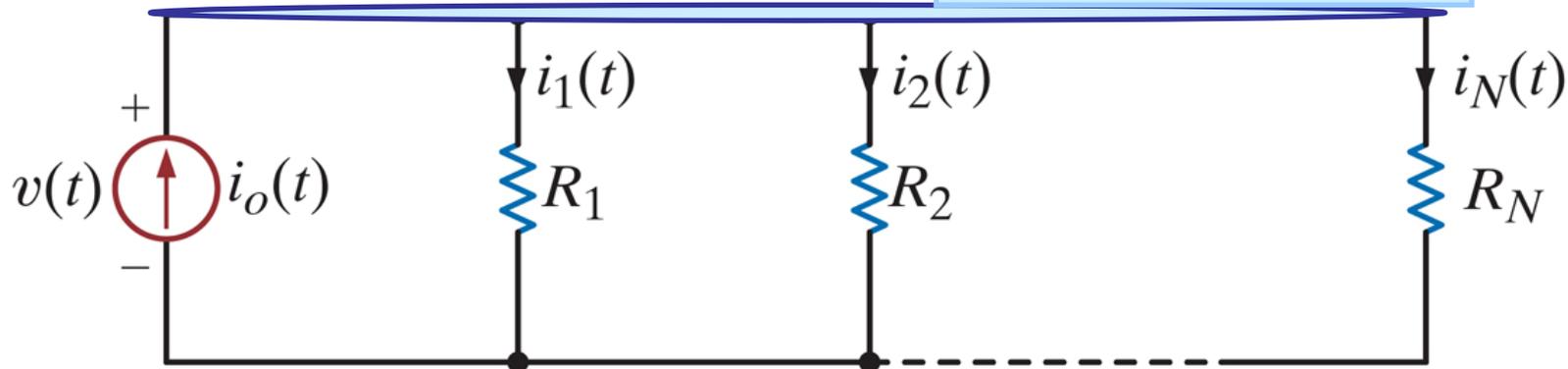

$$\begin{aligned}
 i_o(t) &= i_1(t) + i_2(t) + \dots + i_N(t) \\
 &= \left(\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N} \right) v(t)
 \end{aligned}$$


Ohm's Law at every resistor

$$\frac{1}{R_p} = \sum_{i=1}^N \frac{1}{R_i} \quad i_o(t) = \frac{v(t)}{R_p}$$

$$\left. \begin{aligned}
 v(t) &= R_p i_o(t) \\
 i_k(t) &= \frac{v(t)}{R_k}
 \end{aligned} \right\} \Rightarrow i_k(t) = \frac{R_p}{R_k} i_o(t)$$

General current divider

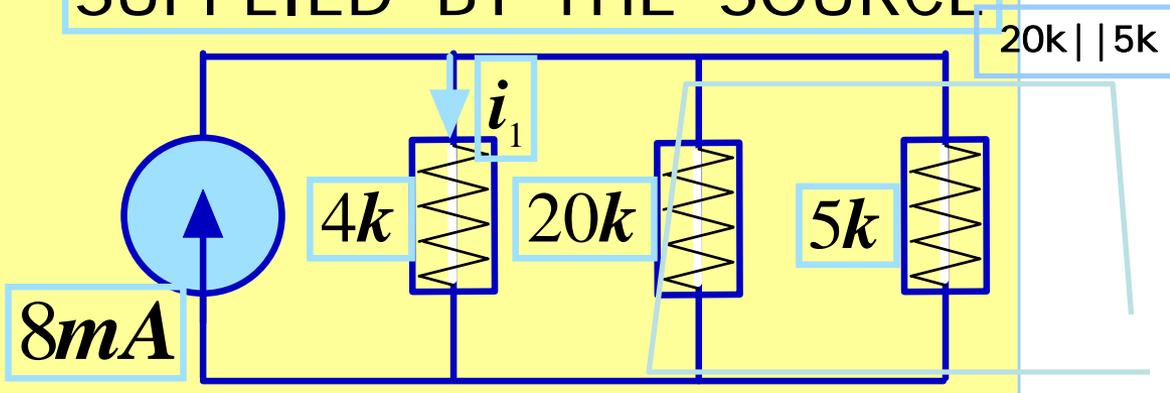FIND i_1 AND THE POWER SUPPLIED BY THE SOURCE



$$\frac{1}{R_p} = \frac{1}{4k} + \frac{1}{20k} + \frac{1}{5k} = \frac{5+1+4}{20k} = \frac{1}{2k} \Rightarrow R_p = 2k$$

$$i_1 = \frac{2k}{4k}(8) = 4mA$$


$$v = 4k * i_1 = 16V$$

$$P = v(-8mA) = -128mW$$


$$\left. \begin{aligned} v(t) &= R_p i_o(t) \\ i_k(t) &= \frac{v(t)}{R_k} \end{aligned} \right\} \Rightarrow i_k(t) = \frac{R_p}{R_k} i_o(t)$$

General current divider


AN ALTERNATIVE APPROACH

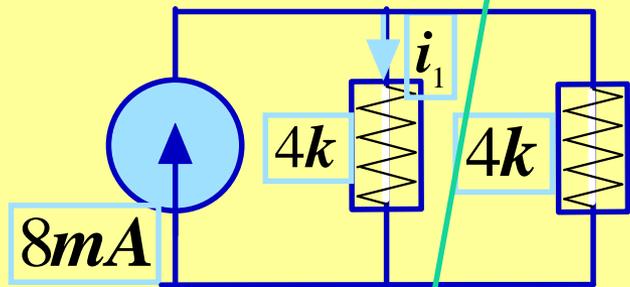

FIND THE CURRENT I_L

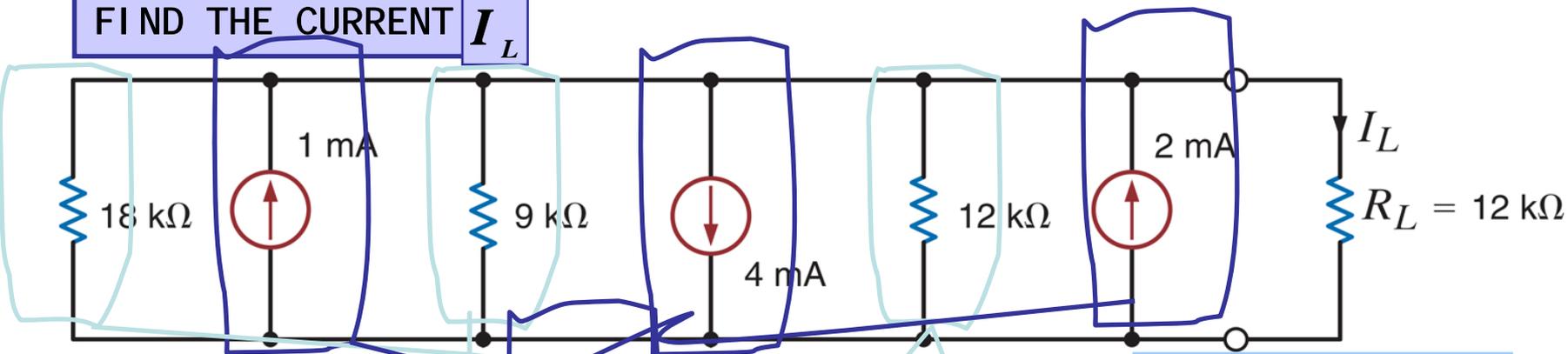


COMBINE THE SOURCES

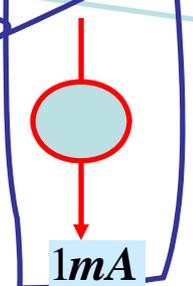

COMBINE RESISTORS

$$\frac{1}{R_p} = \frac{1}{18k} + \frac{1}{9k} + \frac{1}{12k}$$

$$R_p = 4 \text{ k}\Omega$$

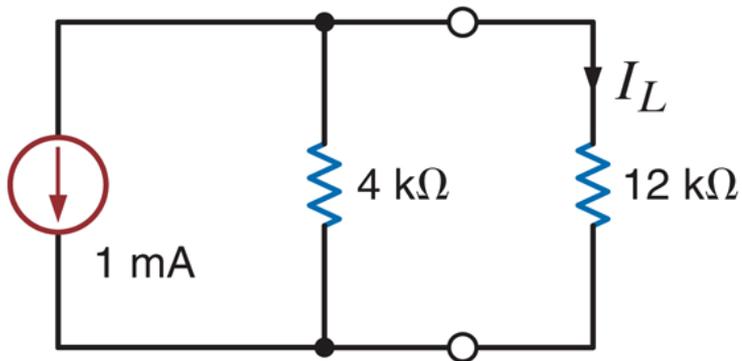


STRATEGY: CONVERT THE PROBLEM INTO A BASIC CURRENT DIVIDER BY COMBINING SOURCES AND RESISTORS. THE NEXT SECTION EXPLORES IN MORE DETAIL THE IDEA OF COMBINING RESISTORS

$$I_L = - \left[\frac{4k}{4k + 12k} \right] (1 \times 10^{-3})$$



$$= -0.25 \text{ mA}$$

NOTICE THE MINUS SIGN

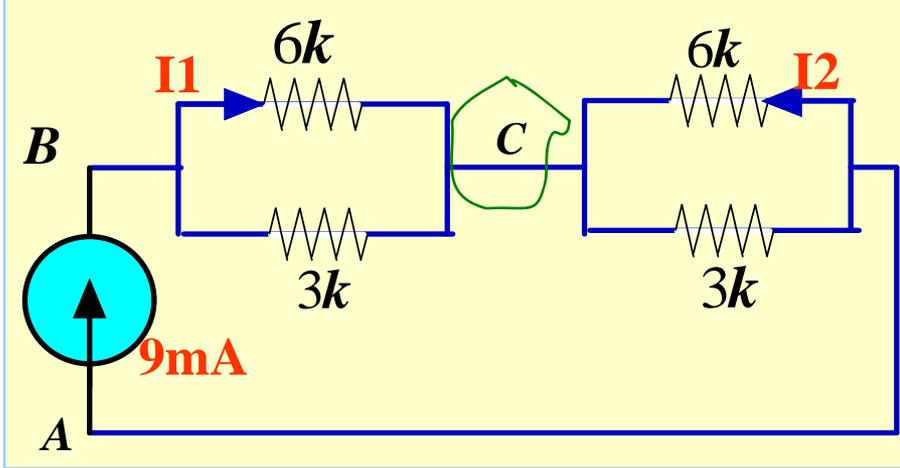


$$I_1 = \frac{3}{9} 9[mA] = 3mA$$


$$I_2 = -I_1$$

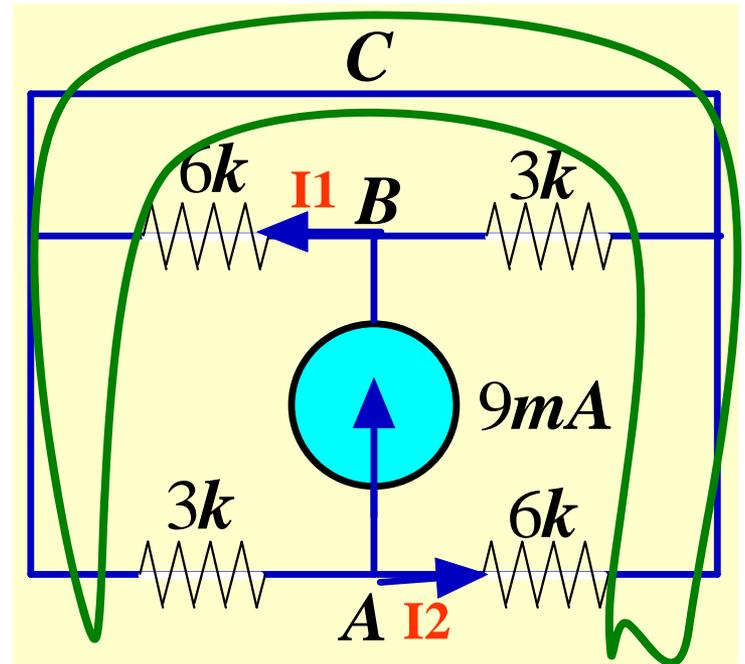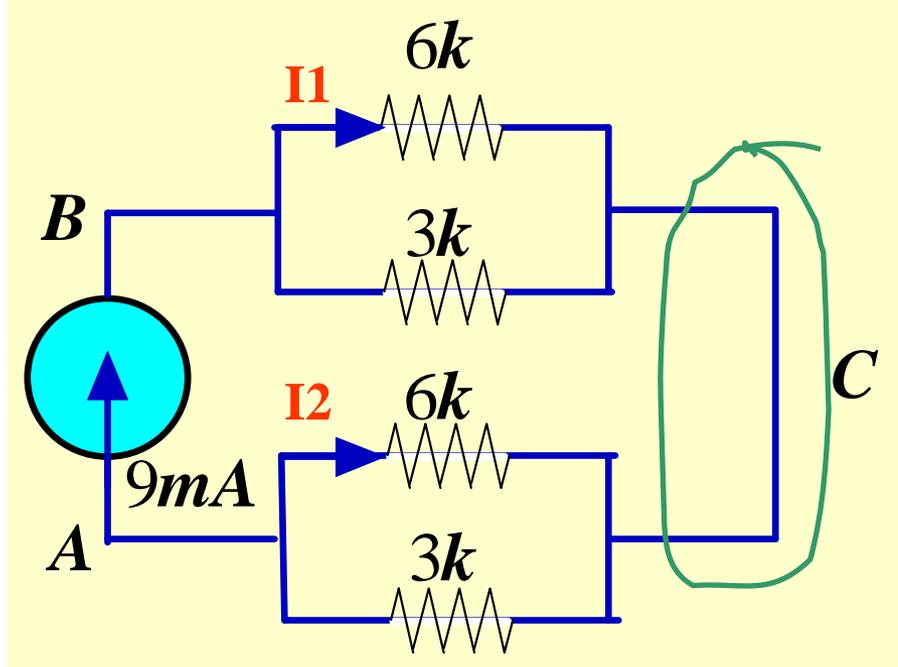


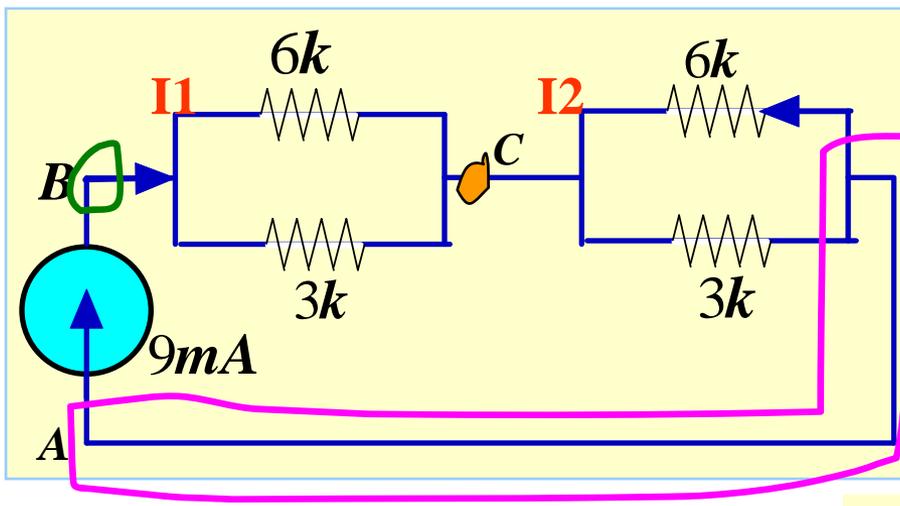DIFFERENT LOOKS FOR THE SAME ELECTRIC CIRCUIT



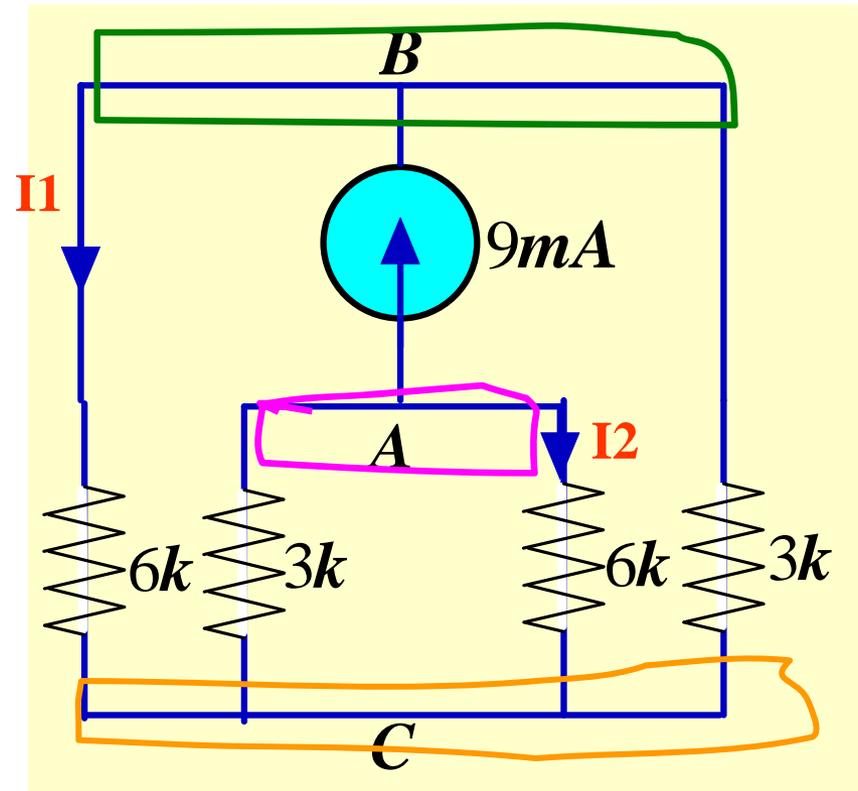REDRAWING A CIRCUIT MAY, SOMETIMES, HELP TO VISUALIZE BETTER THE ELECTRICAL CONNECTIONS



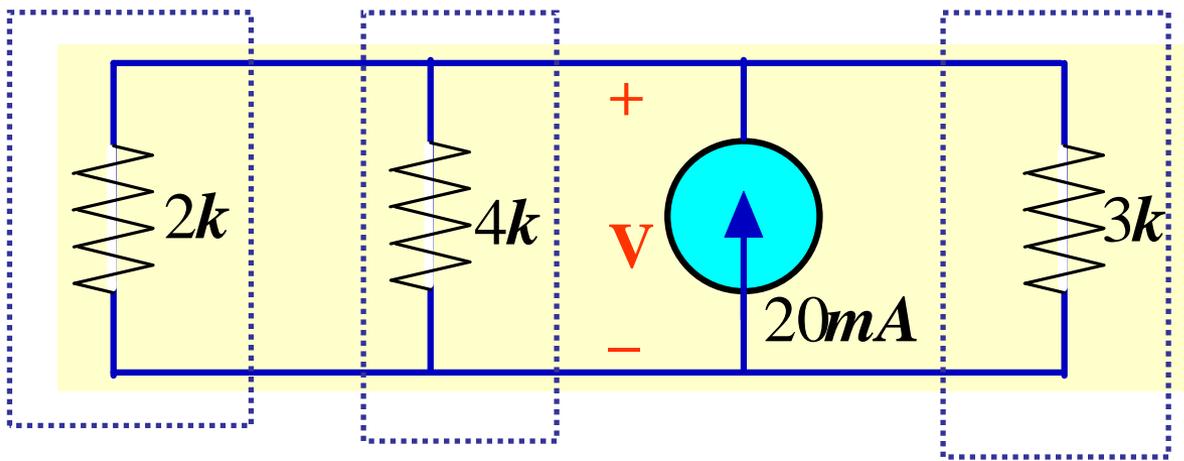

Determine power delivered by source

$$P = R_p * (20mA)^2$$

$$\frac{1}{R_p} = \frac{1}{2k} + \frac{1}{4k} + \frac{1}{3k} = \frac{6+3+4}{12k}$$

$$R_p = \frac{12}{13}k$$

$$P = \frac{12}{13} * 10^3 \Omega * (20 * 10^{-3})^2 [A]$$

$$P = \frac{4.800}{13} W$$