

ADDITIONAL ANALYSIS TECHNIQUES

REVIEW LINEARITY

The property has two equivalent definitions.
We show an application of homogeneity

APPLY SUPERPOSITION

We discuss some implications of the superposition property in linear circuits









THE METHODS OF NODE AND LOOP ANALYSIS PROVIDE POWERFUL TOOLS TO DETERMINE THE BEHAVIOR OF EVERY COMPONENT IN A CIRCUIT

The techniques developed with combination series/parallel, voltage divider and current divider are special techniques that are more efficient than the general methods, but have a limited applicability. It is to our advantage to keep them in our repertoire and use them when they are more efficient.

In this section we develop additional techniques that simplify the analysis of some circuits.

In fact these techniques expand on concepts that we have already introduced: linearity and circuit equivalence

SOME EQUIVALENT CIRCUITS
ALREADY USED

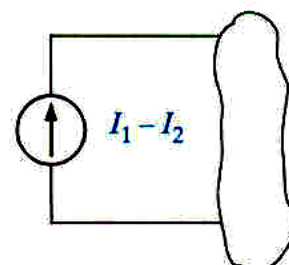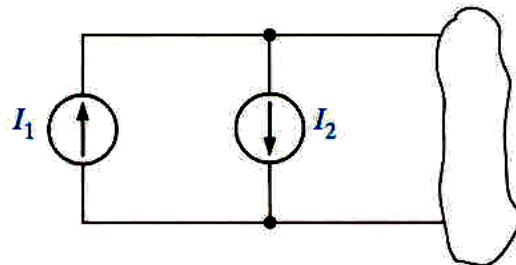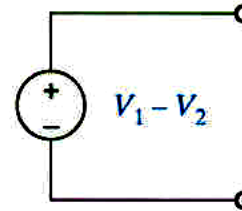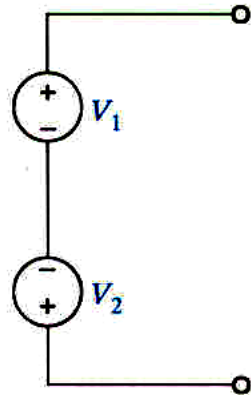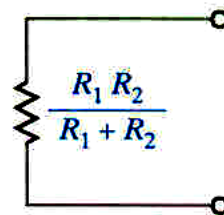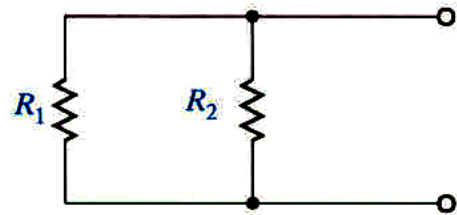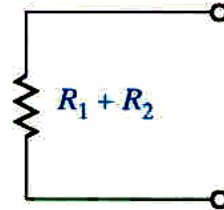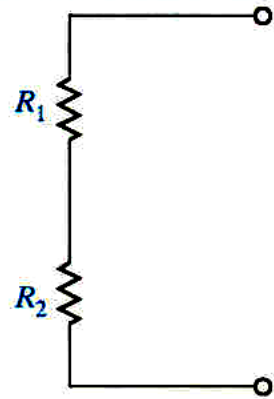

LINEARITY

THE MODELS USED ARE ALL LINEAR.
MATHEMATICALLY THIS IMPLIES THAT THEY
SATISFY THE PRINCIPLE OF SUPERPOSITION

THE MODEL $y = Tu$ IS LINEAR IFF

$$T(\alpha_1 u_1 + \alpha_2 u_2) = \alpha_1 T u_1 + \alpha_2 T u_2$$

for all possible input pairs u_1, u_2
and all possible scalars α_1, α_2

AN ALTERNATIVE, AND EQUIVALENT,
DEFINITION OF LINEARITY SPLITS THE
SUPERPOSITION PRINCIPLE IN TWO.

THE MODEL $y = Tu$ IS LINEAR IFF

1. $T(u_1 + u_2) = T u_1 + T u_2, \forall u_1, u_2$ additivity
2. $T(\alpha u) = \alpha T u, \forall \alpha, \forall u$ homogeneity

FOR CIRCUIT ANALYSIS WE CAN USE THE
LINEARITY ASSUMPTION TO DEVELOP
SPECIAL ANALYSIS TECHNIQUES

Source Superposition

This technique is a direct application of linearity.

It is normally useful when the circuit has only a few sources.

FOR CLARITY WE SHOW A CIRCUIT WITH ONLY TWO SOURCES

Due to Linearity


$$V_L = a_1 V_S + a_2 I_S$$

CONTRIBUTION BY V_S

$$V_L^1$$

CONTRIBUTION BY I_S

$$V_L^2$$

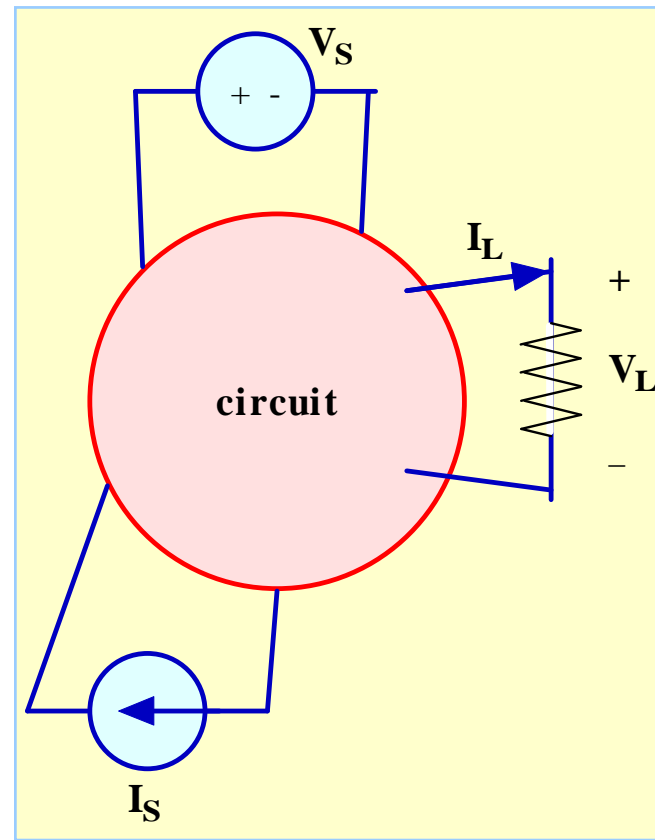


$$V_L^1$$

Can be computed by setting the current source to zero and solving the circuit


$$V_L^2$$

Can be computed by setting the voltage source to zero and solving the circuit

SOURCE SUPERPOSITION

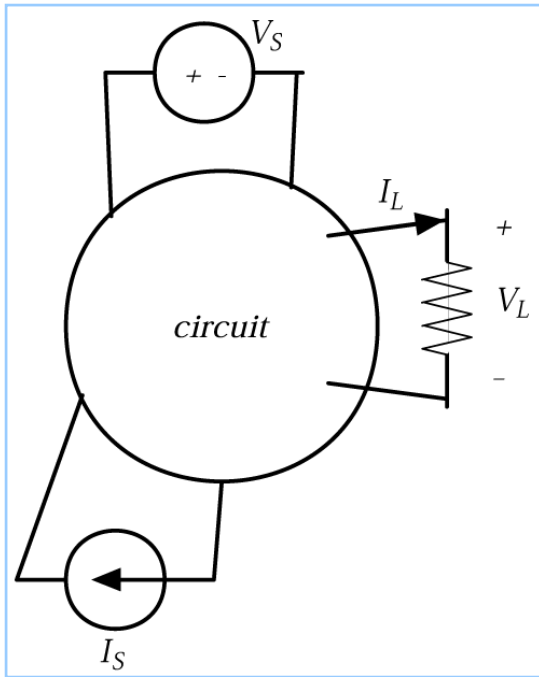


=

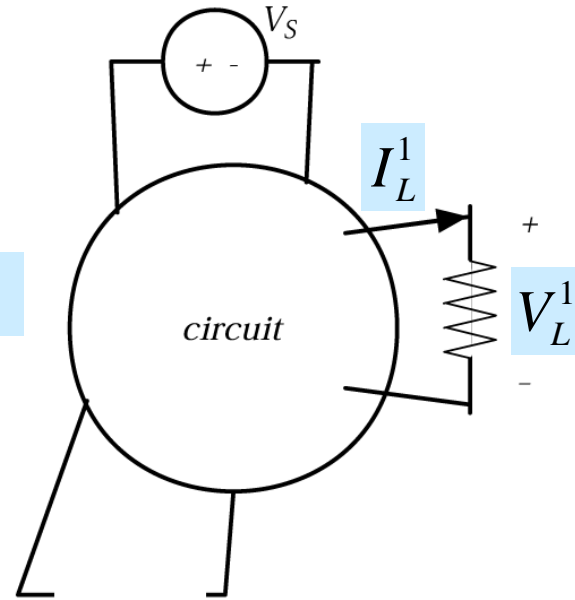

Circuit with current source set to zero (OPEN)

+

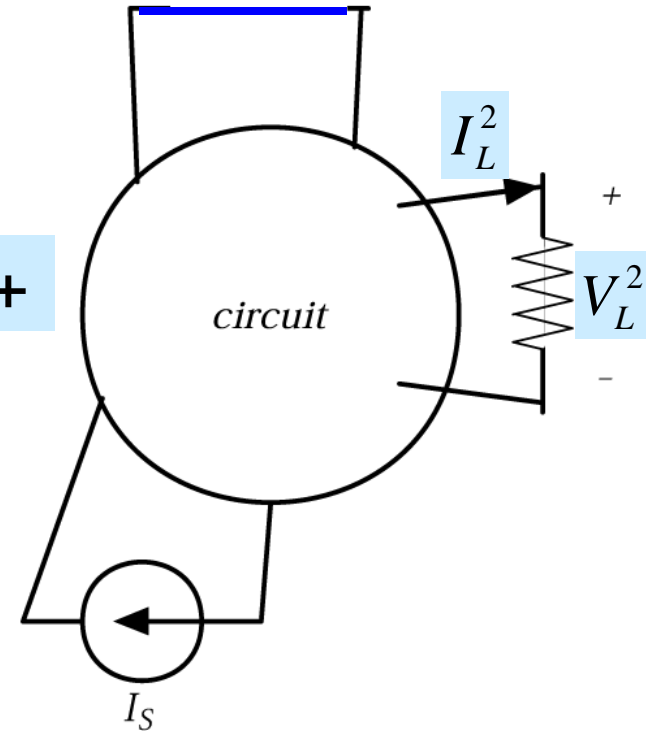

Circuit with voltage source set to zero (SHORT CIRCUITED)

Due to the linearity of the models we must have

$$I_L = I_L^1 + I_L^2 \quad V_L = V_L^1 + V_L^2$$


Principle of Source Superposition

The approach will be useful if solving the two circuits is simpler, or more convenient, than solving a circuit with two sources


We can have any combination of sources. And we can partition any way we find convenient

EXAMPLE


WE WISH TO COMPUTE THE CURRENT i_1

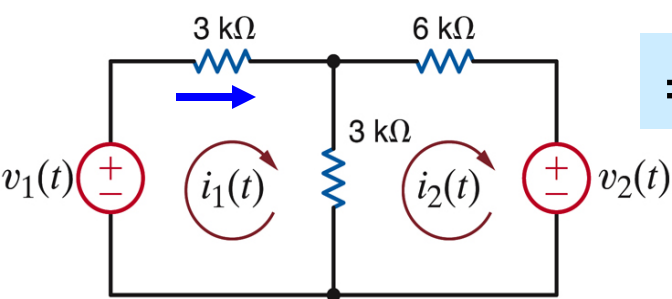

=

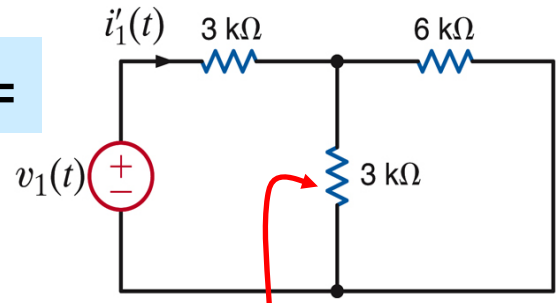

+

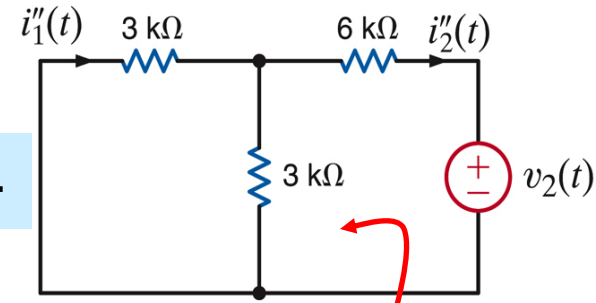

$$6ki_1(t) - 3ki_2(t) = v_1(t)$$

$$-3ki_1(t) + 9ki_2(t) = -v_2(t)$$

Loop equations

$$R_{eq} = 3 + 3 \parallel 6 [k]$$

$$R_{eq} = 6 + (3 \parallel 3) [k]$$

$$i_1'(t) = \frac{v_1(t)}{3k + \frac{(3k)(6k)}{3k + 6k}}$$

$$= \frac{v_1(t)}{5k}$$

Contribution of v_1


$$i_2'' = \frac{v_2}{R_{eq}}$$

$$i_1''(t) = \frac{-2v_2(t)}{15k} \left(\frac{3k}{3k + 3k} \right)$$


$$= \frac{-v_2(t)}{15k}$$

Contribution of v_2

Once we know the “partial circuits” we need to be able to solve them in an efficient manner

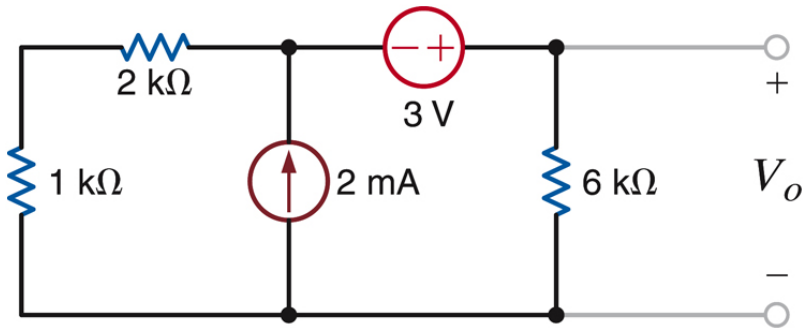EXAMPLECompute V_0 using source superposition


We set to zero the voltage source

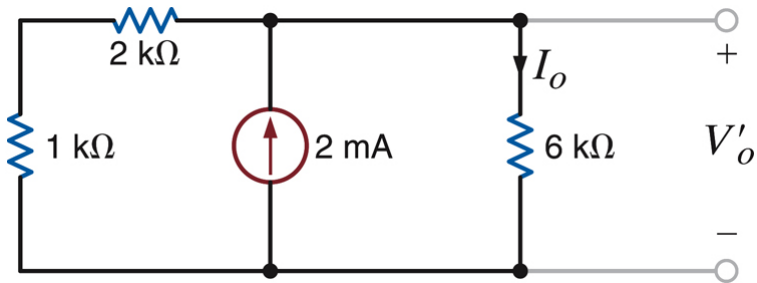


$$I_0 = (2 \times 10^{-3}) \left(\frac{1\text{k} + 2\text{k}}{1\text{k} + 2\text{k} + 6\text{k}} \right) \quad \text{Current division}$$

$$V'_0 = I_0(6\text{k}) = 4\text{ V} \quad \text{Ohm's law}$$

Now we set to zero the current source

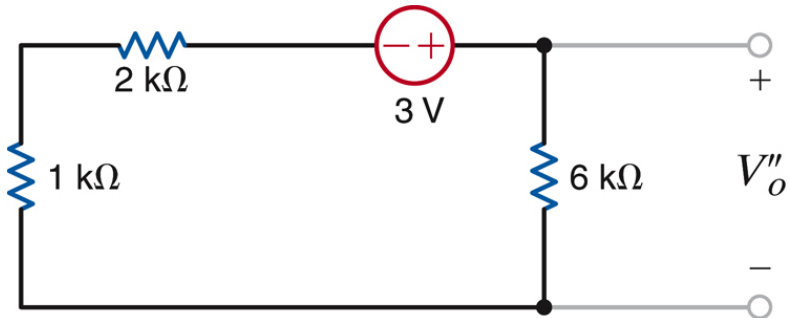


Voltage Divider

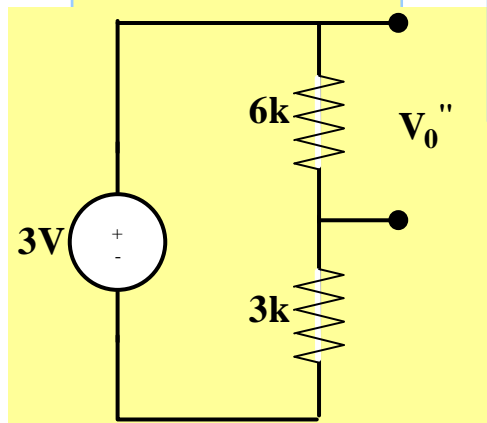


$$V''_0 = 3 \left(\frac{3\text{k}}{1\text{k} + 2\text{k} + 6\text{k}} \right) = 2[\text{V}]$$

$$V_0 = V'_0 + V''_0 = 6[\text{V}]$$

USE SOURCE SUPERPOSITION TO COMPUTE I_O

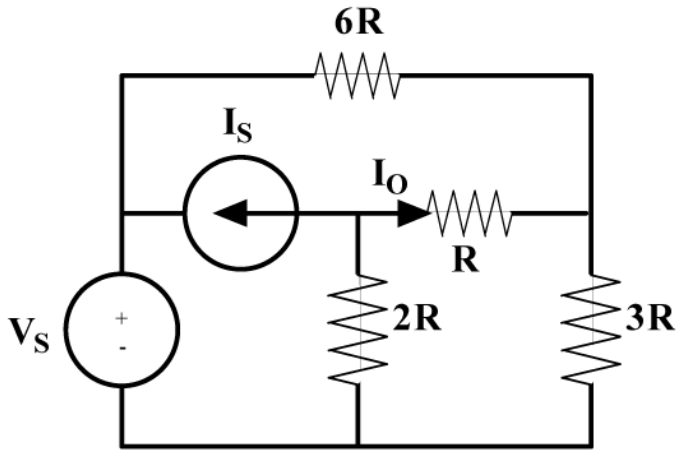


open current source

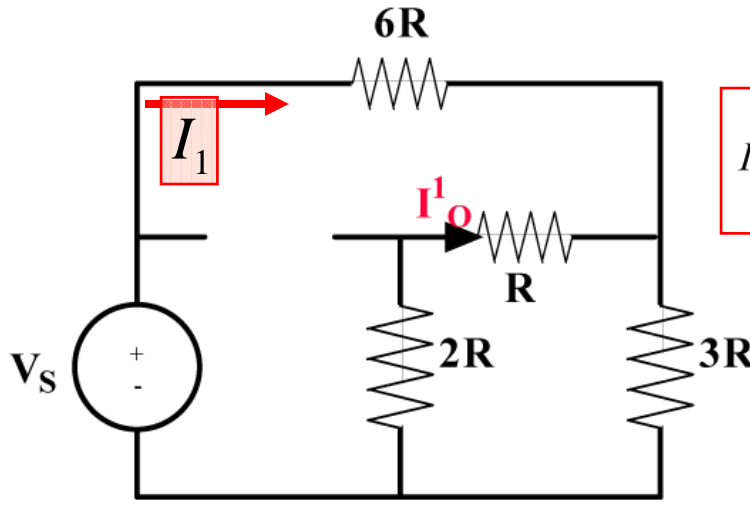


$$I_1 = \frac{V_s}{6R + \parallel 3R, 3R \parallel}$$

$$I_o^1 = -\frac{I_1}{2}$$

short circuit voltage source

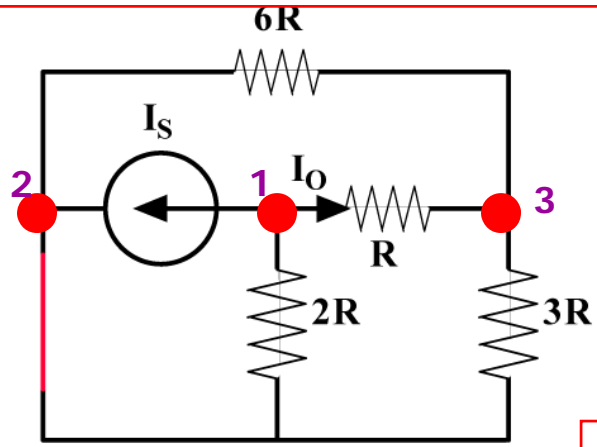

in case of doubt: REDRAW CIRCUIT!

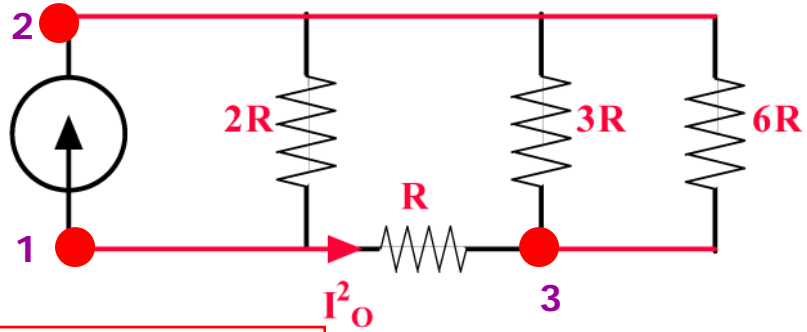

NOW USE CURRENT DIVIDER

$$I_o^2 = -\frac{2R}{2R + R + \parallel 3R, 6R \parallel} I_s$$

$$I_o^2 = -\frac{2}{5} I_s$$

$$I_o = I_o^1 + I_o^2$$

$$I_o = -\frac{V_s}{15R} - \frac{2}{5} I_s$$