

ADDITIONAL ANALYSIS TECHNIQUES

DEVELOP THEVENIN'S AND NORTON'S THEOREMS

These are two very powerful analysis tools that allow us to focus on parts of a circuit and hide away unnecessary complexities

MAXIMUM POWER TRANSFER

This is a very useful application of Thevenin's and Norton's theorems

THEVENIN'S AND NORTON'S THEOREMS


These are some of the most powerful analysis results to be discussed.

They permit to hide information that is not relevant and concentrate in what is important to the analysis

Low distortion audio power amplifier

TO MATCH SPEAKERS AND AMPLIFIER ONE SHOULD ANALYZE THIS CIRCUIT

From PreAmp (voltage)

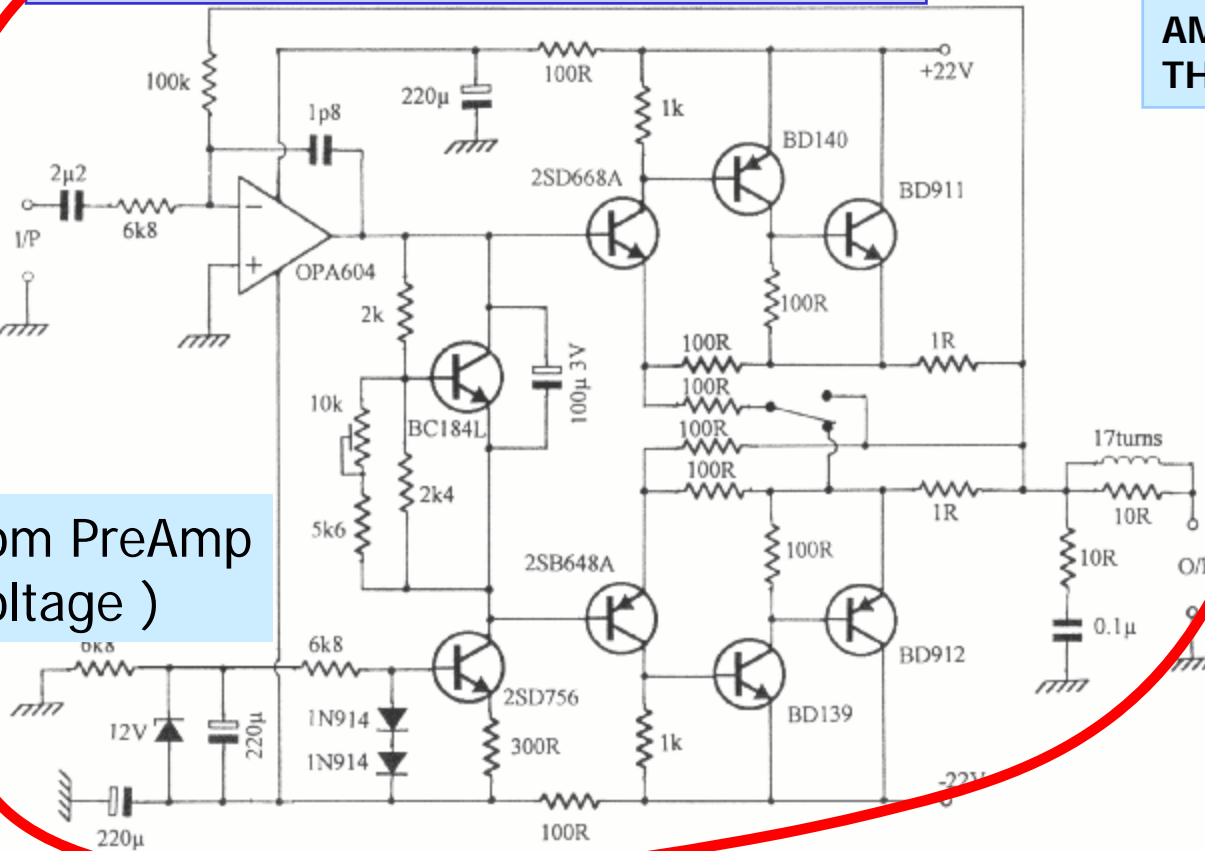


To speakers

Courtesy of M.J. Renardson



<http://angelfire.com/ab3/mjramp/index.html>

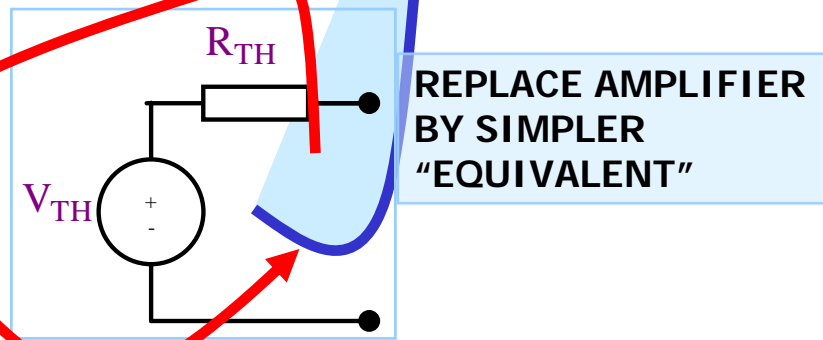TO MATCH SPEAKERS AND AMPLIFIER IT IS MUCH EASIER TO CONSIDER THIS EQUIVALENT CIRCUIT!



REPLACE AMPLIFIER BY SIMPLER "EQUIVALENT"



THEVENIN'S EQUIVALENCE THEOREM

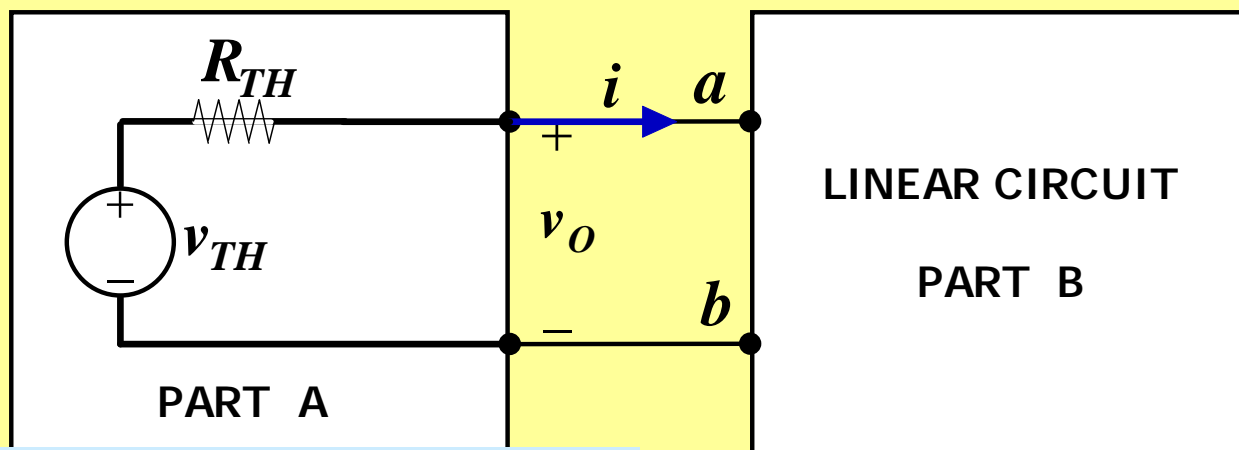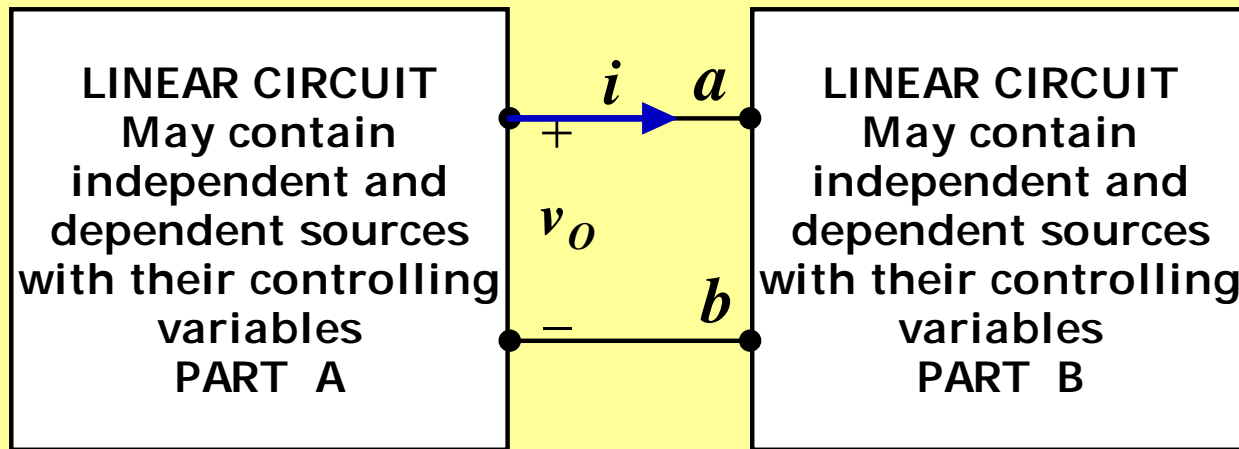

Thevenin Equivalent Circuit
for PART A

- v_{TH} Thevenin Equivalent Source
- R_{TH} Thevenin Equivalent Resistance

NORTON'S EQUIVALENCE THEOREM

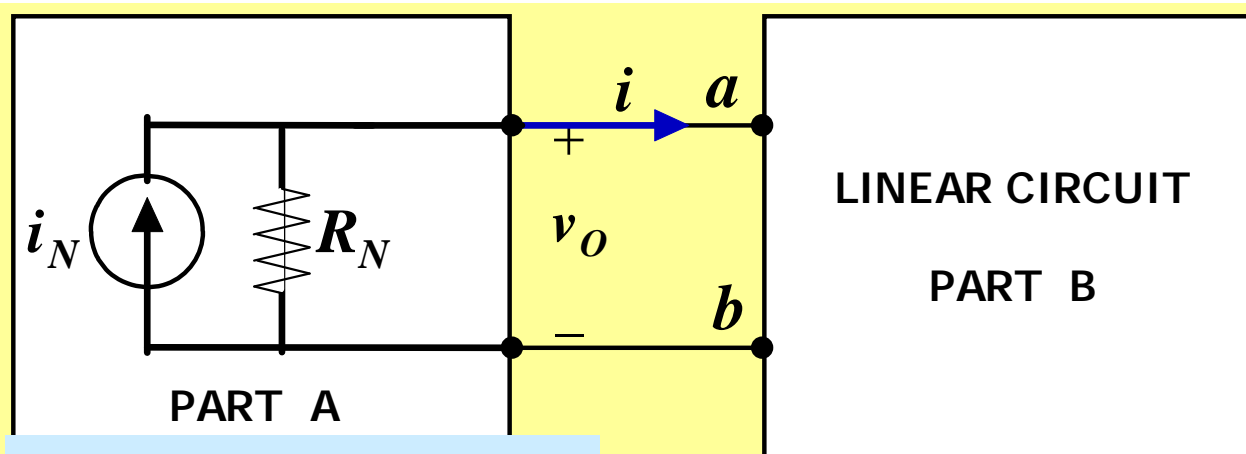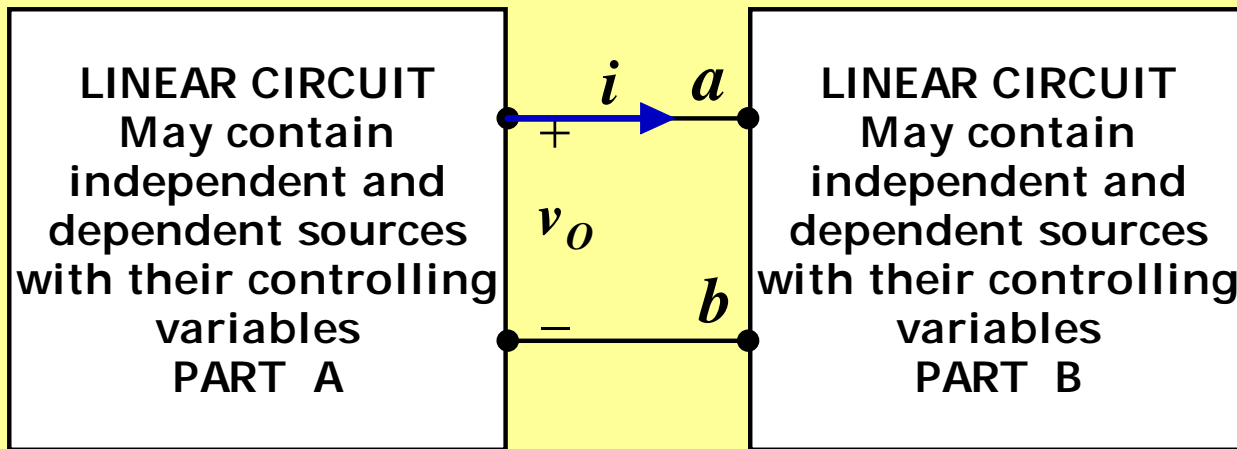


Norton Equivalent Circuit
for PART A

i_N Norton Equivalent Source

R_N Norton Equivalent Resistance

OUTLINE OF PROOF

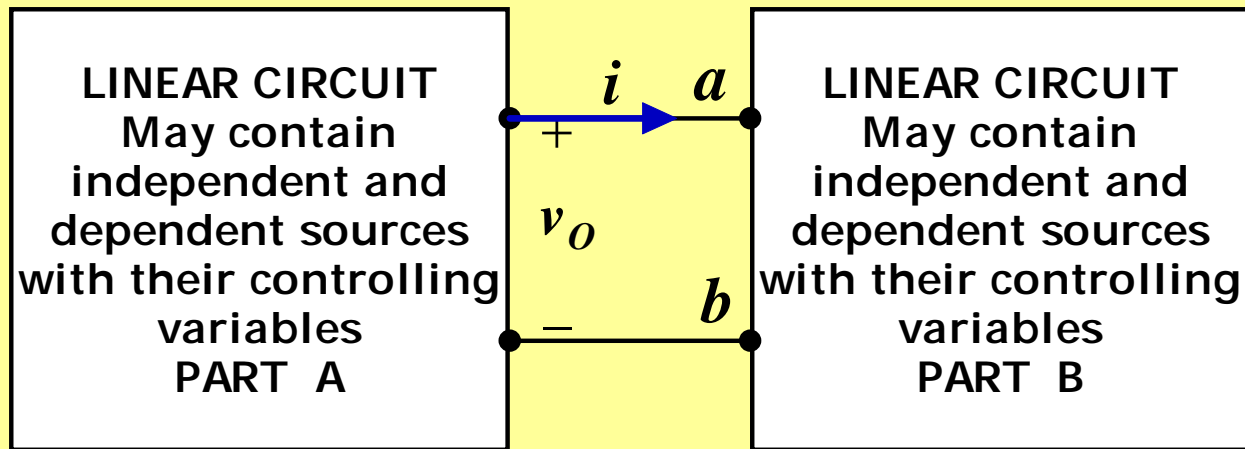


1. Because of the linearity of the models, for any Part B the relationship between v_o and the current, i , has to be of the form $v_o = m * i + n$
2. Result must hold for "every valid Part B" that we can imagine
3. If part B is an open circuit then $i=0$ and... $n = v_{OC}$
4. If Part B is a short circuit then v_o is zero. In this case

$$0 = m * i_{SC} + v_{OC} \Rightarrow m = -\frac{v_{OC}}{i_{SC}} = -R_{TH}$$


$$v_o = -R_{TH} i + v_{OC}$$

THEVENIN APPROACH

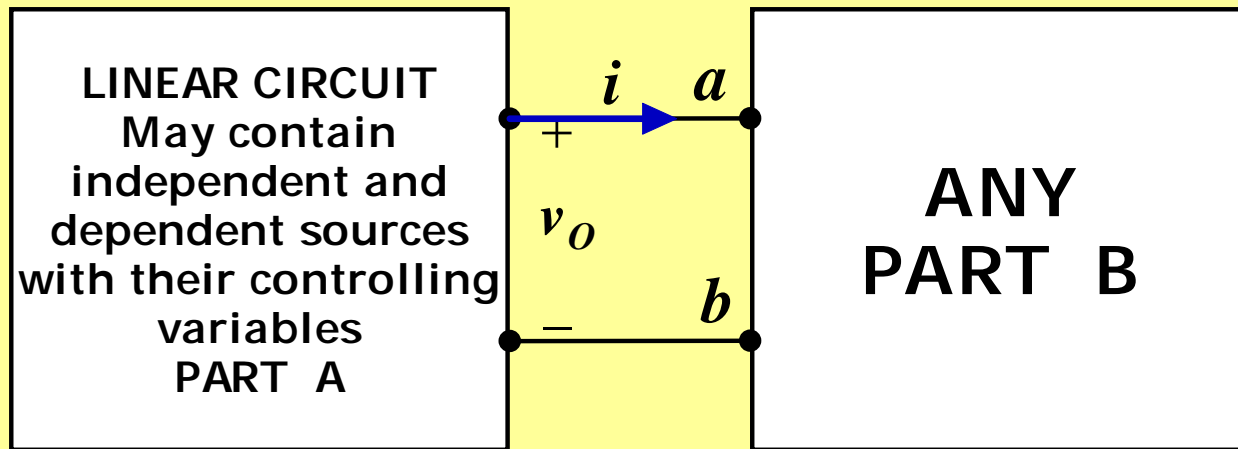

$$v_o = -R_{TH}i + v_{OC}$$

For ANY circuit in Part B

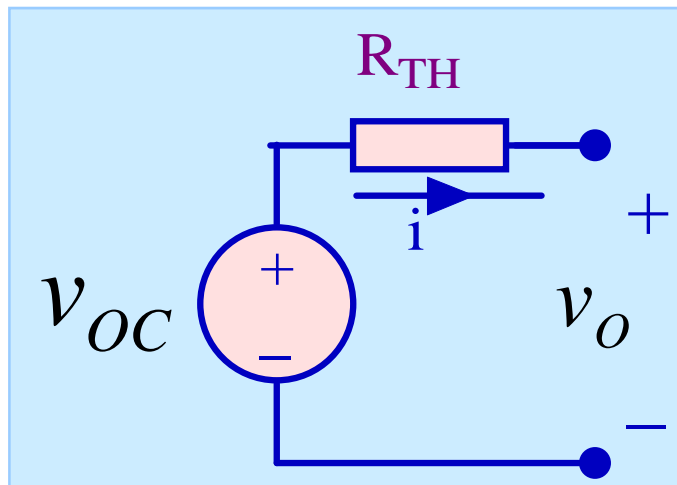

PART A MUST BEHAVE LIKE THIS CIRCUIT

This is the Thevenin equivalent circuit for the circuit in Part A



The voltage source is called the THEVENIN EQUIVALENT SOURCE

The resistance is called the THEVENIN EQUIVALENT RESISTANCE

Norton Approach

$$v_O = v_{OC} - R_{TH}i \Rightarrow i = \frac{v_{OC}}{R_{TH}} - \frac{v_O}{R_{TH}}$$


$$\frac{v_{OC}}{R_{TH}} = i_{SC}$$

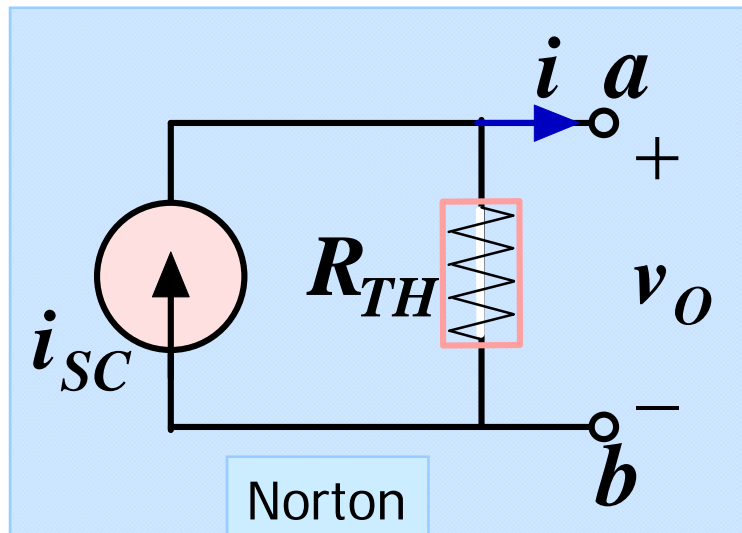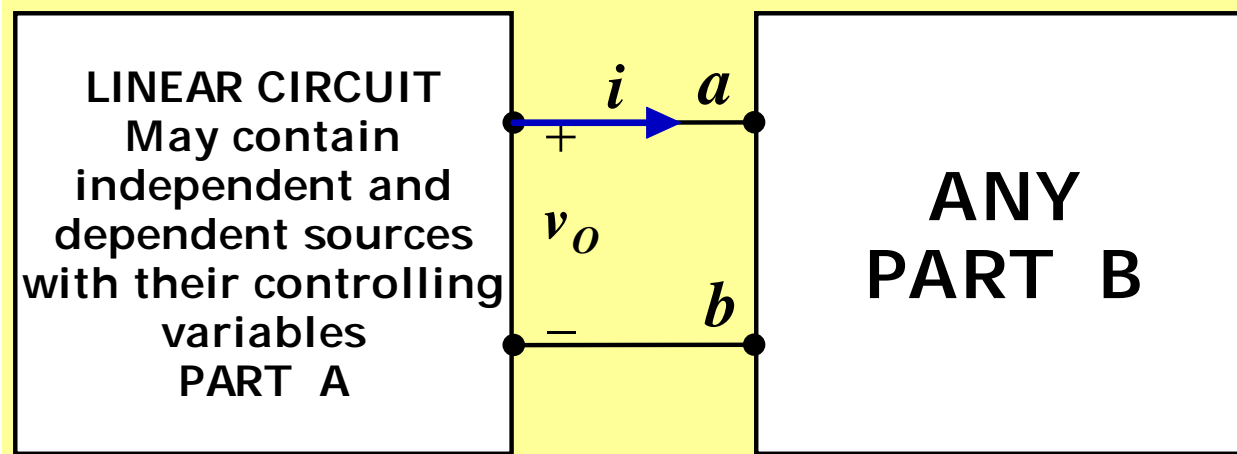


Norton Equivalent
Representation for Part A

i_{SC} Norton Equivalent Source

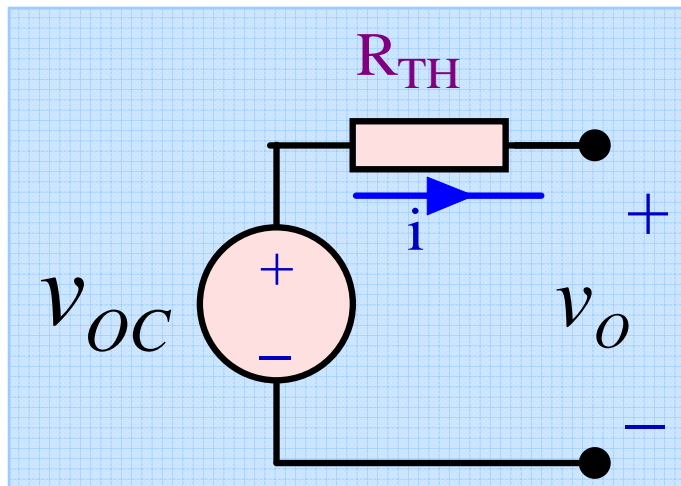ANOTHER VIEW OF THEVENIN'S AND NORTON'S THEOREMS



Thevenin

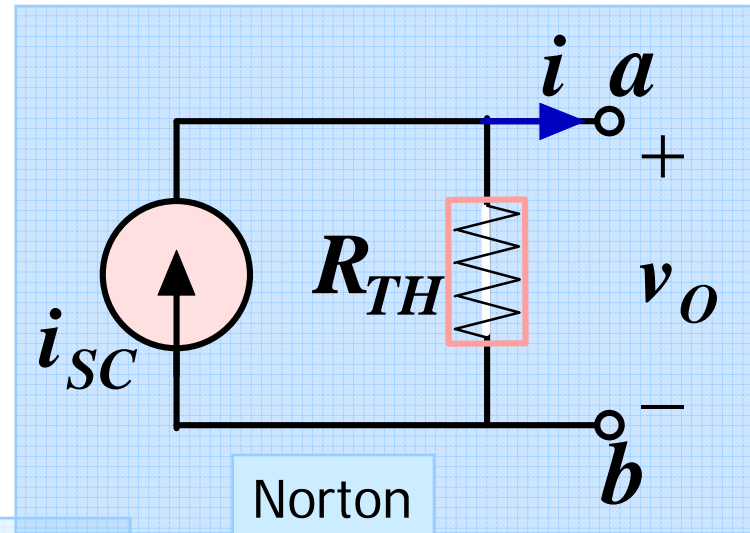


Norton

$$i_{SC} = \frac{v_{OC}}{R_{TH}}$$

This equivalence can be viewed as a source transformation problem. It shows how to convert a voltage source in series with a resistor into an equivalent current source in parallel with the resistor.

SOURCE TRANSFORMATION CAN BE A GOOD TOOL TO REDUCE THE COMPLEXITY OF A CIRCUIT


EXAMPLE: SOLVE BY SOURCE TRANSFORMATION

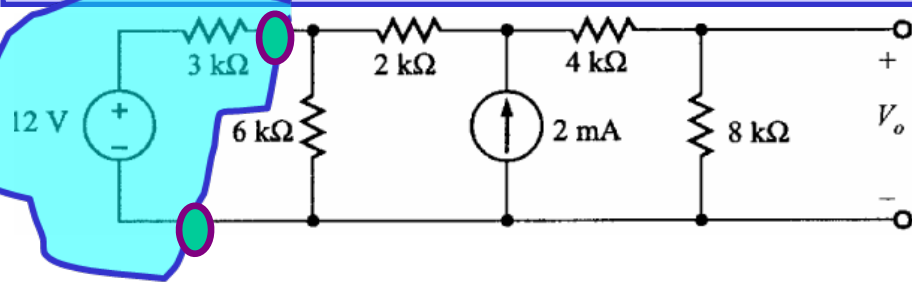

In between the terminals we connect a current source and a resistance in parallel

The equivalent current source will have the value $12V/3k$

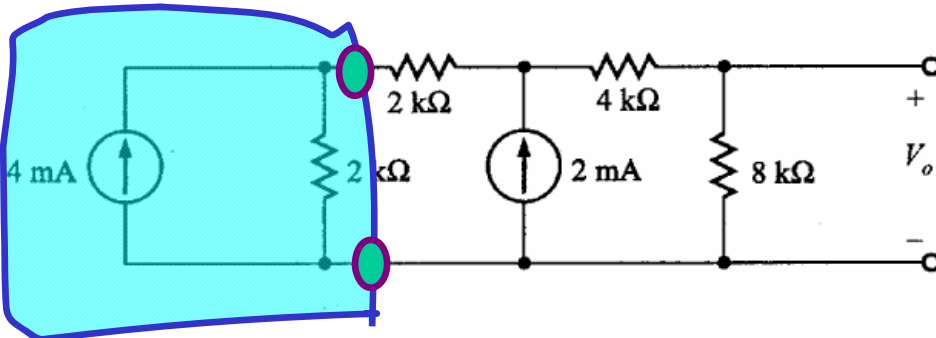
The 3k and the 6k resistors now are in parallel and can be combined



In between the terminals we connect a voltage source in series with the resistor

The equivalent source has value $4mA * 2k$

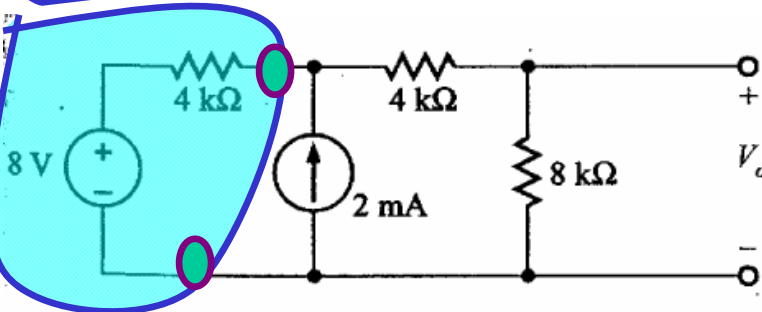The 2k and the 2k resistor become connected in series and can be combined




After the transformation the sources can be combined

The equivalent current source has value $8V/4k$ and the combined current source has value 4mA

Options at this point

1. Do another source transformation and get a single loop circuit

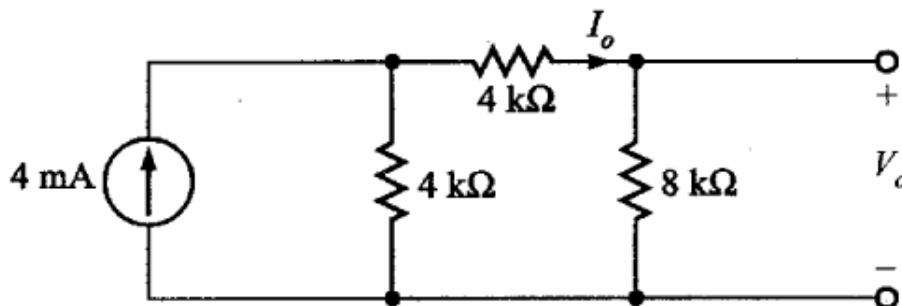2. Use current divider to compute I_0 and then compute V_0 using Ohm's law



A General Procedure to Determine the Thevenin Equivalent

v_{TH} Open Circuit voltage
voltage at a - b if Part B is removed

i_{SC} Short Circuit Current
current through a - b if Part B is replaced
by a short circuit

$R_{TH} = \frac{v_{TH}}{i_{SC}}$ Thevenin Equivalent Resistance

1. Determine the
Thevenin equivalent
source


Remove part B and
compute the OPEN
CIRCUIT voltage V_{ab}

2. Determine the
SHORT CIRCUIT
current


Remove part B and
compute the SHORT
CIRCUIT current I_{ab}

$$v_{TH} = v_{OC}, R_{TH} = \frac{v_{OC}}{i_{SC}}$$


One circuit problem

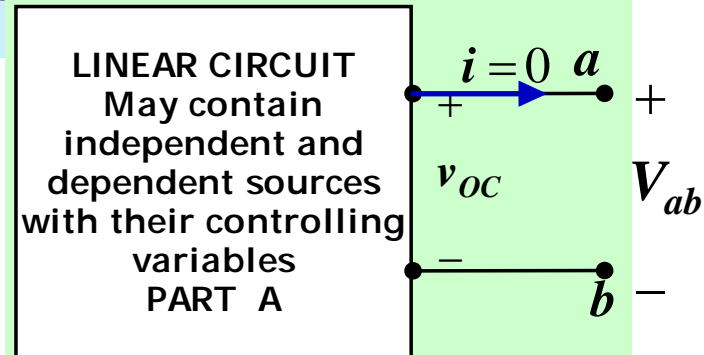

Second circuit problem

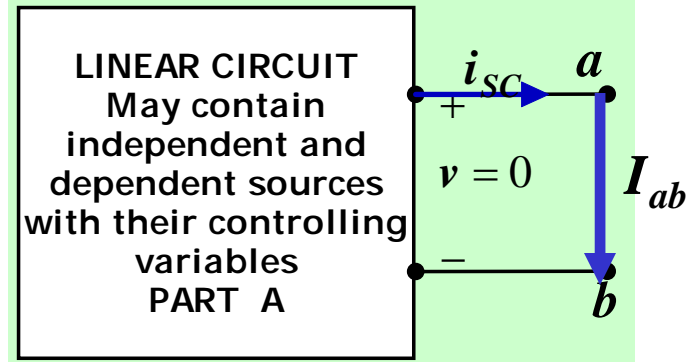

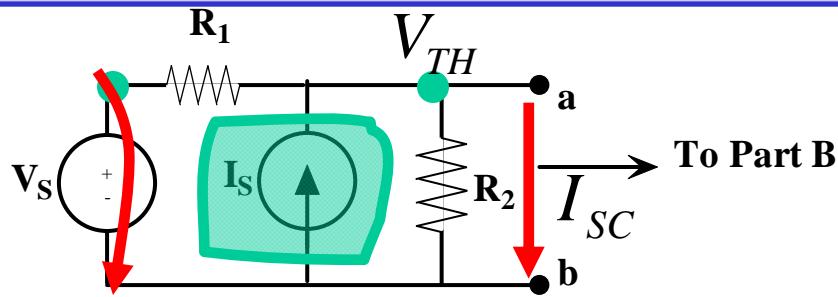AN EXAMPLE OF DETERMINING THE THEVENIN EQUIVALENT



Part B is irrelevant.

The voltage V_{ab} will be the value of the Thevenin equivalent source.

What is an efficient technique to compute the open circuit voltage?

Now for the short circuit current
Let's try source superposition

When the current source is open the current through the short circuit is

$$I_{SC}^1 = \frac{V_S}{R_1}$$

When the voltage source is set to zero, the current through the short circuit is

$$I_{SC}^2 = I_S$$

$$I_{SC} = I_S + \frac{V_S}{R_1}$$

To compute the Thevenin resistance we use

$$R_{TH} = \frac{V_{TH}}{I_{SC}}$$

For this case the Thevenin resistance can be computed as the resistance from a - b when all independent sources have been set to zero

$$\frac{V_{TH}}{R_2} + \frac{V_{TH} - V_S}{R_1} - I_S = 0$$

$$\left(\frac{1}{R_1} + \frac{1}{R_2}\right)V_{TH} = \frac{V_S}{R_1} + I_S$$

$$V_{TH} = \frac{R_2}{R_1 + R_2}V_S + \frac{R_1 R_2}{R_1 + R_2}I_S$$

$$V_{TH} = \frac{R_1 R_2}{R_1 + R_2} \left(\frac{V_S}{R_1} + I_S \right)$$




$$R_{TH} = \frac{R_1 R_2}{R_1 + R_2}$$

NODE ANALYSIS

Determining the Thevenin Equivalent in Circuits with Only INDEPENDENT SOURCES


The Thevenin Equivalent Source is computed as the open loop voltage

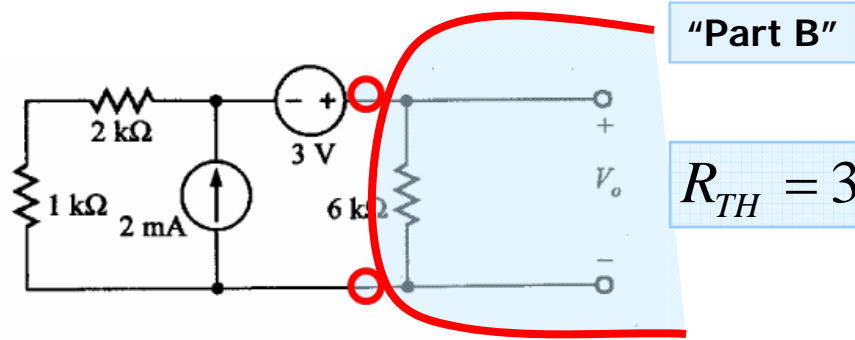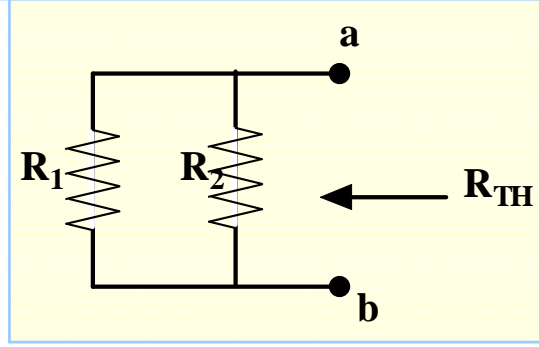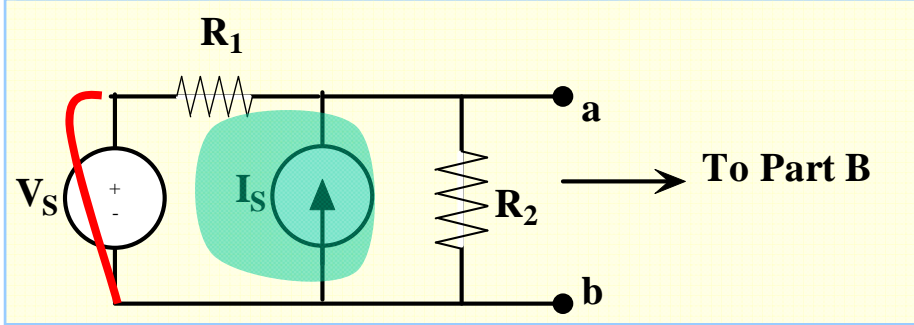The Thevenin Equivalent Resistance CAN BE COMPUTED by setting to zero all the sources and then determining the resistance seen from the terminals where the equivalent will be placed



$R_{TH} = 3k\Omega$




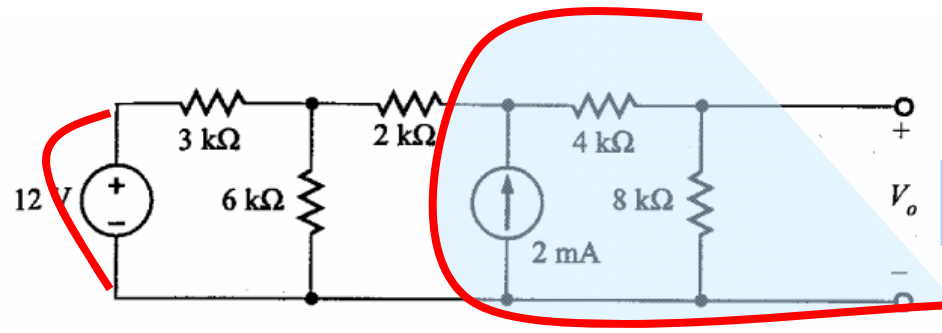
Since the evaluation of the Thevenin equivalent can be very simple, we can add it to our toolkit for the solution of circuits!!



$R_{TH} = 4k\Omega$

"Part B"

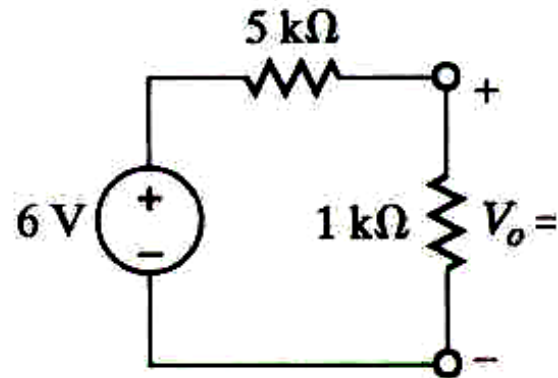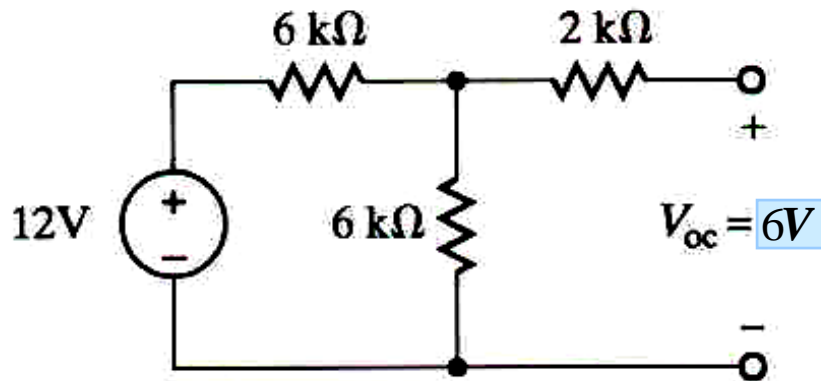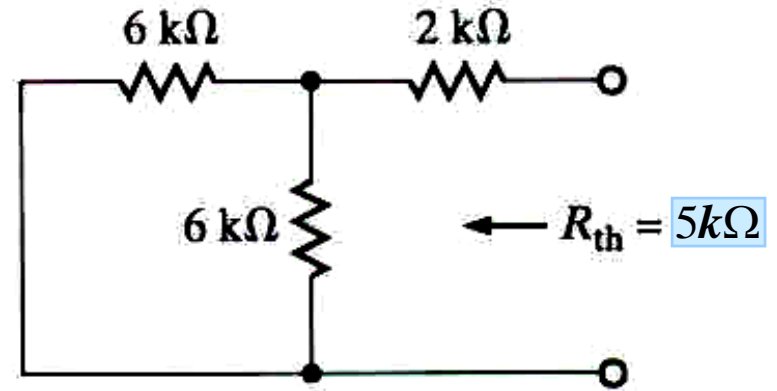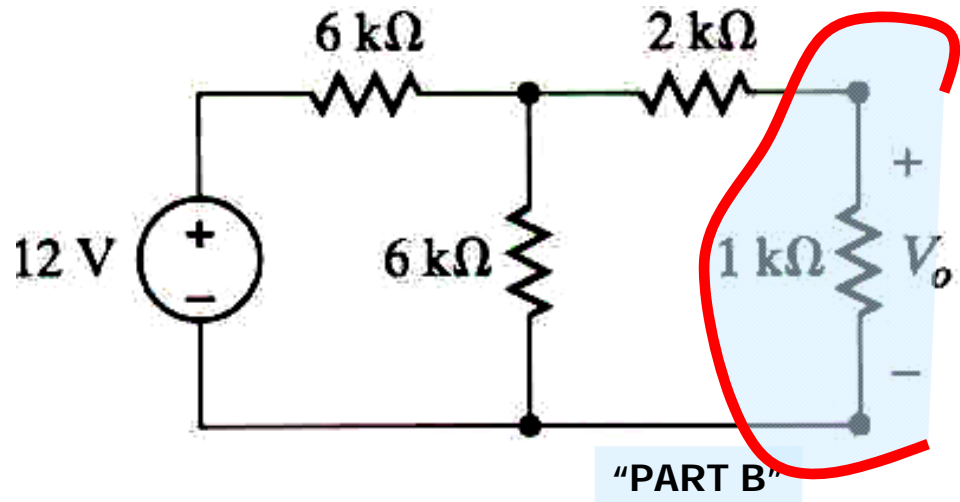
Find V_o in the following network using Thévenin's theorem.



$$V_o = \frac{1k}{1k + 5k} (6V) = 1[V]$$

EXAMPLE

COMPUTE V_o USING THEVENIN

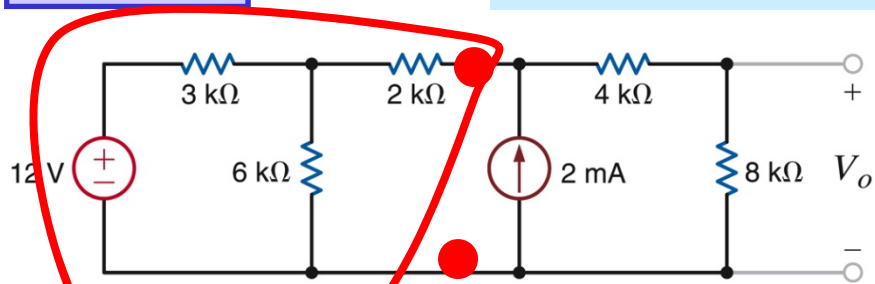

In the region shown, one could use source transformation twice and reduce that part to a single source with a resistor.

... Or we can apply Thevenin Equivalence to that part (viewed as "Part A")

$$R_{TH} = 4k\Omega$$

For the open loop voltage the part outside the region is eliminated


$$V_{TH} = \frac{6}{3+6} 12[V] = 8[V]$$

And one can apply Thevenin one more time!

For open loop voltage use KVL


$$V_{TH}^1 = 4k * 2mA + 8V = 16V$$

The original circuit becomes...

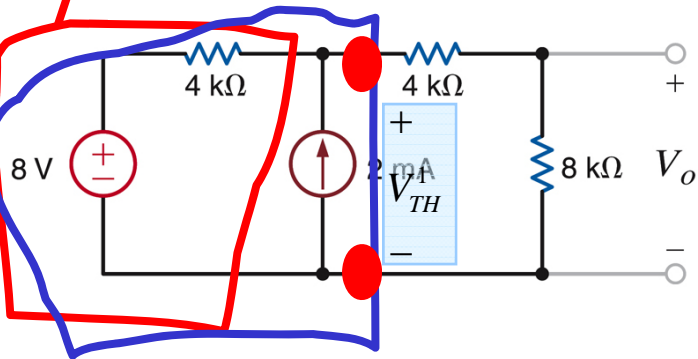

$$R_{TH}^1 = 4k\Omega$$


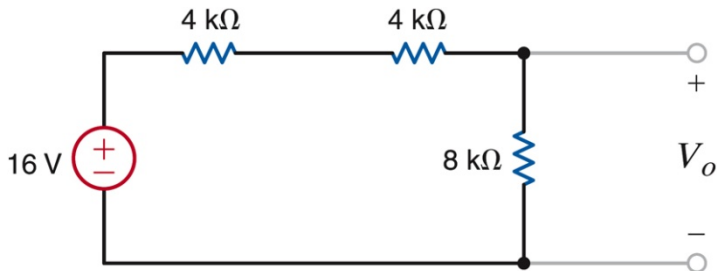
...and we have a simple voltage divider!!



$$V_o = \frac{8}{8+8} 16[V] = 8V$$

Or we can use Thevenin only once to get a voltage divider


For the Thevenin resistance

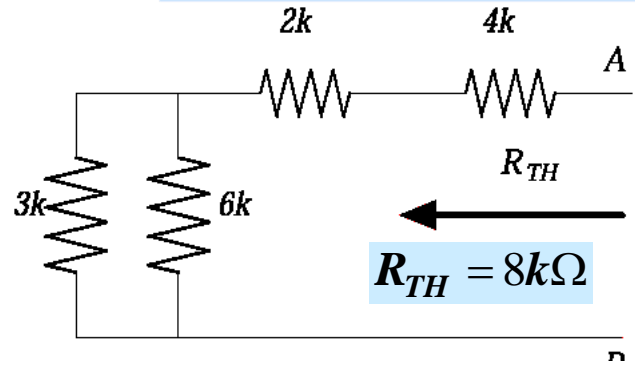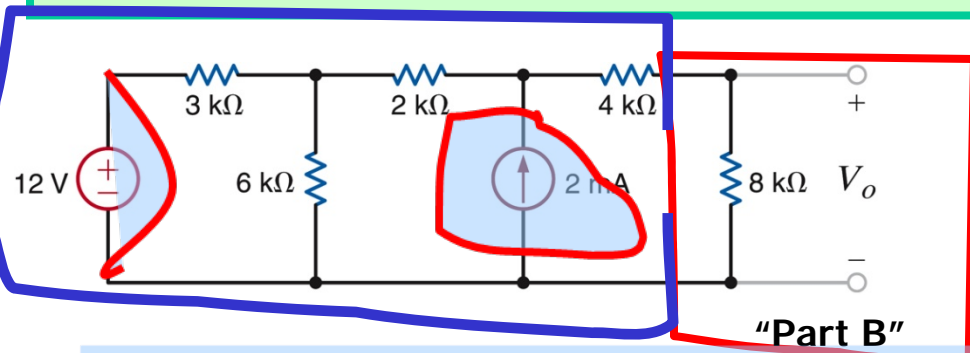

For the Thevenin voltage we have to analyze the following circuit

METHOD??

Source superposition, for example

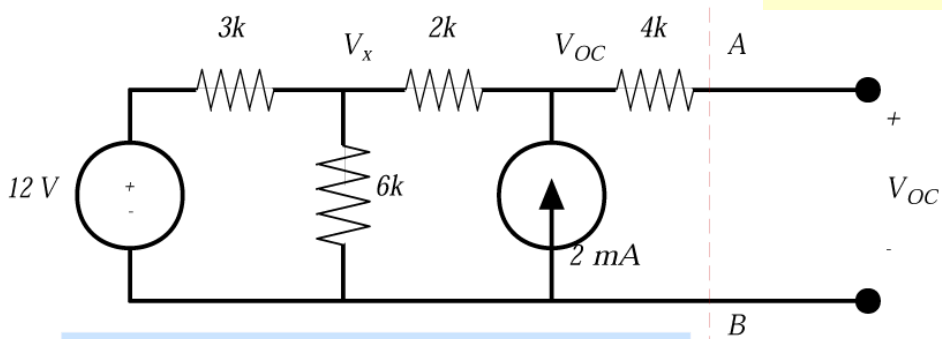

Contribution of the voltage source


$$V_{OC}^1 = \frac{6}{3+6} 12V = 8V$$

Contribution of the current source


$$V_{OC}^2 = (2k + 2k) * (2mA) = 8V$$

Thevenin Equivalent of "Part A"

Simple Voltage Divider

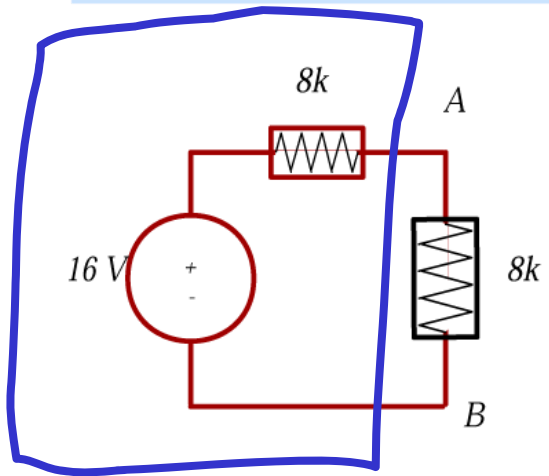


COMPUTE V_o USING NORTON

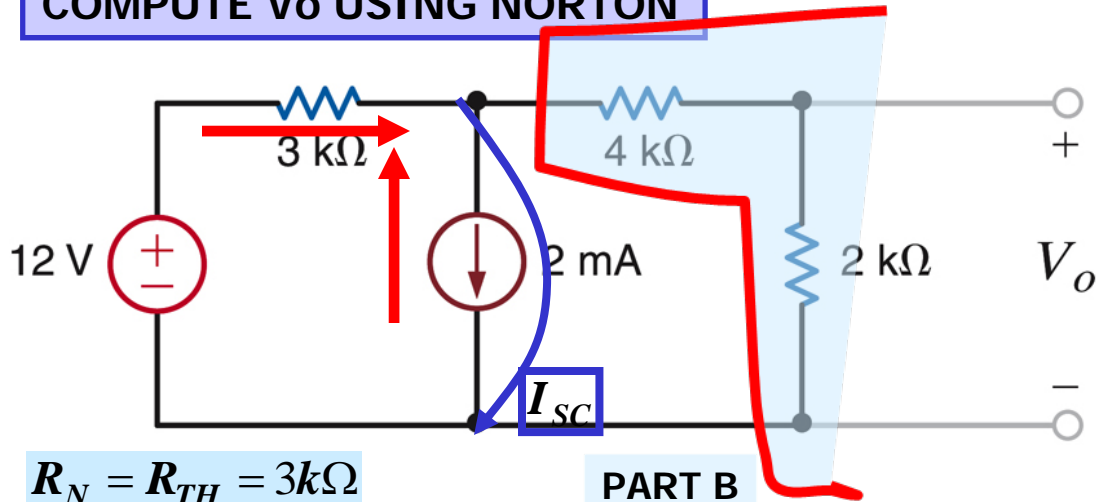

$$R_N = R_{TH} = 3k\Omega$$

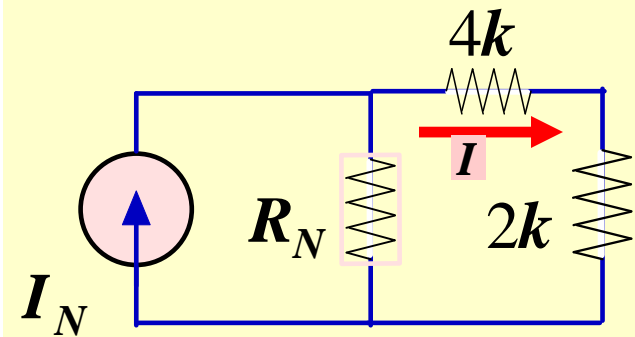
$$I_{SC} = I_N = \frac{12V}{3k} - 2mA = 2mA$$



$$V_o = 2kI = 2k \left(\frac{R_N}{R_N + 6k} I_N \right)$$


$$V_o = 2 \frac{3}{9} (2) = \frac{4}{3} [V]$$

COMPUTE V_o USING THEVENIN

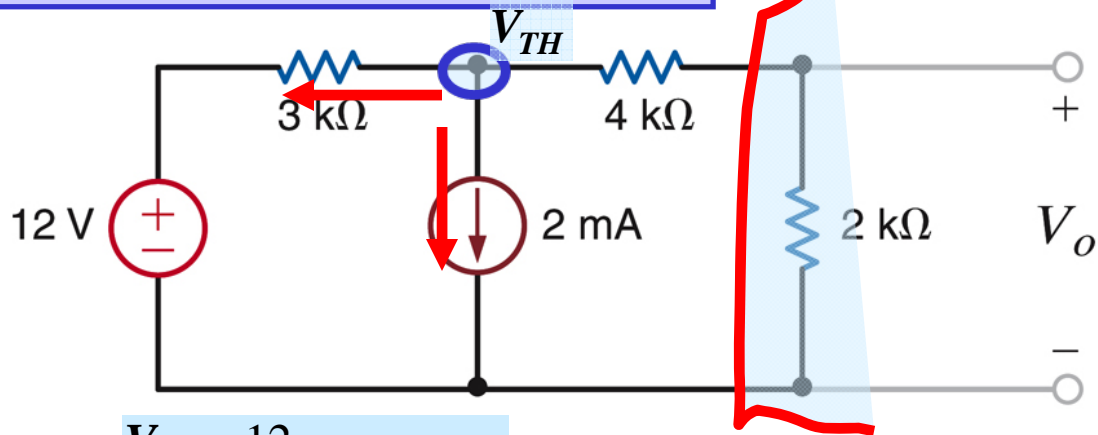

$$\frac{V_{TH} - 12}{3k} + 2mA = 0$$

$$R_{TH} = 3k + 4k$$

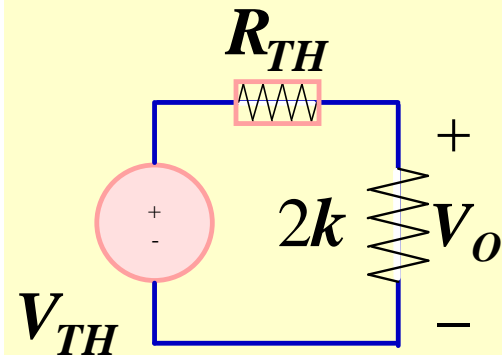


$$V_o = \frac{2}{2+7} (6V) = \frac{4}{3} [V]$$

MAXIMUM POWER TRANSFER

Courtesy of M.J. Renardson


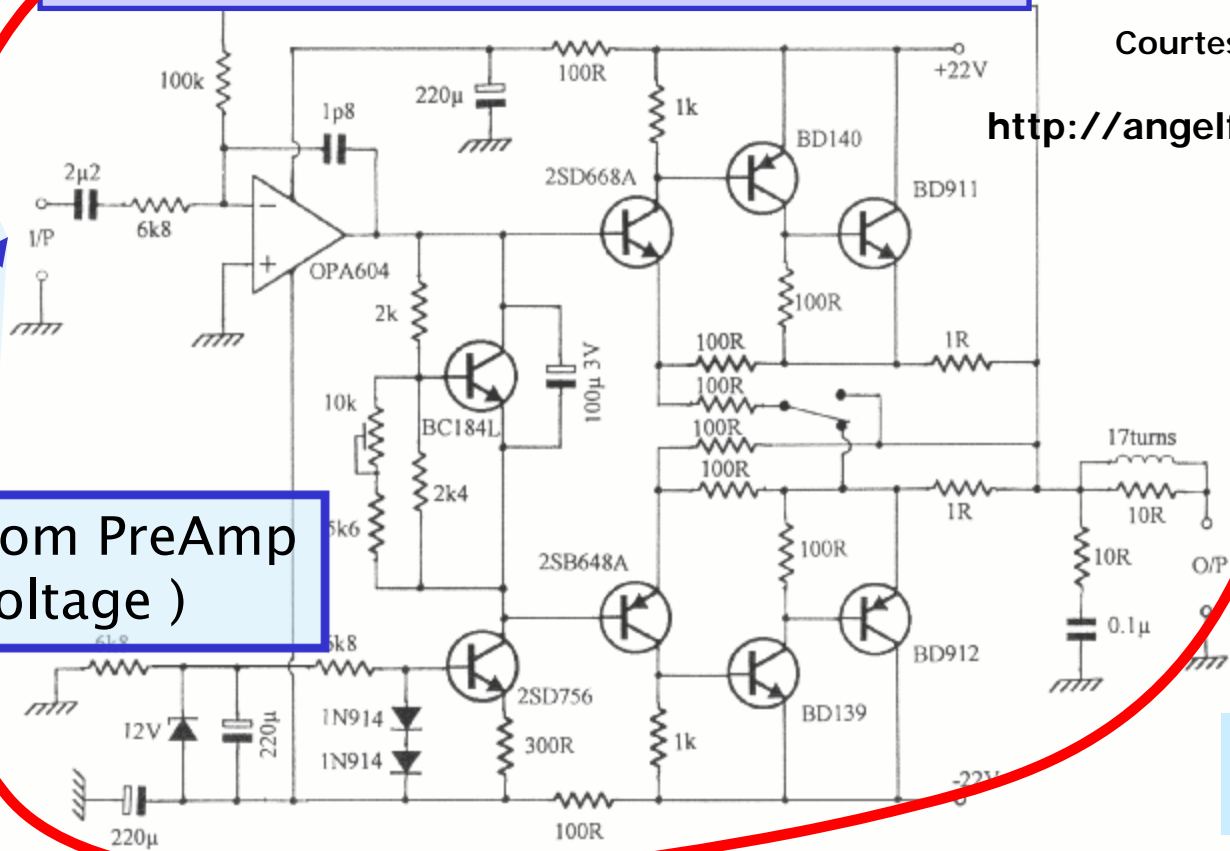
<http://angelfire.com/ab3/mjramp/index.html>



From PreAmp
(voltage)


To speakers

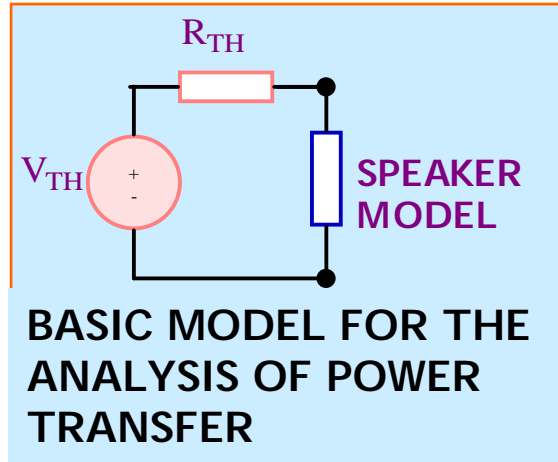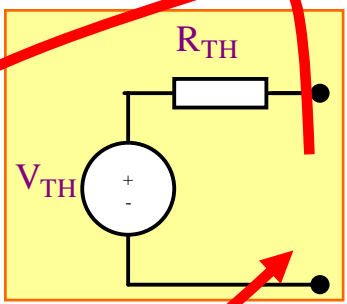The simplest model for a speaker is a resistance...



BASIC MODEL FOR THE ANALYSIS OF POWER TRANSFER

MAXIMUM POWER TRANSFER

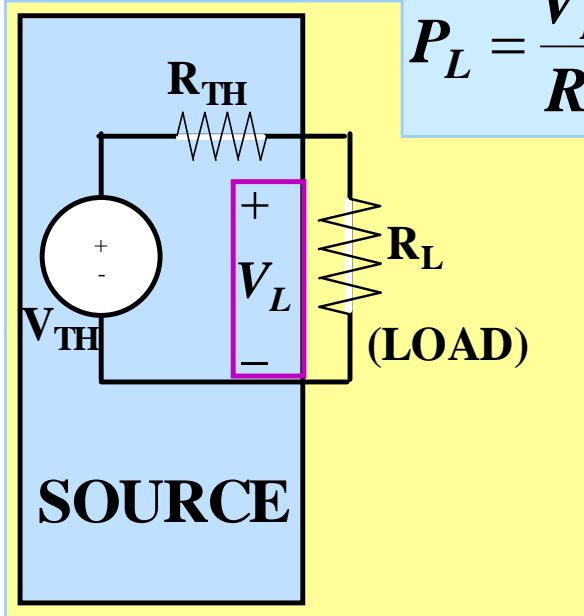

$$P_L = \frac{V_L^2}{R_L}; V_L = \frac{R_L}{R_{TH} + R_L} V_{TH}$$

$$P_L = \frac{R_L}{(R_{TH} + R_L)^2} V_{TH}^2$$

For every choice of R_L we have a different power. How do we find the maximum value?

Consider P_L as a function of R_L and find the maximum of such function

$$\frac{dP_L}{dR_L} = V_{TH}^2 \left(\frac{(R_{TH} + R_L)^{-2} - 2R_L (R_{TH} + R_L)^{-3}}{(R_{TH} + R_L)^4} \right)$$

Set the derivative to zero to find extreme points. For this case we need to set to zero the numerator

$$R_{TH} + R_L - 2R_L = 0 \Rightarrow R_L^* = R_{TH}$$

The maximum power transfer theorem

The value of the maximum power that can be transferred is

The load that maximizes the power transfer for a circuit is equal to the Thevenin equivalent resistance of the circuit.

$$P_L(\max) = \frac{V_{TH}^2}{4R_{TH}}$$

ONLY IN THIS CASE WE NEED TO COMPUTE THE THEVENIN VOLTAGE