 


# ELEC 3500: Assignment 4


Due on 6th Apr 2005 in class. Total marks: 20

- The state diagram shown below describes a synchronous FSM with inputs  $x$ ,  $y$  and  $z$ .  $z$  is a synchronous signal whereas  $x$  and  $y$  are asynchronous. Is there a problem with this design? If so, suggest a solution to the problem. 5 Marks




Ans: Make S2 and S6 differ by one bit; S3 and S4 differ by one bit; S6 and S5 differ by one bit.

 - Interface the gadget with the FSM shown in the following figure using debouncing. 3 Marks



Ans:

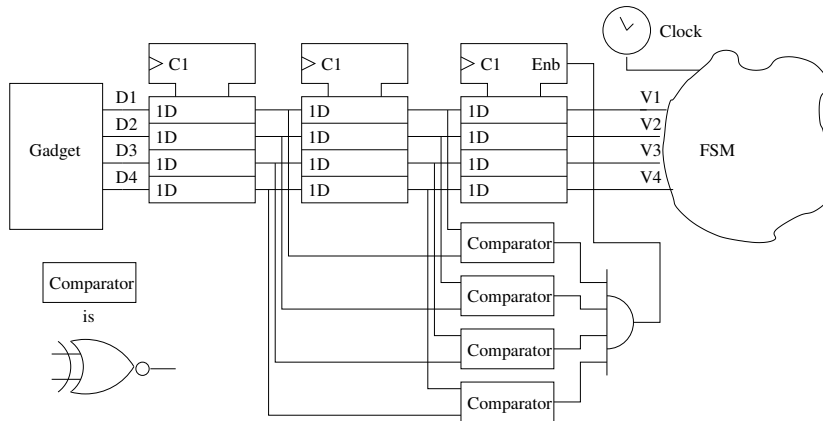


- Find the maximum delay in the clock buffers for the shift registers shown.  $t_{clk} = 10ns$

(a)

2 Marks

 $t_{CHQV} = 2ns$  max  
 $t_{hold} = 0ns$  min  
 For all flip-flops




Ans:  $t_{PD} \geq t_{hold} + t_{skew} - t_{CHQV} \implies 1 \geq 0 + t_{skew1-2} - 2$  and  $1 \geq 0 + t_{skew2-3} - 2$ . Hence,  $t_{skew1-2} \leq 3ns$  and  $t_{skew2-3} \leq 3ns$

(b)

2 Marks

 
$t_{CHQV} = 2ns$  max  
 $t_{hold} = 0ns$  min  
 For all flip-flops



Ans:  $t_{skew1-2} \leq t_{clk} = 1ns$  and  $t_{skew2-3} \leq t_{clk} = 1ns$

4. Find  $t_{PD(min)}$  and  $t_{PD(max)}$  in the following circuit.

4 Marks

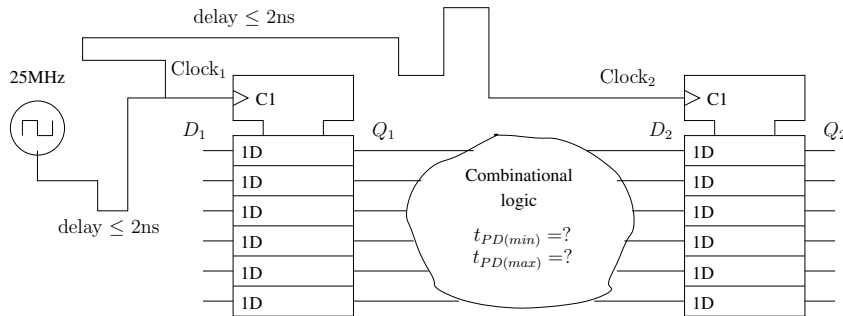

$|t_{skew}| \leq 2ns$   
 $t_{hold} = 1ns$  max  
 $t_{hold} = 0ns$  min  
 $t_{CHQV} = 3ns$   
 $t_{setup} = 3ns$

Ans:  $t_{PD(min)} = t_{hold} + |t_{skew}| - t_{CHQV}$  so  $t_{PD(min)} = 1 + 2 - 3 = 0ns$ .  $t_{PD(max)} = t_{clk} - |t_{skew}| - t_{setup} - t_{CHQV}$  so  $t_{PD(max)} = 40 - 2 - 3 - 3 = 32ns$

5. (a) An asynchronous signal is synchronized through a single D flip-flop before being fed directly to a flip-flop in a synchronous FSM. The system is clocked at a frequency of 20MHz and the average data frequency is 1MHz. The rise time of the data signal is 1ms. The setup time of the signal is 30ns and the  $\tau$  of the D latches is given to be 0.43ns. Calculate MTBF. 2 Marks

Ans:

$$MTBF = \frac{e^{T_J/\tau}}{K \cdot f_C \cdot f_D}$$

$K = 2t_{rise}$ ,  $T_J = T_{CLK} - T_{setup} = 50ns - 30ns = 20ns$ . MTBF can be evaluated to be  $3.96 \times 10^9$ .

- (b) In the above question instead of using one flip-flop for synchronization, two flip-flops are used for synchronization. In addition, a digital gate is introduced between the synchronization block and the FSM. The digital gate has a propagation delay of 10ns. Calculate MTBF. 2 Marks

Ans:

$T_J = 2T_{CLK} - T_{prop-delay} - 2T_{setup} = 2 * 50ns - 10ns - 2 * 30ns = 30ns$ . MTBF can be evaluated to be  $4.98 \times 10^{19}$ .