

October 23, 2012 10:05 AM –11:25 AM

R. Mason



answer all questions on the exam sheet provided, one 8.5 x 11 crib sheet allowed

1. (5 points) multiple choice, circle the **BEST** answer.

- (a) A three input NOR gate with input values of “1”, “X” and “Z” would have an output value of ?
 - i) “Z”
 - ii) “0”
 - iii) “1”
 - iv) “X”
- (b) Verilog code of the form **always @(school)** could synthesize to:
 - i) a latch
 - ii) a flip-flop
 - iii) a class
 - iv) a clock
- (c) What is the typical hold time of a CMOS flip-flop:
 - i) -0.5nS
 - ii) 0.5nS
 - iii) 1uS
 - iv) -1uS
- (d) Which transistors changes will decrease the output delay of a CMOS inverter:
 - i) increase $|V_T|$, increase W
 - ii) increase $|V_T|$, decrease W
 - iii) decrease $|V_T|$, increase W
 - iv) decrease $|V_T|$, decrease W
- (e) A case statement should have a default case to:
 - i) make all cases mutually exclusive
 - ii) to prevent a synchronous reset
 - iii) to prevent unwanted latches
 - iv) make a stronger case

2. (10 points) Answer the following:

  - (a) Draw the expected output waveform for Q in the following circuit with the given signals for D and CLK (assume setup and hold times are 0).



(b) Draw a gate level (i.e. AND, OR, etc.) schematic for the hardware that would be produced from the following Verilog behavioral code? Is there anything wrong with this code?

```

module midterm(a, b, c);
input [3:0] a;
input b;
output [7:0] c;
register [7:0] c;
always @ (a)
begin
c = 0;
if (b) begin
case (a)
4'b0000 : c = 8'h01;
4'b0001 : c = 8'h02;
4'b0010 : c = 8'h04;
4'b0011 : c = 8'h08;
4'b0100 : c = 8'h10;
4'b0101 : c = 8'h20;
4'b0110 : c = 8'h40;
endcase
end
end
endmodule

```


(c) A CMOS inverter has $V_{OH}=0.8V$, $V_{OL}=0.1V$, $V_{IH}=0.6V$, $V_{IL}=0.4V$. Calculate the noise margins for this circuit. What would happen to the output if the input to this circuit was at 0.5V?

$NM_L = \underline{\hspace{2cm}} V$

If input = 0.5V , output = $\underline{\hspace{2cm}}$

$NM_H = \underline{\hspace{2cm}} V$

 (d) Complete the complex CMOS gate below by adding the require NMOS transistors. Write the logic equation for the completed circuit (i.e. $Z = ?$)



(e) Write a COMPLETE (including module statement etc.) verilog module using BEHAVIOURAL code to implement an 10-to-1 multiplexer (i.e. 10 input, 1 output and 4 select lines)

3. (5 points) A 2.0V supply voltage, FIVE input CMOS NAND gate has transistors with the following characteristics: $W_P=2\mu\text{m}$, $W_N=2\mu\text{m}$, $L=0.2\mu\text{m}$, $k_p'=50\mu\text{A}/\text{V}^2$, $k_n'=100\mu\text{A}/\text{V}^2$, $V_T=0.5\text{V}$, $\lambda=0$. Where k_p' and k_n' are the process gains and W_P and W_N are the transistor widths for PMOS and NMOS transistors respectively. If the gate has an output load capacitance of 0.1pF and assuming all transistors are in saturation mode, calculate (a) worst case rising delay, (b) worst case falling delay, (c) resize the NMOS transistor widths (keeping all NMOS transistors with the same width) so that the worst case falling delay is equal to the worst case rising delay (d) calculate the dynamic power dissipation when the output is toggling at 100 MHz.

(a) _____ ns

(b) _____ ns

(c) _____ μm

(d) _____ μW

$$I_d = \frac{1}{2} k' \frac{W}{L} (V_{gs} - V_t)^2 (1 - \lambda V_{ds}) \quad D = \frac{CV_{dd}}{2I} \quad P = CV_{dd}^2 f$$