

Sample Midterm Exam
MidDay, MidMonth, MidYear
ELEC4708: Advanced Digital Electronics
Department of Electronics, Carleton University

Instructor: Maitham Shams
Booklets: None
Aids Allowed: Calculator

Exam Duration: 1 hour
Number of Pages: 4 with this
Number of Students: MidNumber

Last Name: _____
First Name: _____
ID: _____

| Q1 | Q2 | Q3 | Q4 | Total |
|-----|----|-----|-----|-------|
| /10 | /5 | /20 | /15 | /50 |

-
- Write your name and ID number clearly on all pages. No questions answered.
 - Attempt all questions. Marking scheme for all questions are given.
 - If in a question you are asked to make an assumption, then you must use it.
 - Formula

$$\hat{D} = NF^{\frac{1}{N}} + P, \quad F = GBH, \quad \hat{f} = F^{\frac{1}{N}}, \quad H = \frac{C_{out}}{C_{in}}$$

$$f = gh, \quad b = \frac{C_{onpath} + C_{offpath}}{C_{onpath}}, \quad G = \Pi g_i, \quad P = \Sigma p_i$$


- Data

$$V_{DD} = 1.8 \text{ v}, \quad V_{tn} = 0.4 \text{ v}, \quad V_{tp} = 0.5 \text{ v}$$

[1] (10 marks, 1 marks each) Mark True or False.

 
1. Body (substrate) of PMOS transistors are usually grounded. True False
2. A CMOS transmission gate consists of a PMOS and an NMOS transistor connected in parallel. True False
3. Stick diagrams may be used to estimate the area of logic gates. True False
4. Using only the true (not inverted) inputs, it is impossible to implement a CMOS non-inverting logic gate in one stage. True False
5. An ideal flip-flop is never transparent. True False
6. In modern CMOS IC technologies diffusion capacitances are much smaller than gate-oxide capacitances. True False
7. In modern CMOS digital circuits electron velocity doesn't saturate. True False
8. MOS threshold voltage is independent of source-body potential. True False
9. In modern CMOS digital circuits junction leakage current is less than subthreshold leakage current. True False
10. CMOS circuits operate faster at lower temperatures. True False

[2] (5 marks) Obtain the steady-state voltages at the nodes of the following circuit. All capacitances are 0.1 pF each and all the transistors have $W/L = 3$.



- $V_A =$
- $V_B =$
- $V_C =$
- $V_D =$
- $V_E =$

 [3] (20 marks) Consider the following circuit. The inverter has an input capacitance of 6 units (i.e. twice as large as the unit inverter). The output capacitance is 345.6 units.



- Calculate the minimum possible delay for the circuit, if the delay of a unit inverter is 15 ps in this technology.

- Find the size of all unknown PMOS and NMOS transistors in the circuit.

[4] (15 marks) Implement the following function in conventional CMOS. Assume that both the true and inverted inputs are available. If there are more than one possible implementations, do the one that imposes less capacitive load at the output, i.e., faster.

- $Z = \overline{A(B + C) + \bar{D}E}$

- Size the transistors such that the logic gate is equivalent (in resistance and current) to a unit inverter (i.e. $W_p/L_p = 2$ and $W_n/L_n = 1$). If there are more than one way of sizing, do the one that results in a faster circuit.
- If the output diffusion capacitance of a unit inverter is 12 fF, calculate the energy dissipation at the output Z .
- How much power do you save by operating with a power supply of 1.2 v instead of 1.8 v.