

# Frequency System ARCHITECTURE and DESIGN

JOHN W. M. ROGERS  
CALVIN PLETT  
IAN MARSLAND




## RF Systems Course: PLL Lecture I

# Basic Phase Locked Loop (PLL) Operation

- Many ways to make a freq synthesizer, but PLL based is very common.
- Can have either integer N or frac N but most of this lecture will work for both.
- Integer N is simpler, so we start with it.
- PLL is a feedback system compares phase of a reference to phase of divided down VCO signal.
- Feedback forces these signals to be equal.

$$f_o = N \cdot f_{\text{ref}}$$

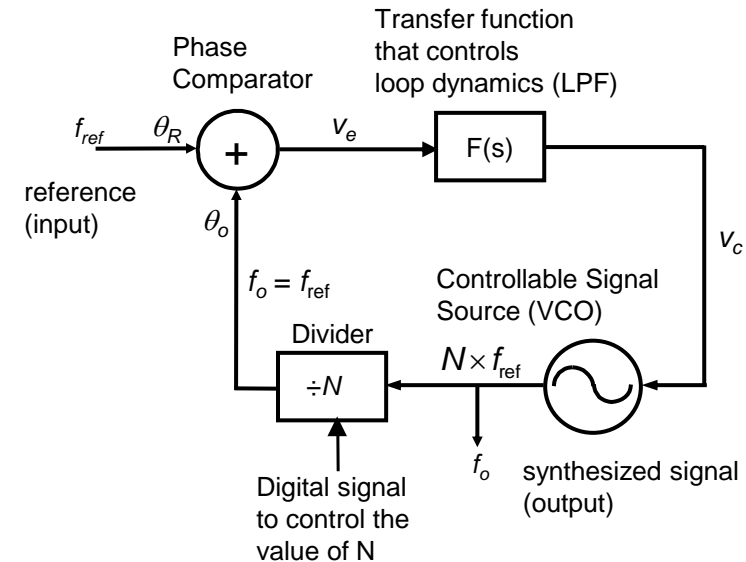- We use phase so no finite freq error.
- Reference is a quartz crystal
- very accurate, but can't make at high freq or make tunable.



# PLL Components VCOs and Dividers

- VCO has an output freq which depends on an input voltage.
- Generally we assume it is linear but really it never is.


$$\omega_o = \omega_{\text{nom}} + \omega_{\text{VCO}} = \omega_{\text{nom}} + K_{\text{VCO}}v_c$$

- Since phase and freq are related by  $\omega = \frac{d\theta}{dt}$
- We note that  $\theta_{\text{VCO}} = \int \omega_{\text{VCO}} dt = K_{\text{VCO}} \int_0^t v_c(\tau) d\tau$

- We will do a lot of analysis in Laplace domain so:

$$\frac{\theta_{\text{VCO}}(s)}{v_c(s)} = \frac{K_{\text{VCO}}}{s}$$

 - For a divider we also note that:  $\frac{\theta_o}{v_c} = \frac{1}{N} \cdot \frac{K_{\text{VCO}}}{s}$





# PLL Components: Phase Detectors

- Phase detector produces output proportional to phase difference of two input signals.

$$v_e(s) = K_{\text{phase}} (\theta_R(s) - \theta_o(s))$$

 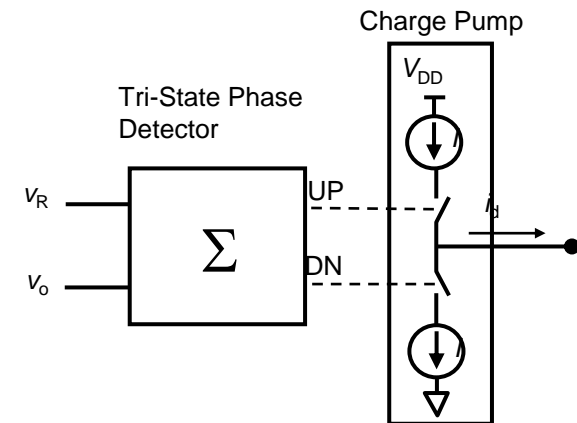- equation is linear -> may not hold over all phase differences.
- Typical tri-state phase detector shown at the right.
- It responds to rising edges that cause it to change state and produce UP and DN signals that control two current sources.



# PLL Components: Phase Detectors


- If a rising edge of  $v_o$  is received  $\rightarrow$  VCO too fast  $\rightarrow$  DN pulse generated until  $v_r$  arrives.
- If a rising edge of  $v_r$  is received  $\rightarrow$  VCO too slow  $\rightarrow$  UP pulse generated until  $v_o$  arrives.
- If currents have a value of  $I$  then average output current is:

$$i_d = I \frac{\tau}{T} = \left( \frac{I}{2\pi} \right) (\theta_R - \theta_o)$$

- phase detector gain is:



$$K_{\text{phase}} = \frac{I}{2\pi}$$

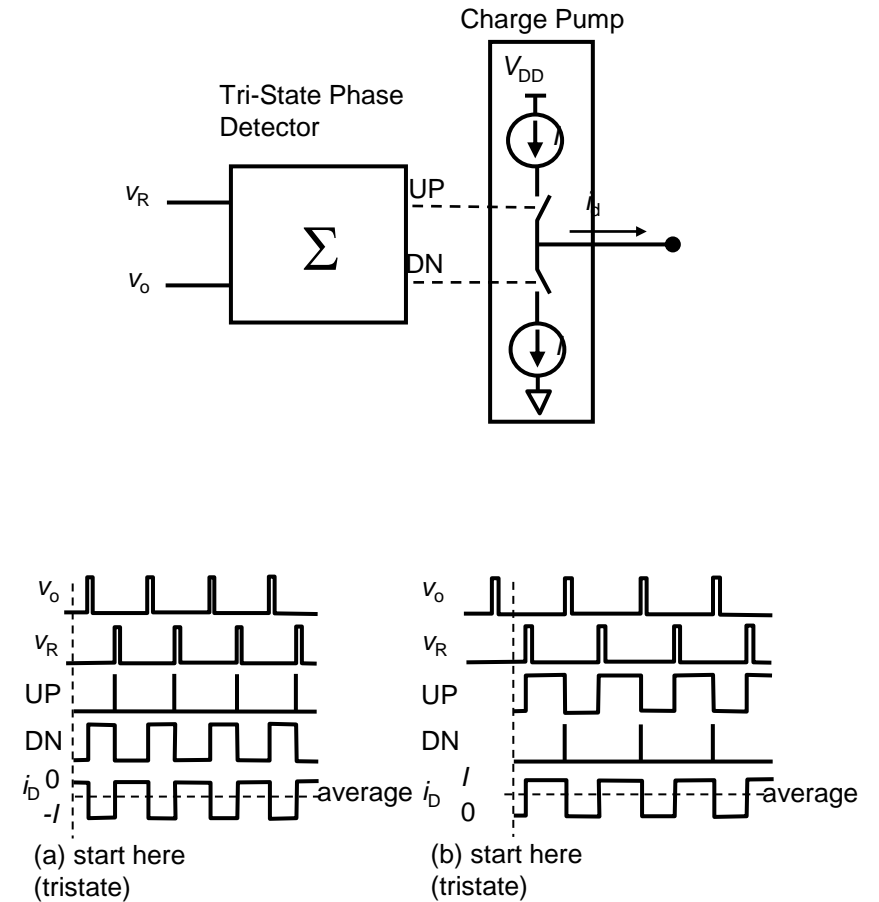- Note responds to edges so waveform shape not that important.


  
# PLL Components: Phase Detectors

- Note that for every given phase difference there is always two interpretations depending on when phase detector was started.
- Also note that phase detector is only linear for a limited range after which there is a nonlinear event!
- What if signals are at two different freqs?
- Turns out it will act like a freq detector as well no matter where you start it.
- Output will then push VCO in the right direction to try and make freqs equal.




# PLL Components: The Loop Filter

- Loop filter typically an RC network that accepts current as input and produces voltage as output.
- transfer function is an impedance
- For typical filter shown at the right:

$$Z = R + \frac{1}{sC_1}$$



- Therefore the output can be found as

$$v_c = Zi_d$$

 
  
# PLL Components: The Loop Filter

- Often to provide more attenuation at higher freqs 2<sup>nd</sup> cap is added that is much smaller than  $C_1$
- With that cap freq response of filter is plotted below:





# Continuous-Time Analysis of PLLs

- We now have s domain eqs for all the blocks that make up the system.

- Assuming that:  $F(s) = R + \frac{1}{sC_1} = \frac{sC_1R + 1}{sC_1}$

- transfer function for the loop is:


$$\frac{\theta_o}{\theta_R} = \frac{\frac{IK_{VCO}}{2\pi \cdot N} \left( R + \frac{1}{sC_1} \right)}{s + \frac{IK_{VCO}}{2\pi \cdot N} \left( R + \frac{1}{sC_1} \right)} = \frac{\frac{IK_{VCO}}{2\pi \cdot NC_1} (RC_1s + 1)}{s^2 + \frac{IK_{VCO}}{2\pi \cdot N} Rs + \frac{IK_{VCO}}{2\pi \cdot NC_1}}$$

This system has a natural freq and damping constant:

$$\omega_n = \sqrt{\frac{IK_{VCO}}{2\pi \cdot NC_1}} \quad \zeta = \frac{R}{2} \sqrt{\frac{IK_{VCO}C_1}{2\pi \cdot N}}$$

This can also be written as:
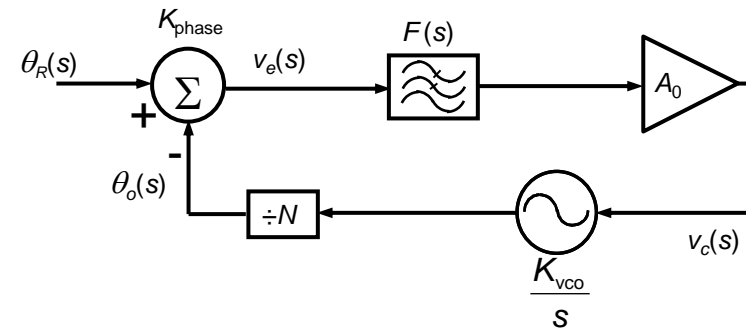
$$C_1 = \frac{IK_{VCO}}{2\pi \cdot N\omega_n^2} \quad R = 2\zeta \sqrt{\frac{2\pi \cdot N}{IK_{VCO}C_1}} = \zeta \frac{4\pi \cdot N\omega_n}{IK_{VCO}}$$




- Sometimes it is more useful to have an eqn for control voltage because that is what we can see easily in simulation:

$$\frac{V_C}{\omega_R} = \frac{N\omega_n^2 \left( \frac{2\zeta}{\omega_n} s + 1 \right)}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$


 
# Continuous-Time Analysis of PLLs

- freq response of loop.
- below the natural freq, loop has gain and output phase will track input phase as intended.
- Above natural freq, loop has less and less effect so more and more the phase of the VCO has no relationship to the phase of the reference.



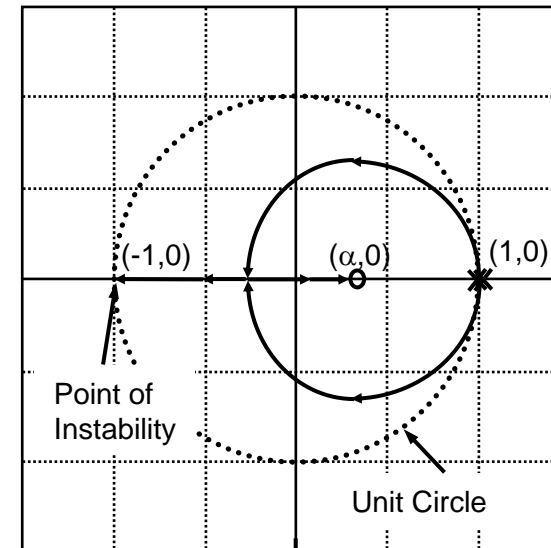
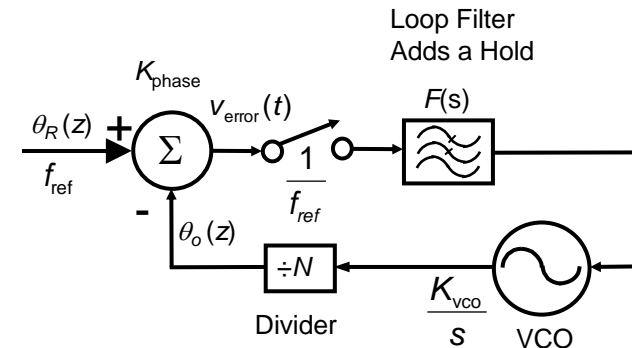
# Discrete Time Analysis for PLL

- model of a PLL in s domain breaks down if things start changing at a significant fraction of reference freq.
- Since loop only “updates” once every reference period, in order for it to approximate continuous behaviour not much can change over that interval.
- This is guaranteed by choosing a loop BW which is small fraction (less than  $1/10^{\text{th}}$ ) of the reference freq.
- If we fail to do this, loop can become unstable even if s domain poles are all in left hand plane.
- There is some detailed analysis in the book which isn't that important for the RF systems course.


  
# Transient Behavior of PLLs

- We can take inverse Laplace transform of previous loop eqns to get eqns for transient response.
- eqns are given in the book and results are plotted on the right.
- Note phase always returns to zero (there are 2 integrators in the loop) while control voltage settles to a new normalized value as expected.
- This is a linear response and only holds if phase detector and other components remain well modeled by their linear eqns.



# Example of Limits of Theory So Far

- Assume damping const. = 0.707, 3dB BW = 150kHz.
- What is max freq step at input such that theory will still work? How long to settle under this condition?

$$\omega_n \approx \frac{\omega_{3dB}}{(1 + \zeta\sqrt{2})} = \frac{2\pi \cdot 150kHz}{2} = 2\pi \cdot 75kHz$$


- max normalized phase error is 0.46 so max phase error is:

$$\theta_{e\_max} = 0.46 \frac{\Delta\omega}{\omega_n}$$

- max phase error that PFD can withstand is  $2\pi$
- Largest freq step system can handle is:

$$\Delta\omega_{max} = \frac{\theta_{e\_max}\omega_n}{0.46} = \frac{2\pi(2\pi \cdot 75kHz)}{0.46} = \frac{6.43Mrad}{s} = 1.02MHz$$

 
- If freq step bigger than this, PLL will lose lock and cycle slip.
- Trans resp will look different than shown.
- Here will take till  $\omega_n t = 7$  for PLL to settle or  $14.9\mu s$ .


 
# Nonlinear Transient Behaviour

- If a larger freq step is experienced PLL will “cycle slip” and have to re-acquire lock.
- In this case PFD will push VCO back in the right direction but it will be operating as a freq detector for a while.
- If we assume that CP is on roughly half the time:  $\frac{\Delta v_C}{\Delta t} = \frac{I}{2C_1}$

- Solving for settling time:  $\frac{\Delta v_C}{\Delta t} = \frac{I}{2C_1}$





Some more math equivalents yields:

$$T_s = \frac{2C_1 \Delta \omega N}{IK_{VCO}} = \frac{\Delta \omega}{\pi \omega_n^2}$$

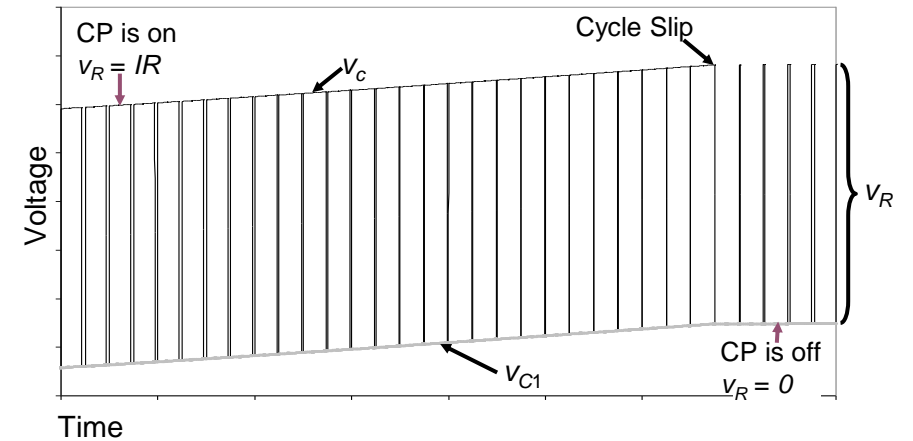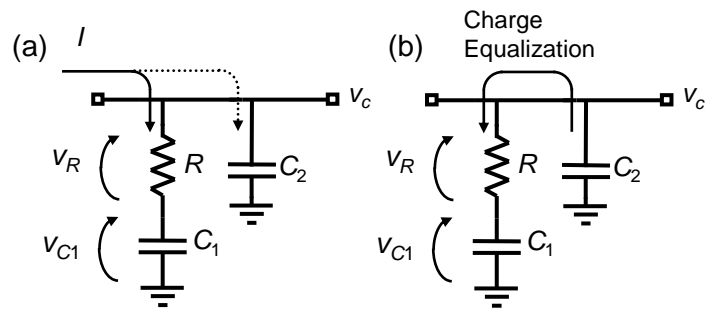
# Nonlinear Transient Behaviour

- PLL will have 2 modes (CP on) means current is being pushed onto  $C_1$  and  $C_2$ , and CP off where charge equalization happens between the 2 caps.
- At cycle slip CP goes from being on almost all the time to off almost all the time.


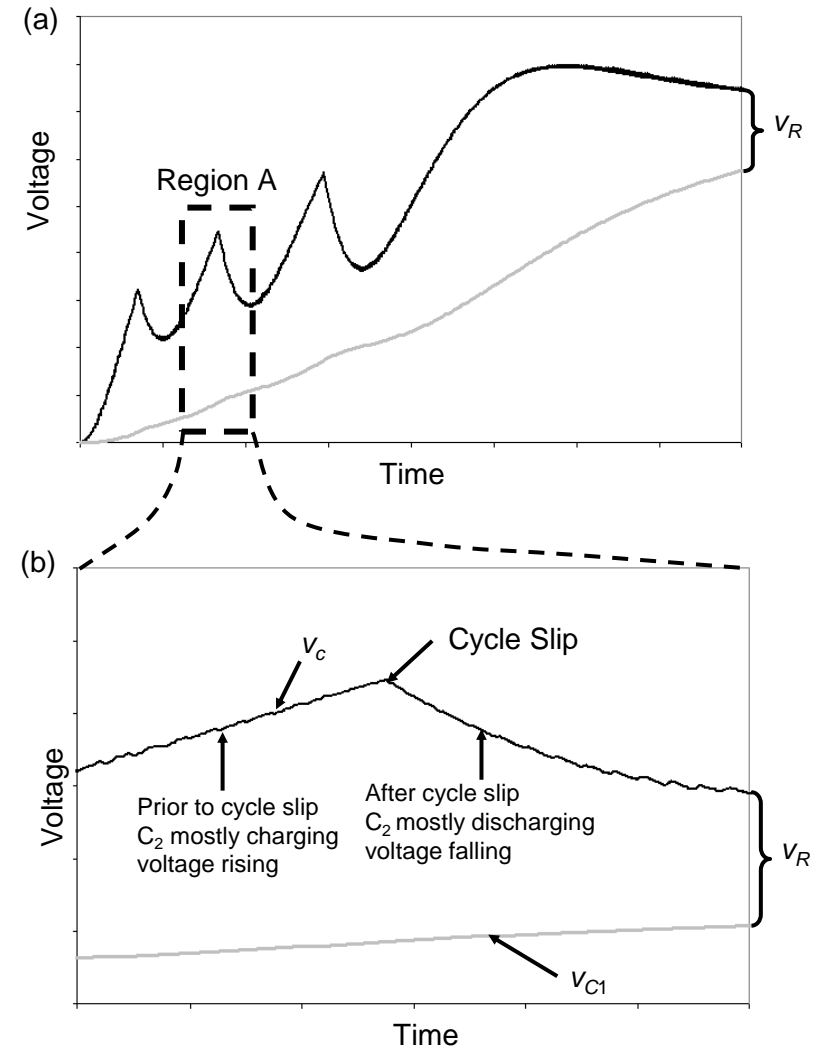
# Nonlinear Transient Behaviour

- This is a more zoomed out look at a PLL that is acquiring lock.
- looking at the loop filter voltage.
- There are three cycle slips in the example.
- $C_2$  “smooths out” the behaviour so voltages don’t try and change instantly.





# Example of Estimation of Settling Times

- 3.7-4.3GHz synth with step size of 1MHz
- 40MHz XTAL, CP with  $2\pi \cdot 100\mu\text{A}$  of output current, VCO with 3V supply are available
- Design frac N synth with loop BW = 150kHz
- Estimate settling time for 30MHz and 300MHz freq step.
- VCO operating with 3V supply must have 600MHz tuning range  $\rightarrow K_{\text{VCO}} \sim 200\text{MHz/V}$ .
- For CP  $K_{\text{phase}} = 100\mu\text{A/rad}$
- VCO freq 4GHz, reference freq 40MHz  $\rightarrow$  division ratio 100.
- 3dB freq of 150kHz for loop requires natural freq of 75kHz.

$$C_1 = \frac{IK_{\text{VCO}}}{2\pi \cdot N\omega_n^2} = \frac{2\pi \cdot 100\mu\text{A} \cdot (2\pi \cdot 200\text{MHz/V})}{2\pi \cdot 100(2\pi \cdot 75\text{kHz})^2} = 5.66\text{nF}$$


- Need damping const.  $\rightarrow$  choose 0.707

$$R = 2\zeta \sqrt{\frac{2\pi \cdot N}{IK_{\text{VCO}}C_1}} = \left(\frac{2}{\sqrt{2}}\right) \sqrt{\frac{2\pi \cdot 100}{2\pi \cdot 100\mu\text{A} \left(2\pi \cdot \frac{200\text{MHz}}{\text{V}}\right) \cdot 5.66\text{nF}}} = 530\Omega$$


- Set  $C_2 = 566\text{pF}$  ( $1/10^{\text{th}}$   $C_1$ )
- Output freq step of 30MHz and 300MHz corresponds to input step of 0.3MHz and 3MHz.
- From previous example can tolerate 1MHz input step without cycle slip.
- So for 30MHz step expect  $15\mu\text{s}$  as before.
- 2<sup>nd</sup> case will have cycle slip so acquisition time is:

$$T_s = \frac{\Delta\omega}{\pi\omega_n^2} = \frac{2\pi \cdot 3\text{MHz}}{\pi(2\pi \cdot 75\text{kHz})^2} = 27\mu\text{s}$$

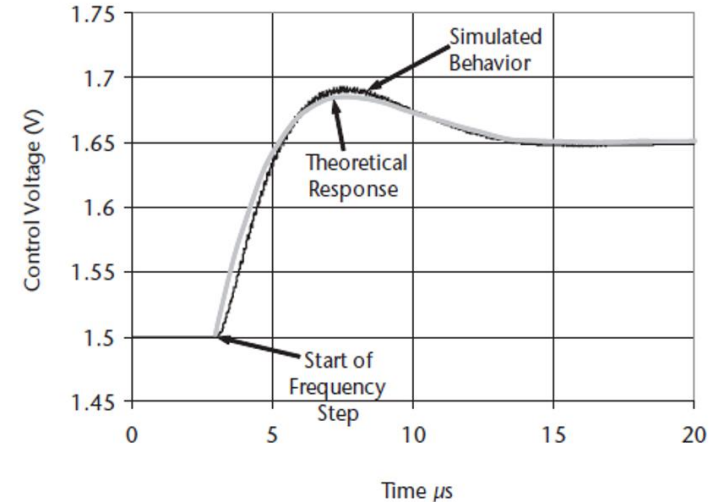- Complete settling will be  $27\mu\text{s}$  plus  $15\mu\text{s}$  for phase lock.
- Can simulate this with a circuit simulator using behavioural blocks.



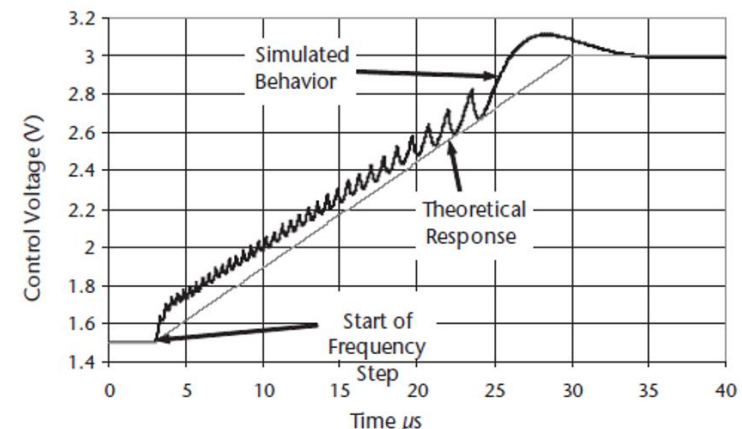Response of the PLL design's control voltage during a 30-MHz frequency step.



Response of the PLL design's control voltage during a 300-MHz frequency step.

# Various Noise Sources in PLLs

- VCO noise  $\varphi^2_{\text{VCO}}(\Delta\omega) = \frac{C}{\Delta\omega^2} + D$

- Crystal reference noise

$$\varphi^2_{\text{XTAL}}(\Delta\omega) = 10^{-16\pm 1} \cdot \left[ 1 + \left( \frac{\omega_0}{2\Delta\omega \cdot Q_L} \right)^2 \right] \left[ 1 + \frac{\omega_c}{\Delta\omega} \right]$$

- Frequency divider noise


$$\varphi^2_{\text{Div\_Added}}(\Delta\omega) \approx \frac{10^{-14\pm 1} + 10^{-27\pm 1} \omega_{\text{do}}^2}{2\pi \cdot \Delta\omega} + 10^{-16\pm 1} + \frac{10^{-22\pm 1} \omega_{\text{do}}}{2\pi}$$

- Phase detector noise

- Charge pump noise  $\varphi^2_{\text{PD}}(\Delta\omega) \approx \frac{2\pi \cdot 10^{-14\pm 1}}{\Delta\omega} + 10^{-16\pm 1}$

- Loop filter noise
 
$$i_{n\_LPF} = \frac{1}{R} \cdot \frac{v_n s}{s + \frac{C_1 + C_2}{C_1 C_2 R}} \approx \frac{1}{R} \cdot \frac{v_n s}{s + \frac{1}{C_2 R}}$$



- $\Sigma\Delta$  noise

$$\frac{\varphi^2_{\Sigma\Delta}(f) [\text{rad}^2/\text{Hz}]}{2} = \frac{(2\pi)^2}{24 f_r} \cdot \left[ 2 \sin\left(\frac{\pi f}{f_r}\right) \right]^{2(m-1)}$$

$$PN_{\Sigma\Delta}(f) [\text{dBc}/\text{Hz}] = 10 \log \left\{ \frac{(2\pi)^2}{24 f_r} \cdot \left[ 2 \sin\left(\frac{\pi f}{f_r}\right) \right]^{2(m-1)} \right\}$$

# In Band and Out of Band Noise

- Whether noise is LPF or HPF depends on where in the loop it is injected. Most noise is LPF:


$$\frac{\varphi_{\text{noiseout}}(s)}{\varphi_{\text{noiseI}}(s)} = \frac{\frac{IK_{\text{VCO}}}{2\pi \cdot C_1}(1 + RC_1s)}{s^2 + \frac{IK_{\text{VCO}}}{2\pi \cdot N}Rs + \frac{IK_{\text{VCO}}}{2\pi \cdot NC_1}}$$

- VCO noise is HPF:

$$\frac{\varphi_{\text{noiseout}}(s)}{\varphi_{\text{noiseII}}(s)} = \frac{s^2}{s^2 + \frac{IK_{\text{VCO}}}{2\pi \cdot N}Rs + \frac{IK_{\text{VCO}}}{2\pi \cdot NC_1}}$$

- $\Sigma\Delta$  noise has its own transform but is also LPF
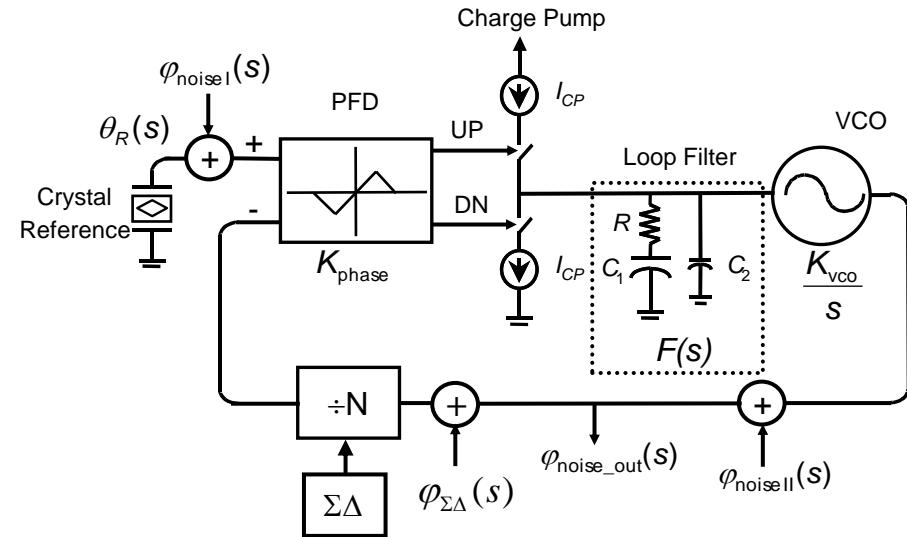
$$\frac{\varphi_{\text{noise\_out}}(s)}{\varphi_{\Sigma\Delta}(s)} = \frac{K_{\text{VCO}}K_{\text{phase}}(1 + sC_1R)}{s^2N(C_1 + C_2)(1 + sC_3R) + K_{\text{VCO}}K_{\text{phase}}(1 + sC_1R)}$$



# Example Phase Noise Calculations

- Continue with same specs as previous examples.
- VCO has PN = -120dBc/Hz @ 1MHz offset (bottoms at -130dBc/Hz), CP noise current =  $10\text{pA}/\sqrt{\text{Hz}}$
- Ignore all other noise what does PN plot look like? What if you needed to do this with only integer N?
- With Int N to get a step size of 1MHz need 1MHz reference so in that case N = 4000.
- With loop BW of 150KHz and damping const of 0.707 get C1 =141.5pF and R =21.2kΩ.
- will assume VCO falls at 20dB/decade thus VCO PN is:

$$C = \log^{-1}\left(\frac{PN_{VCO}}{10}\right) \cdot \Delta\omega^2 = \log^{-1}\left(\frac{-120}{10}\right) \cdot (2\pi \cdot 1\text{MHz})^2 = 39.5 \frac{\text{rad}^4}{\text{Hz}^2}$$

- VCO bottoms at -130dBc/Hz :

$$D = \log^{-1}\left(\frac{PN_{VCO}}{10}\right) = \log^{-1}\left(\frac{-130}{10}\right) = 10^{-13} \frac{\text{rad}^2}{\text{Hz}}$$

$$\phi^2_{VCO}(\Delta\omega) = \sqrt{\frac{39.5}{\Delta\omega^2} + 10^{-13}} \frac{\text{rad}}{\sqrt{\text{Hz}}}$$

- noise from CP can be input referred by dividing by  $K_{\text{Phase}}$

$$\text{Noise}_{CP} = \frac{i_n}{K_{\text{Phase}}} = \frac{10 \frac{\text{pA}}{\sqrt{\text{Hz}}}}{100 \frac{\mu\text{A}}{\text{rad}}} = 100\text{n} \cdot \frac{\text{rad}}{\sqrt{\text{Hz}}}$$

- Noise from the loop filter also moved back to input:

$$\text{Noise}_{LF}(\omega) = \frac{1}{K_{\text{Phase}}} \left| \sqrt{\frac{4kT}{R}} j\omega \right| \left| j\omega + \frac{1}{C_2 R} \right|$$

- Now need to transfer all noise to the output using appropriate TF


$$\phi_{\text{noise out}_{CP}}(s) = \frac{2.22 \cdot 10^{13}(1 + 3 \cdot 10^{-6}s)}{s^2 + 6.66 \cdot 10^5s + 2.22 \cdot 10^{13}} 100\text{n} \cdot \frac{\text{rad}}{\sqrt{\text{Hz}}}$$

- To plot PN in dBc/Hz:

$$PN_{CP}(\Delta\omega) = 20\log\left(\left|\frac{2.22 \cdot 10^{13}(1 + 3 \cdot 10^{-6}j\Delta\omega)}{j\Delta\omega^2 + 6.66 \cdot 10^5j\Delta\omega + 2.22 \cdot 10^{13}}\right| 100\text{n} \cdot \frac{\text{rad}}{\sqrt{\text{Hz}}}\right)$$

- Others done in similar way.
- To get total noise:
 
$$\phi_{\text{total}} = \sqrt{\phi_{\text{noise out}_{CP}}^2 + \phi_{\text{noise out}_{VCO}}^2 + \phi_{\text{noise out}_{LPF}}^2}$$




# Example Phase Noise Calculations

- Now can compute int PN:

$$IntPN_{rms} = \frac{180\sqrt{2}}{\pi} \sqrt{\int_{f=10kHz}^{f=10MHz} \phi_{total}^2 df} = 0.41$$

 - Using integer N specs results look like:



- Large division ratio clearly blows up in band noise!
- Clearly shows why you want frac N!

# PLL Reference Feedthrough

- If CP up and down currents aren't equal can cause constant correction even in the locked state.
- E.g. charge is added, creating a phase error that then needs to be removed next cycle.
- This causes spurs at the reference frequency to get modulated onto the VCO output.

