

Name: _____

Student Number: _____

1. Fig. 1.1 on p. 8 shows the layout of a circuit fabricated in the n-well CMOS technology used in Lab 2. The layout is not complete: the p+ mask is not shown. Draw the outline of this region (or regions) on the layout, and use cross-hatching to indicate the interior of the region. (Note: In this CMOS technology, by default any region which is not covered by the p+ layer receives the n+ implant) 4 marks

2. In the space provided below the layout in Fig. 1.1, carefully sketch a cross-section through the integrated circuit along line X-Y (i.e., show how the IC would look if cut along line X-Y and viewed from the side). Indicate the n-well and n+ and p+ regions on your cross-section. 16 marks

3. a) Underneath the layout of Fig. 1.1, draw the circuit schematic corresponding to the layout. Show the substrate (body) connection for each transistor. 10 marks
- b) On the circuit schematic, indicate which transistor(s) may have their threshold voltages modified by the body effect. 3 marks
- c) Determine the W/L ratio for each transistor and write it on the circuit schematic. 3 marks
- d) Complete the timing diagram in Fig. 3.1 below showing the output waveform Q produced by the circuit. "T" is short for "Toggle". Briefly explain your answer. 11 marks

 


Fig. 3.1

- e) Show how your schematic could be modified to provide an asynchronous reset capability that will force Q low when the reset line is high. 3 marks


Name: _____

Student Number: _____

 4. The layout of Fig. 1.1 is prone to latch-up. Explain why. Briefly explain how the layout could be modified to minimize the tendency for latch-up. 4 marks

The n-well and p-well contacts are not close to the well edges.

The contacts should be placed as follows:



5. a) Will the inverter in the circuit of Fig. 1.1 with input labelled "A" give equal output rise and fall times when driven by a square wave input swinging from 0 to V_{DD} ? Briefly explain. ~~5~~ 4 marks

This inverter has $w/L = 2$ for both pMOS pull-up and nMOS pull-down transistors. Since the holes in the pMOS channel have roughly half the mobility of the electrons in the nMOS channel, the rise time will be about twice as long as the fall time.

- b) Over what range does the voltage at node A actually swing? Explain briefly. ~~1~~ 2 mark

The voltage at node A is supplied through an nMOS transmission gate.

The highest it can rise (when the gate of the MOSFET switch is at V_{DD}) is $V_{DD} - V_T$.

Because of this, it is actually reasonable to use equal w/L for the nMOS and pMOS transistors in the inverter.

1/10

Name: _____

Student Number: _____

6. The circuit of Fig. 6.1 produces a voltage at node Y that is proportional to absolute temperature (PTAT).

 


Fig. 6.1 Base-emitter area of D2 is ten times that of D1

a) Assuming transistors M1 and M2 are ideal identical long channel devices operating in saturation, explain why the currents through M1 and M2 are equal. 4 marks

V_{GS} is the same for M1 and M2. In saturation I_D only depends on V_{GS} , so the currents must be equal.

b) Assuming transistors M3 and M4 are identical ideal long channel devices in saturation, explain why the voltage at node X is equal to the voltage at node Y. 4 marks


From part (a), M3 and M4 must carry the same current I_D . If they are in saturation, this means they must have the same V_{GS} — but the gates are at the same potential so the sources must be too.

Name: _____

Student Number: _____


- c) Suggest a modification to the circuit that could help keep the current through the left and right branches equal, even if M1 and M2 are not ideal. Draw a schematic for the modification. 4 marks

Cascode current mirror:

 

-- drains of M1 and M2 at nearly the same potential, which improves current matching.

 - d) The PTAT circuit requires use of a bipolar transistor. Sketch the structure of a lateral *pn*p bipolar transistor that can be made in a conventional n-well CMOS technology. Explain how the device should be biased to operate as a bipolar transistor. 6 marks



Bias: CB junction in reverse bias \therefore C negative relative to B
 BE junction in forward bias: E positive relative to B
~~trans~~ MOSFET channel turned off: V_G positive relative to E by at least $|V_{T_p}|$

Name: _____

Student Number: _____

7. Fig. 7.1 shows a cross-section through a high voltage MOSFET that could be made in a modified ELEC4609 nMOS process. The device has a lightly doped drain (LDD) region extending from the edge of the gate a distance L_D to a more heavily doped n^+ drain contact. The gate oxide thickness is 100 nm. The device is formed in a uniformly-doped (100) p -type substrate of 10 Ωcm resistivity. The polysilicon gate is heavily doped with phosphorus.

 


Fig. 7.1

a) If there is no threshold adjust implant, what backgate bias V_{SB} is required to give $V_{Tn} = 0.7$ V? (Note: the LDD region has no effect on V_T). 14 marks

$$V_{Tn} = V_{FB} + 2\phi_B + \sqrt{2\epsilon_s q N_A \frac{2\phi_B + V_{SB}}{C_{ox}}} \quad C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} = \frac{3.9(8.85 \times 10^{-14} \text{ F cm}^{-1})}{100 \times 10^{-7} \text{ cm}} = 3.45 \times 10^{-8} \text{ F cm}^{-2}$$

$$\rho = \frac{1}{q\mu_p N_A} \quad \therefore N_A = \frac{1}{q\mu_p \rho} = \frac{1}{(1.6 \times 10^{-19} \text{ C})(480 \text{ cm}^2 \text{ V}^{-1} \text{ s}^{-1})(10 \text{ cm})} = 1.3 \times 10^{15} \text{ cm}^{-3}$$

$$\phi_B = \frac{kT}{q} \ln\left(\frac{N_A}{n_i}\right) = 0.0259 \ln\left(\frac{1.3 \times 10^{15}}{10^{10}}\right) = 0.305 \text{ V}$$

$$\text{From band diagram } V_{FB} = -\frac{E_G}{2q} - \phi_B = -\frac{1.12 \text{ V}}{2} - 0.305 \text{ V} = -0.865 \text{ V}$$

$$2\epsilon_s q N_A (2\phi_B + V_{SB}) = C_{ox}^2 [V_{Tn} - V_{FB} - 2\phi_B]^2 \quad \therefore V_{SB} = \frac{C_{ox} (V_{Tn} - V_{FB} - 2\phi_B)^2}{2\epsilon_s q N_A} - 2\phi_B$$

$$V_{SB} = \frac{[(3.75 \times 10^{-8}) (0.7 + 0.865 - 0.610)]^2}{2(11.9)(8.85 \times 10^{-14})(1.6 \times 10^{-19})(1.3 \times 10^{15})} - 0.610 = 1.86 \text{ V}$$

Name: _____

Student Number: _____

- b) The LDD region is formed using a phosphorus implant with an energy of 20 keV and a dose of $3 \times 10^{13} \text{ cm}^{-2}$ followed by a drive-in diffusion at 1100°C for 10 minutes. All oxide is removed from the silicon surface prior to the implant. What is the metallurgical junction depth x_j for the n -LDD region? Show your work and state any assumptions made. 9 marks

Assume the profile is determined primarily by diffusion, so $C(x) = \frac{Q_{\text{impl}}}{\sqrt{\pi Dt}} e^{-x^2/4Dt}$

At the metallurgical junction $C(x) = N_A \quad \therefore \frac{Q_{\text{impl}}}{\sqrt{\pi Dt}} e^{-x_j^2/4Dt} = N_A \quad e^{-x_j^2/4Dt} = \frac{\sqrt{\pi Dt} N_A}{Q_{\text{impl}}}$

$$x_j = 2\sqrt{Dt} \left[\ln \left(\frac{Q_{\text{impl}}}{\sqrt{\pi Dt} N_A} \right) \right]^{1/2} \quad \text{from diffusion chart at } 1100^\circ\text{C } D \approx 10^{-13} \text{ cm}^2 \text{ s}^{-1}$$

$$\sqrt{Dt} = \sqrt{(10^{-13})(600)} = 7.75 \times 10^{-6} \text{ cm}$$

∴

$$\therefore x_j = 2(7.75 \times 10^{-6}) \left[\ln \left(\frac{3 \times 10^{13}}{\sqrt{\pi} (7.75 \times 10^{-6}) (1.03 \times 10^{15})} \right) \right]^{1/2} = 4.29 \times 10^{-5} \text{ cm} = 0.0429 \mu\text{m}$$

- c) Estimate the sheet resistance of the LDD region. 2 marks

$$R_s \approx \frac{1}{q \mu_n (Q_{\text{impl}})} = \frac{1}{(1.6 \times 10^{-19}) (1350 \text{ cm}^2 \text{ V}^{-1} \text{ s}^{-1}) (3 \times 10^{13} \text{ cm}^{-2})} = 154 \Omega/\square$$

↑ underestimate since μ_n is smaller than this

Name: _____

Student Number: _____

 


Fig. 1.1

